

Table of contents

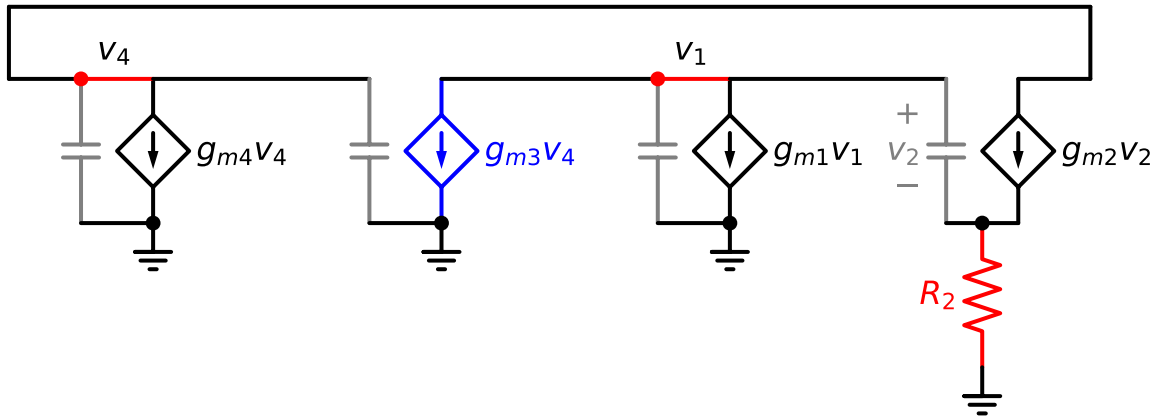


Figure 1: Small signal equivalent model for the constant- g_m bias circuit, (a) red: circuit features that make s_t insertion not possible, (b) blue: best place for s_t insertion