

## Table of contents

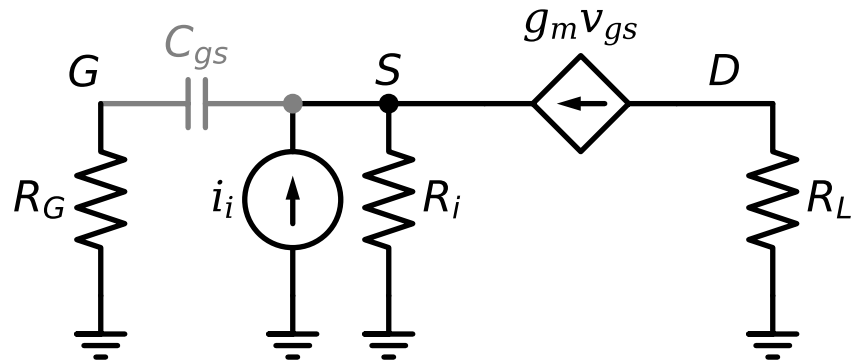


Figure 1: Small signal model for ZVTC calculations, assuming  $r_o$  can be ignored