

## Table of contents

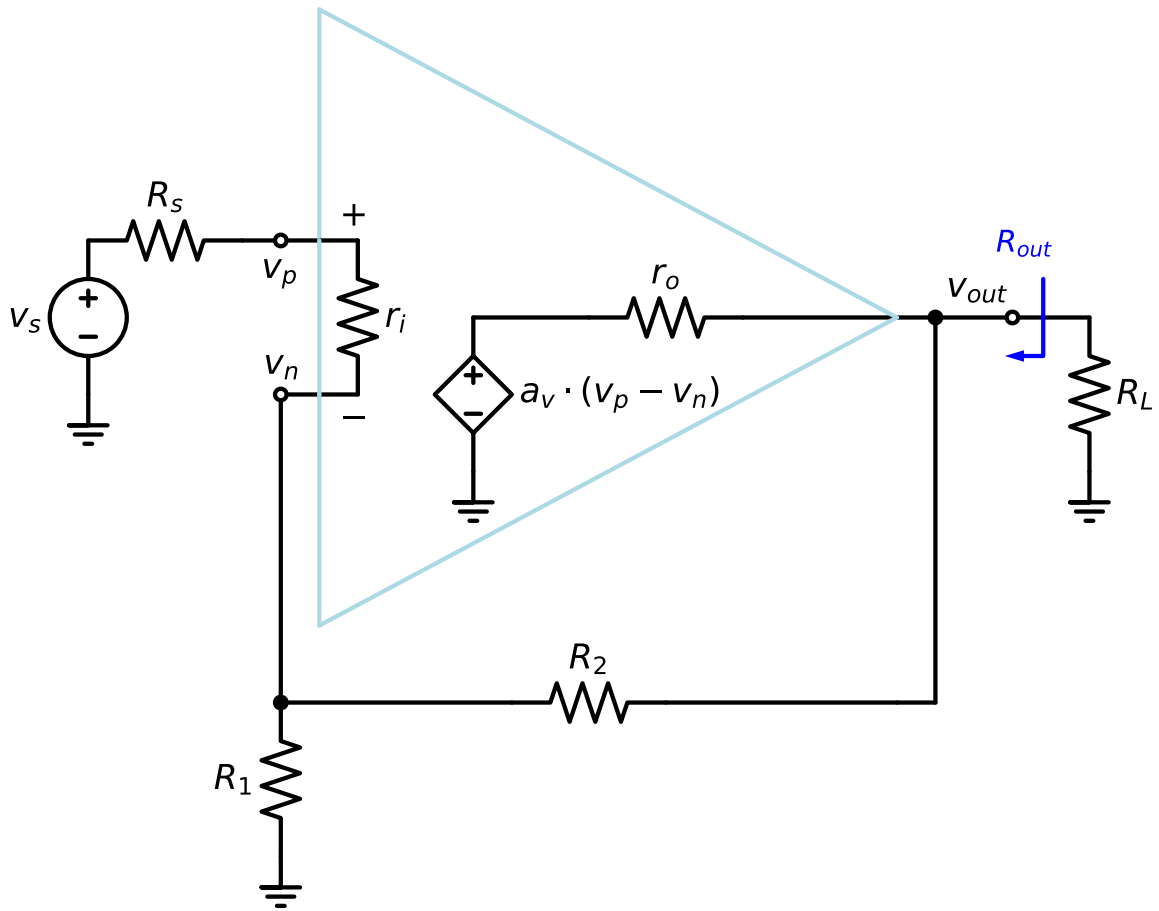


Figure 1: Output resistance of non-inverting op amp circuit