

Table of contents

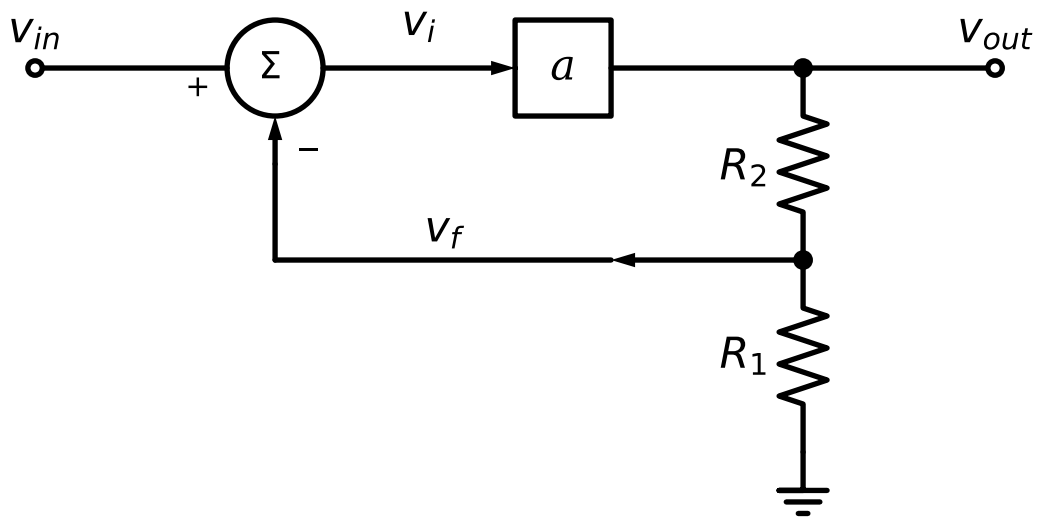


Figure 1: Block diagram of a non inverting voltage amplifier (series-shunt feedback)