

## Table of contents

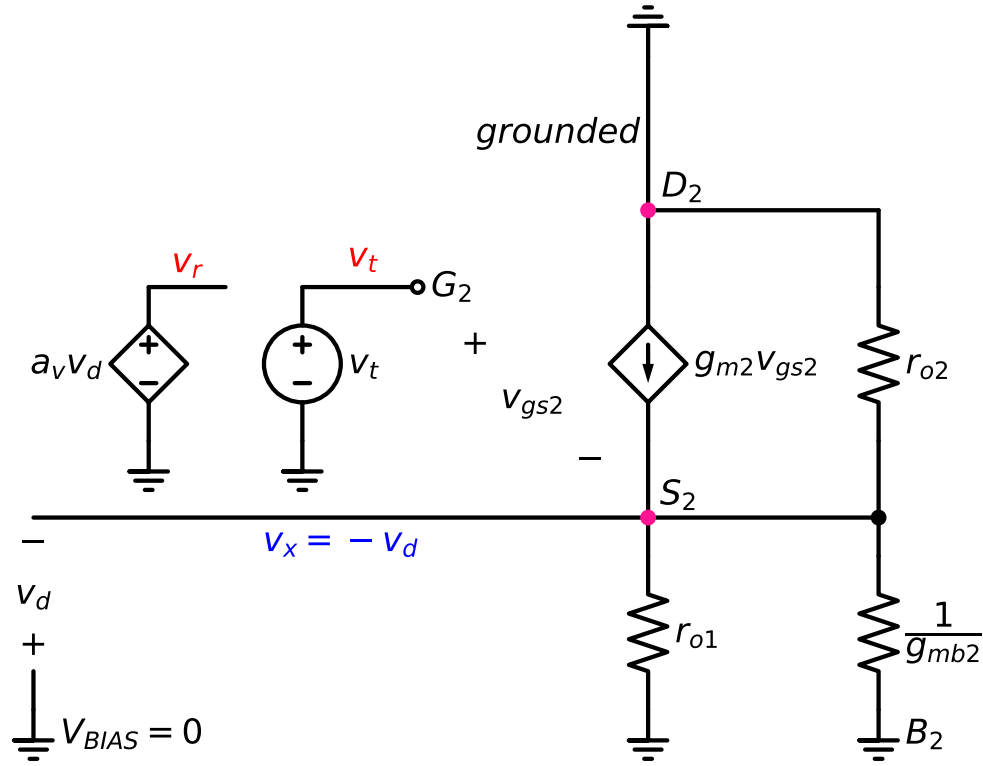


Figure 1: Return ratio for  $a_v$  with the output port shorted