

## Table of contents

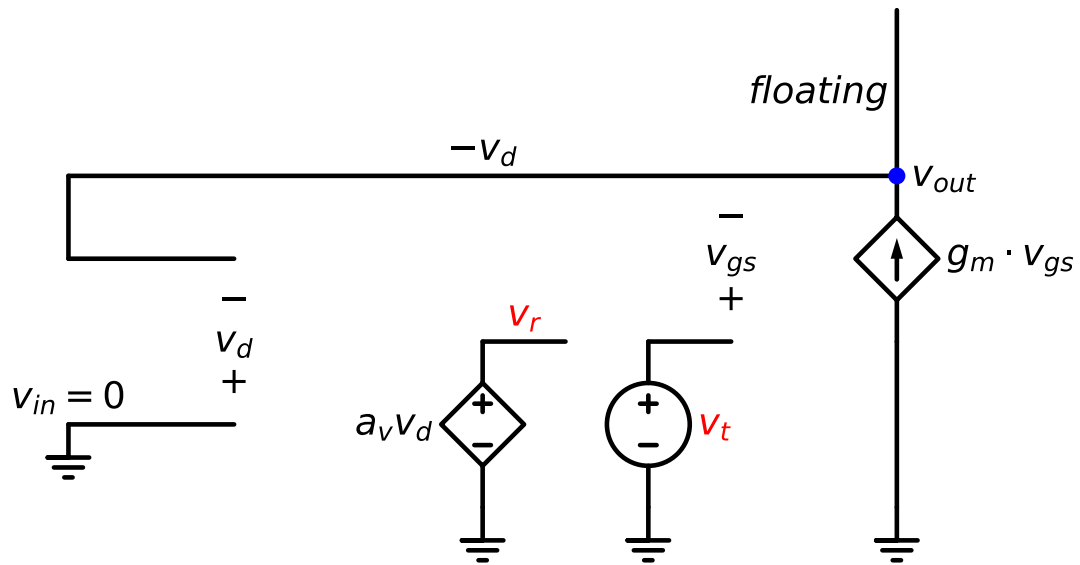


Figure 1: Finding T(with output port open),  $v_{out} = -v_d = -v_{gs} + v_t$