

Table of contents

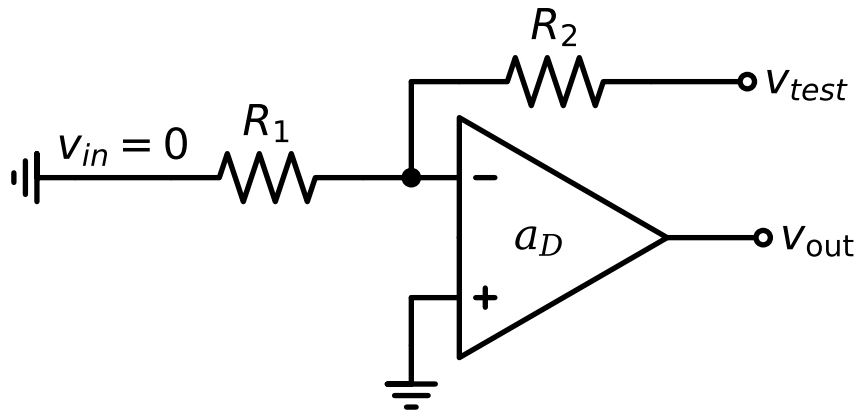


Figure 1: op amp based inverting amplifier with break in the loop ($v_{in} = 0$)