

# Introduction to Feedback

## Table of contents

<b>1</b>	<b>Preliminary Ideas</b>	<b>1</b>
<b>2</b>	<b>Types of Feedback</b>	<b>2</b>
<b>3</b>	<b>Negative Feedback</b>	<b>2</b>
<b>4</b>	<b>General negative feedback structure</b>	<b>2</b>
<b>5</b>	<b>Basic Terminology</b>	<b>3</b>
<b>6</b>	<b>The closed-loop gain</b>	<b>4</b>
<b>7</b>	<b>The error signal <math>s_e</math> and the feedback signal <math>s_f</math></b>	<b>8</b>
<b>8</b>	<b>Benefits of negative feedback)</b>	<b>9</b>
8.1	Gain Desensitivity . . . . .	9
8.2	Effect of feedback on non-linearity . . . . .	9
8.3	Effect of feedback on bandwidth . . . . .	10
8.4	Effect of feedback on input/output resistances . . . . .	10
8.4.1	Series-shunt (voltage-voltage) feedback configuration - Voltage Amplifier	12
8.4.2	Shunt-shunt (current-voltage) feedback configuration - Transimpedance Amplifier . . . . .	13
8.4.3	Series-series (voltage-current) feedback configuration - Transconductance Amplifier . . . . .	13
8.4.4	Shunt-series (current-current) feedback configuration - Current Amplifier	16
<b>9</b>	<b>Feedback analysis of op amp circuits</b>	<b>17</b>
9.1	Non Inverting configuration . . . . .	19
9.2	Inverting configuration . . . . .	21
9.3	Comparison between non-inverting and inverting topology . . . . .	24

9.4	The four feedback configurations using op amps . . . . .	25
9.4.1	Series-Shunt (voltage-voltage) configuration (Voltage Amplifier) . . . . .	25
9.4.2	Shunt-Shunt (current-voltage) configuration (Transimpedance Amplifier) . . . . .	26
9.4.3	Series-Series (voltage-current) configuration (Transconductance Amplifier) . . . . .	28
9.4.4	Shunt-Series (current-current) configuration (Current Amplifier) . . . . .	28
<b>10</b>	<b>Systematic Feedback Analysis Frameworks</b>	<b>28</b>
10.1	Return Ratio Analysis . . . . .	31
10.1.1	Closed-loop gain using return ratio . . . . .	31
10.1.2	Closed-loop impedances using return ratio . . . . .	44
10.1.3	Summary - return ratio analysis . . . . .	62

## 1 Preliminary Ideas

In electronics the term **feedback** refers to the situation where a signal **sensed** (or derived or sampled or measured) from the output port of an amplifier is **returned** to the input port, where it is **combined** (or mixed) with the externally applied input signal to create a new signal to be processed by the amplifier itself.

- when the returned signal is added to the external signal, we have positive feedback,
- when the returned signal is subtracted we have negative feedback.

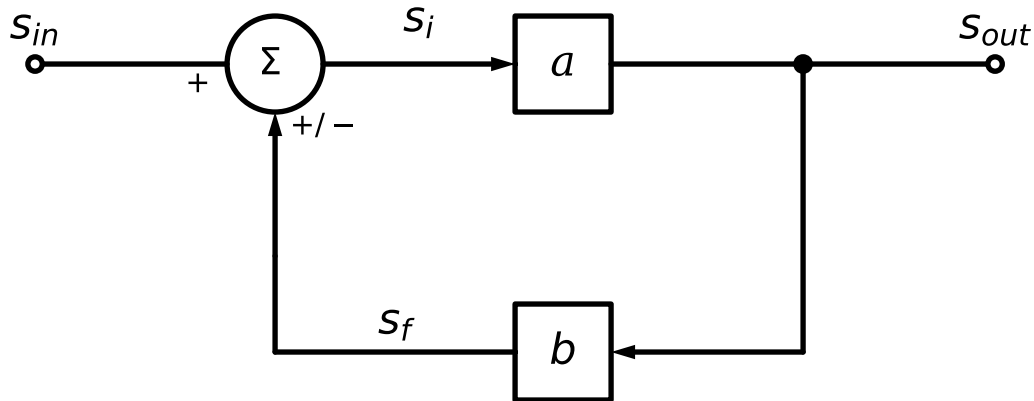


Figure 1: Block diagram of a feedback system.

## 2 Types of Feedback

- Positive feedback (a.k.a. regenerative feedback)
- Negative feedback (a.k.a. degenerative feedback)

Negative Feedback was conceived in 1928 by Harold Black

### **Examples of negative fb circuits we have already seen**

- op amp based amplifiers
- CS (CE) with degeneration  $\rightarrow$  series-series (voltage-current) feedback topology
- CD (CC) a.k.a. voltage follower  $\rightarrow$  series-shunt (voltage-voltage) feedback topology

## **3 Negative Feedback**

- Basic Idea
  - trade off gain for other desirable properties
- Desirable properties
  - desensitize gain
  - extend the bandwidth
  - control input and output impedance
  - reduce NL distortion
- Drawbacks (undesired properties)
  - reduced gain
  - under certain circumstances the negative feedback in an amplifier can become positive and of such a magnitude as to cause oscillations (instability)

**NOTE:** it should not be implied that positive feedback always lead to instability

## **4 General negative feedback structure**

- Assumptions (ideal feedback)
  - The feedback network does not load the basic amplifier output
  - The feedback network does not load the basic amplifier input
  - The feedback network is unilateral
  - The basic amplifier is unilateral

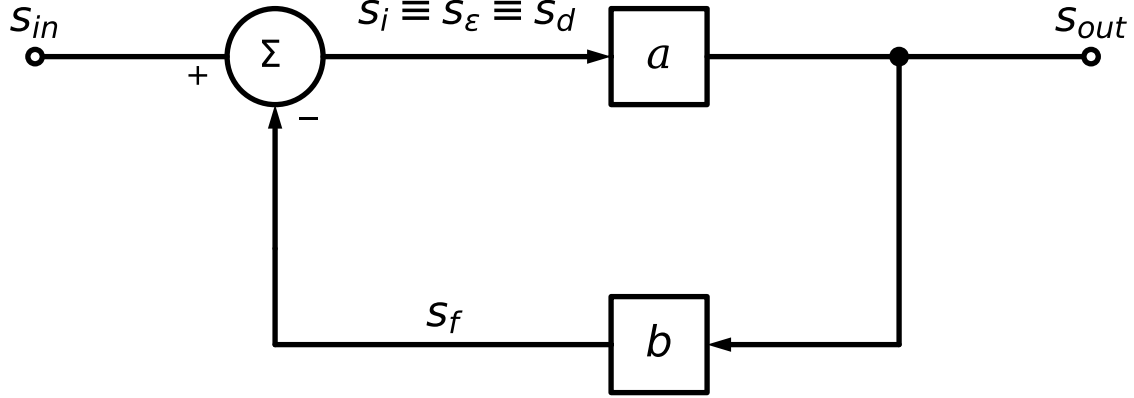


Figure 2: Block diagram of a negative feedback system.

The feedback network measures (or sample or sense) the output signal  $s_{out}$  and provides (returns) a feedback signal  $s_f$  (that is related to  $s_{out}$  by the **feedback factor**  $b$ )

$$\begin{aligned} s_{out} &= a \cdot s_i \\ s_f &= b \cdot s_{out} \\ s_\epsilon \equiv s_d \equiv s_i &= s_{in} - s_f \end{aligned}$$

$$A = \frac{s_{out}}{s_{in}} = \frac{s_{out}}{s_i + s_f} = \frac{1}{\frac{s_i}{s_{out}} + \frac{s_f}{s_{out}}} = \frac{1}{\frac{1}{a} + b} = \frac{a}{1 + ab} \approx \frac{1}{b}$$

This is a key result: for  $ab \gg 1 \Rightarrow A \approx \frac{1}{b}$

## 5 Basic Terminology

$s_{in}$  = input signal applied to the feedback system

$s_{out}$  = output signal from the feedback system

$a = \frac{s_{out}}{s_i}$  = open-loop gain = gain “basic” amplifier = gain feedforward amplifier

$b$  = feedback factor

$a \cdot b = L$  = loop gain (it is always unit-less)

$1 + ab = 1 + L$  = amount of feedback

$s_i \equiv s_e \equiv s_d = s_{in} - s_f = \text{input to "basic" amplifier} = \text{error} = \text{difference}$

$A = \frac{s_{out}}{s_{in}} = \text{closed-loop gain} = \text{gain of feedback system}$

## 6 The closed-loop gain

$$\begin{aligned} A &= \frac{a}{1 + ab} = \frac{1}{b} \cdot \frac{1}{1 + 1/(ab)} = \\ &= \frac{1}{b} \cdot \frac{1}{1 + \frac{1}{L}} \\ &= \frac{1}{b} \cdot \frac{L}{1 + L} \approx \frac{1}{b} \end{aligned}$$

The most important benefit coming from the use of negative feedback is under the condition  $L \gg 1$ :

- For  $L \gg 1$  the actual gain  $A(\approx 1/b)$  is virtually independent of the open-loop gain  $a$ . The open-loop gain  $a$  is an extremely inaccurate parameter, and varies significantly subject to drift with temperature, supply voltage, fabrication process, and DC biasing conditions.

Although physically unattainable the limit  $L \rightarrow \infty$  represent the ideal condition:

$$A_{ideal} \equiv A_{\infty} = \lim_{L \rightarrow \infty} A = \frac{1}{b}$$

Key result: when the loop gain  $L$  is large, the closed loop gain  $A$  approaches the ideal closed loop gain  $A_{ideal}$ , which is equal to  $1/b$

To achieve gain we need  $b \leq 1$ .

$b \leq 1$  is easy to implement. We can for example use a wire ( $b = 1$ ), or a resistive divider (ratiometric) or a capacitive divider (ratiometric).

### Example 1 - voltage follower

$$v_f = v_{out} \Rightarrow b = v_f/v_{out} = 1$$

$$v_{out} = a \cdot (v_{in} - v_{out})$$

$$v_{out}(1 + a) = a \cdot v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{a}{1 + a} \approx 1$$

### Example 2 - non-inverting voltage amplifier

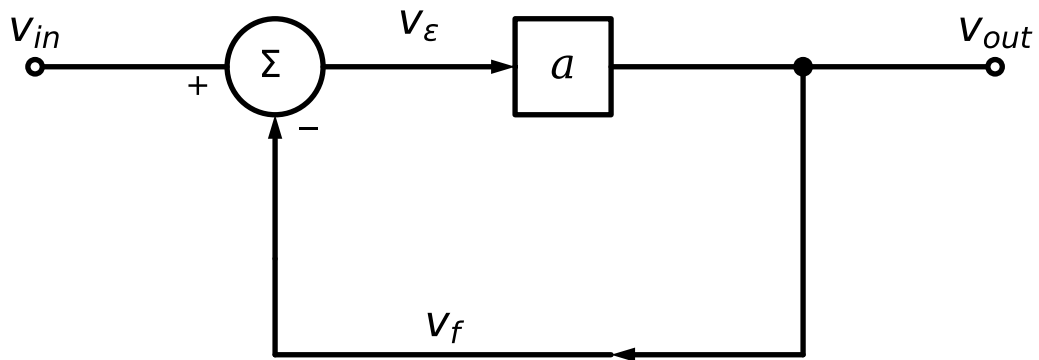


Figure 3: Block diagram of a voltage follower.

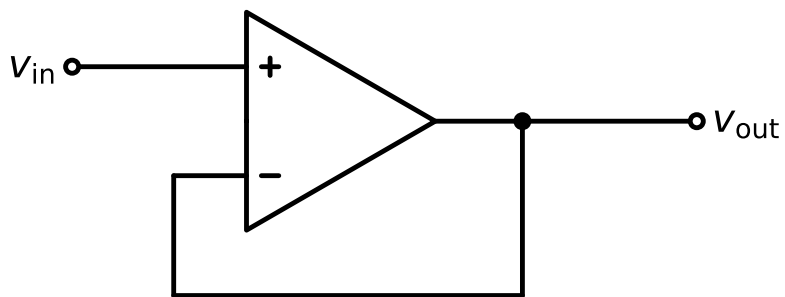


Figure 4: op amp based voltage follower

$$b = \frac{v_f}{v_{out}} = \frac{R_1}{R_1 + R_2}$$

$$\frac{v_{out}}{v_{in}} \approx \frac{1}{b} = 1 + \frac{R_2}{R_1}$$

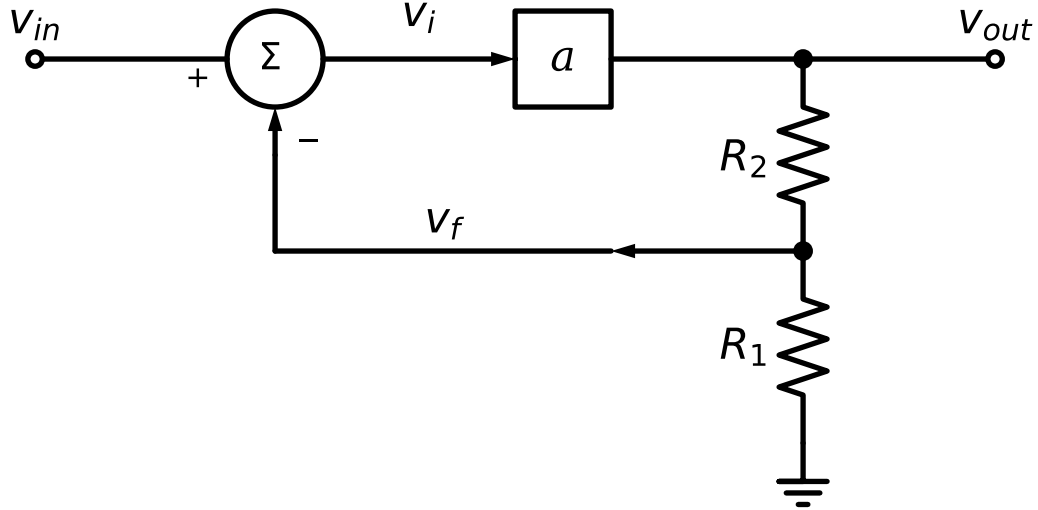


Figure 5: Block diagram of a non inverting voltage amplifier (series-shunt feedback)

If we regard  $1/L$  as an error term, then  $L$  gives a measure of how close the actual gain  $A$  is to the ideal gain  $A_{ideal} = 1/b$ .

$$A = \frac{1}{b} \cdot \frac{1}{1 + \frac{1}{L}} \approx \frac{1}{b} \cdot \left(1 - \frac{1}{L}\right)$$

The % gain error between actual gain  $A$  and ideal gain  $A_{ideal}$  is usually defined as follows:

$$\begin{aligned} \text{gainerror}\% &= 100 \times \frac{A - A_{ideal}}{A_{ideal}} = 100 \times \frac{A_{ideal} \cdot \left(\frac{1}{1 + 1/L}\right) - A_{ideal}}{A_{ideal}} = \\ &= 100 \times \frac{-1}{1 + L} \approx 100 \times \frac{-1}{L} \end{aligned}$$

### Example 3 - op amp based non inverting voltage amplifier

KLC at node  $v_{out}$ :

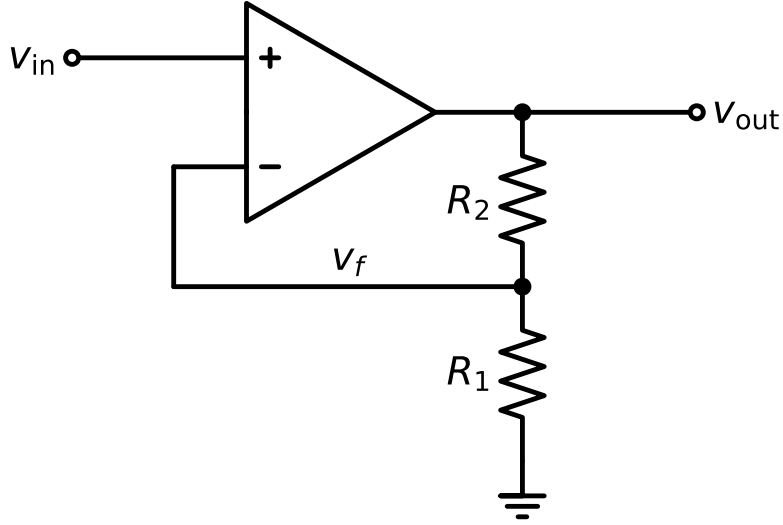


Figure 6: op amp based non inverting voltage amplifier

$$\frac{v_N - v_{out}}{R_2} = \frac{v_{out} - a_D \cdot (v_{in} - v_N)}{r_o}$$

KCL at node  $v_N$ :

$$\frac{v_N - v_{in}}{r_i} + \frac{v_N}{R_1} + \frac{v_N - v_{out}}{R_2} = 0$$

For  $a_D = 10^6$ ,  $r_i = 10M\Omega$ ,  $r_o = 10\Omega$ ,  $R_1 = 20k\Omega$  and  $R_2 = 80k\Omega$ :

$$A_{ideal} = \frac{R_1 + R_2}{R_1}$$

$$A = \frac{v_{out}}{v_{in}} = \frac{a_D \cdot r_i (R_1 + R_2) + R_1 r_o}{a_D \cdot R_1 r_i + r_o (R_1 + r_i) + R_1 R_2 + r_i (R_1 + R_2)} = 4.999975$$

$$gainerror = \frac{4.999975 - 5}{5} = -5 \cdot 10^{-6} = -5ppm$$

The exact analysis is very tedious and does not provide any useful insight compared to the feedback analysis.



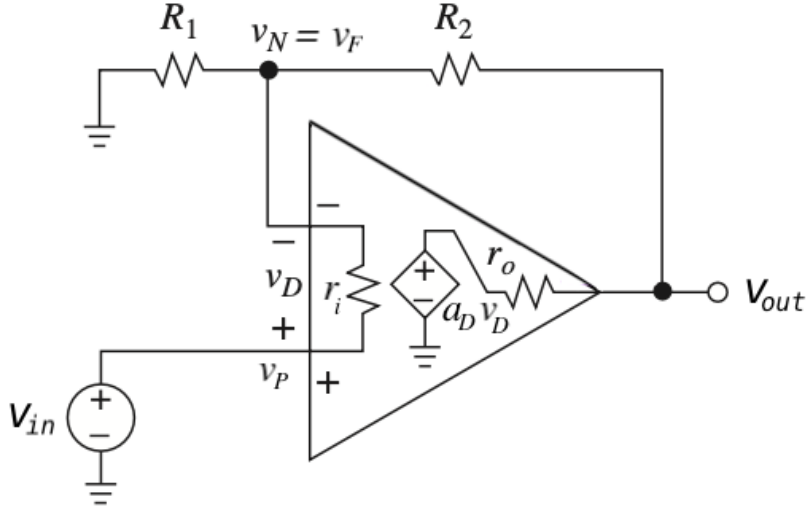


Figure 7: Non inverting voltage amplifier with non ideal op amp (Franco 2015)

## 7 The error signal $s_\epsilon$ and the feedback signal $s_f$

From Figure 2

$$\begin{aligned} s_\epsilon &= \frac{s_{out}}{a} = \frac{A \cdot s_{in}}{a} = \frac{\phi'}{1+L} \cdot \frac{s_{in}}{\phi} \\ &= \frac{s_{in}}{1+L} \end{aligned}$$

also

$$\begin{aligned} s_f &= b \cdot s_{out} = b \cdot A \cdot s_{in} = \cancel{b} \cdot \frac{1}{\cancel{b}} \frac{1}{1+1/L} \cdot s_{in} \\ &= \frac{s_{in}}{1+1/L} \end{aligned}$$

These results show that for a large loop gain (ideally for  $L \rightarrow \infty$ ), the error signal becomes very small (ideally  $s_\epsilon \rightarrow 0$ ), causing the feedback signal  $s_f$  to closely follow the input signal  $s_{in}$  ( $s_f \rightarrow s_{in}$ )

## 8 Benefits of negative feedback)

### 8.1 Gain Desensitivity

To investigate the effect that a variation on the open-loop gain  $a$  causes on the closed-loop gain  $A$  we differentiate  $A$  w.r.t.  $a$

$$A = \frac{a}{1 + ab}$$

$$\frac{dA}{da} = \frac{1 + ab - ab}{(1 + ab)^2} = \frac{1}{(1 + ab)^2}$$

$$\Delta A = \frac{\Delta a}{(1 + ab)^2}$$

$$\frac{\Delta A}{A} = \frac{\Delta a}{A} \cdot \frac{1}{(1 + ab)^2} = \frac{\Delta a}{\frac{a}{1 + ab}} \cdot \frac{1}{(1 + ab)^2} = \frac{\Delta a/a}{(1 + ab)}$$

Thanks to feedback, a fractional change in the gain of the basic amplifier is reduced by a factor  $1 + L = 1 + ab$  in the closed-loop. Conceptually, the loop gain  $L$  can be made arbitrarily large. The loop gain is a key parameter and as we will see later it plays an important role also in bandwidth and impedance calculations.

### 8.2 Effect of feedback on non-linearity

Amplifiers are made up of transistors. Since, transistors are non linear devices, the transfer characteristic of any practical amplifier is non-linear. Assume a basic amplifier that besides the desired linear relationship, also exhibits a cubic relationship between its input and output.

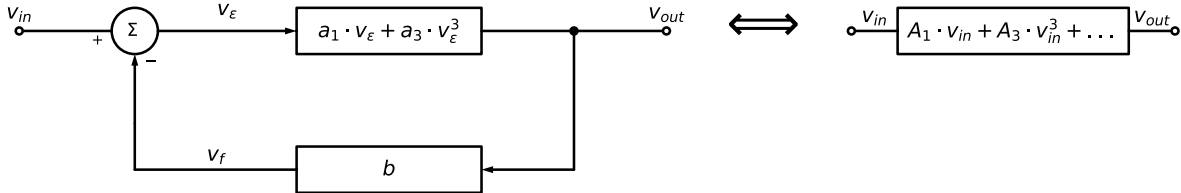


Figure 8: Effect of negative feedback on non-linearity

$$v_{out} = a_1(v_{in} - bv_{out}) + a_3(v_{in} - bv_{out})^3 \quad (1)$$

$$v_{out} = A_1 v_{in} + A_3 v_{in}^3 + \dots \quad (2)$$

Substituting Equation 2 into Equation 1 we get:

$$\begin{aligned} v_{out} &= a_1(v_{in} - bA_1 v_{in} - bA_3 v_{in}^3 - \dots) + a_3(v_{in} - bA_1 v_{in} - bA_3 v_{in}^3 - \dots)^3 \\ &= a_1 v_{in} - a_1 b A_1 v_{in} - a_1 b A_3 v_{in}^3 + a_3 [v_{in}(1 - bA_1)]^3 + \dots \end{aligned}$$

and equating back into Equation 2:

$$A_1 v_{in} = a_1 v_{in} - a_1 b A_1 v_{in} \leftrightarrow A_1 (1 + a_1 b) = a_1$$

$$A_1 = \frac{a_1}{1 + a_1 b}$$

$$A_3 v_{in}^3 = -a_1 b A_3 v_{in}^3 + a_3 v_{in}^3 (1 - b A_1)^3 \leftrightarrow A_3 (1 + a_1 b) = a_3 (1 - b \frac{a_1}{1 + a_1 b})^3 = a_3 \frac{1}{(1 + a_1 b)^3}$$

$$A_3 = \frac{a_3}{(1 + a_1 b)^4}$$

The linear term (as expected) is reduced by  $1 + L$ .

The cubic term is reduced by  $(1 + L)^4$ .

### 8.3 Effect of feedback on bandwidth

As an example, assume the transfer function of the basic amplifier is the following:

$$a(j\omega) = \frac{a_0}{1 + \frac{j\omega}{\omega_p}}$$

Then, the closed-loop transfer function is

$$A(j\omega) = \frac{a(j\omega)}{1 + a(j\omega) \cdot b} = \frac{a_0}{1 + a_0 b} \cdot \frac{1}{1 + \frac{j\omega}{\omega_p} \cdot \frac{1}{(1 + a_0 b)}}$$

The gain is reduced by  $1 + L_0$ , but the bandwidth is increased by  $1 + L_0$ .

The product of gain and bandwidth remains constant

### 8.4 Effect of feedback on input/output resistances

In actual applications the input and output resistances (a.k.a. terminal resistances) of the amplifier play a key role. When an amplifier is driven by a non ideal source and drives an output load, the input resistance forms a divider with the source's resistance, and the output resistance forms a divider with the load, therefore reducing the overall gain from source to load. This reduction is usually referred as loading effect. Negative feedback modifies the terminal resistances in ways that tend to reduce the impact of loading.

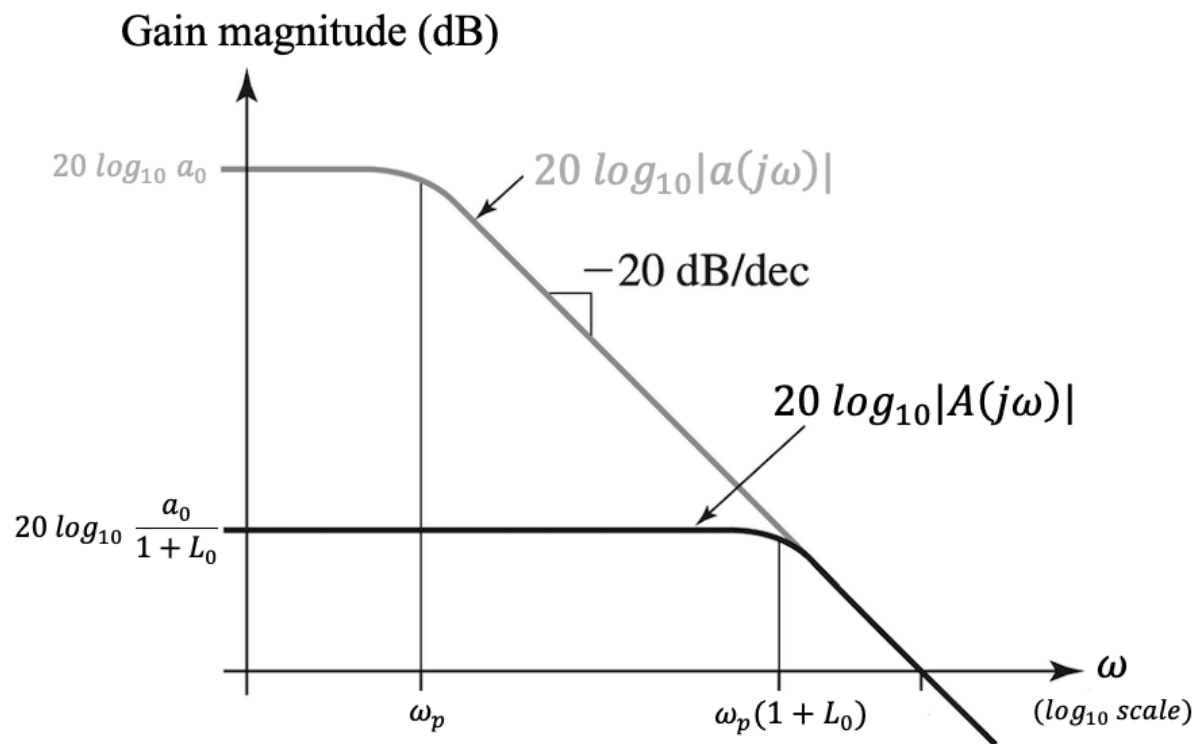


Figure 9: Gain magnitude vs. frequency for the basic amplifier and the feedback amplifier

### 8.4.1 Series-shunt (voltage-voltage) feedback configuration - Voltage Amplifier

Let's consider the application of negative feedback around a voltage amplifier. In this case feedback is performed sampling the output voltage and then feeding back a voltage that is a scaled version of the output voltage “into” the external input voltage source driving the amplifier. Note that the operation of voltage sensing at the output is performed in parallel, or shunt (when we measure a voltage we place the voltmeter in parallel, never in series), while to combine the external input voltage source and the voltage returned by the feedback network we connect them in series (to connect two voltage sources we place them in series, never in parallel).

To focus on the effect of negative feedback on  $r_i$  and  $r_o$  of the basic amplifier, we assume there is no loading effect on both ports of the basic amplifier. To neglect loading at the input's of the basic amplifier, we assume that the sources  $v_{in}$  and  $bv_{out}$  have *zero* series resistances. To neglect loading at the output's port of the basic amplifier, we assume the output port of the basic amplifier is left open and the input port of the feedback network has *infinite* resistance.

Note: for the series-shunt feedback configuration,  $b$  is unitless.

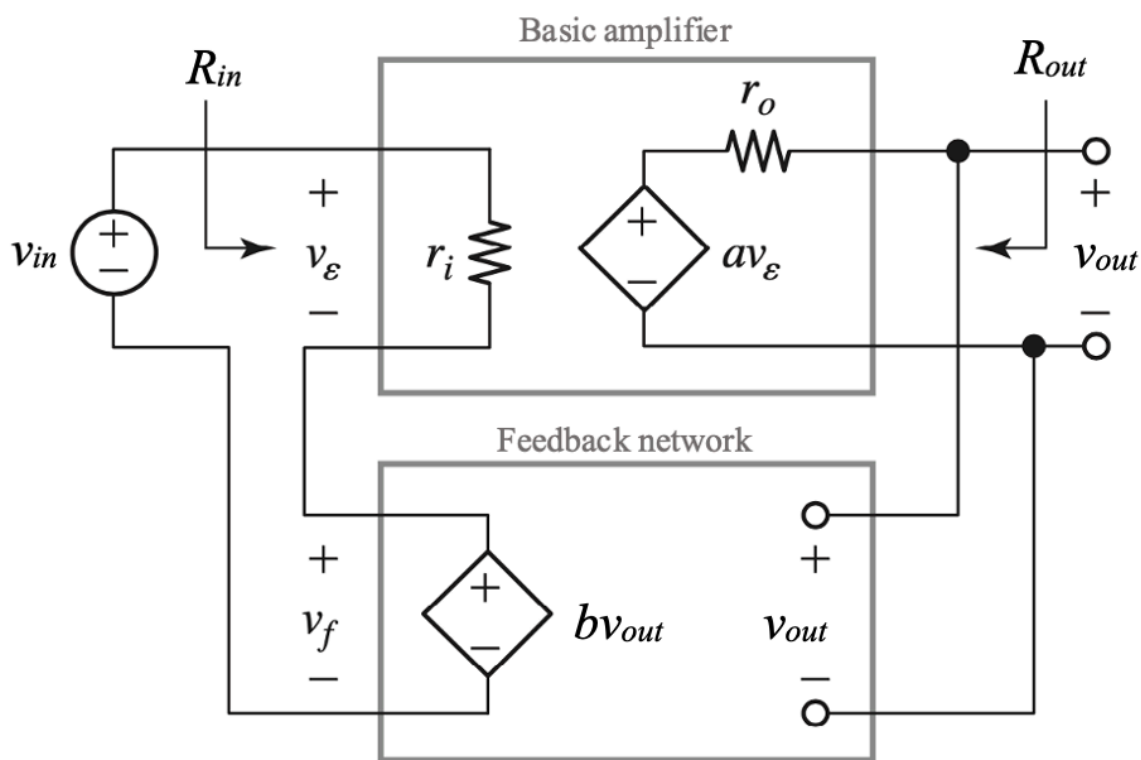


Figure 10: The ideal series-shunt configuration or voltage amplifier (Franco 2015)

$$R_{in} = \frac{v_x}{i_x} = r_i(1 + L)$$

$$R_{out} = \frac{v_t}{i_t} = \frac{r_o}{1 + L}$$

For  $L \rightarrow \infty$  the series-shunt configuration gives  $R_{in} \rightarrow \infty$  and  $R_{out} \rightarrow 0$

#### 8.4.2 Shunt-shunt (current-voltage) feedback configuration - Transimpedance Amplifier

Let's consider the application of negative feedback around a transimpedance amplifier. In this case feedback is performed sampling the output voltage and then feeding back a current that is a scaled version of the output voltage “into” the external input current source driving the amplifier. Note that to combine the external input current source and the current returned by the feedback network we connect them in parallel or shunt (to connect two current sources we place them in parallel, never in series).

To neglect loading at the input's of the basic amplifier, we assume that the sources  $i_{in}$  and  $bv_{out}$  have *infinite* parallel resistances. To neglect loading at the output's port of the basic amplifier, we assume the output port of the basic amplifier is left open and the input port of the feedback network has *infinite* resistance.

Note: for the shunt-shunt feedback configuration,  $b$  has dimensions of  $1/\Omega$ .

$$R_{in} = \frac{r_i}{1 + L}$$


$$R_{out} = \frac{r_o}{1 + L}$$

For  $L \rightarrow \infty$  the shunt-shunt configuration gives  $R_{in} \rightarrow 0$  and  $R_{out} \rightarrow 0$

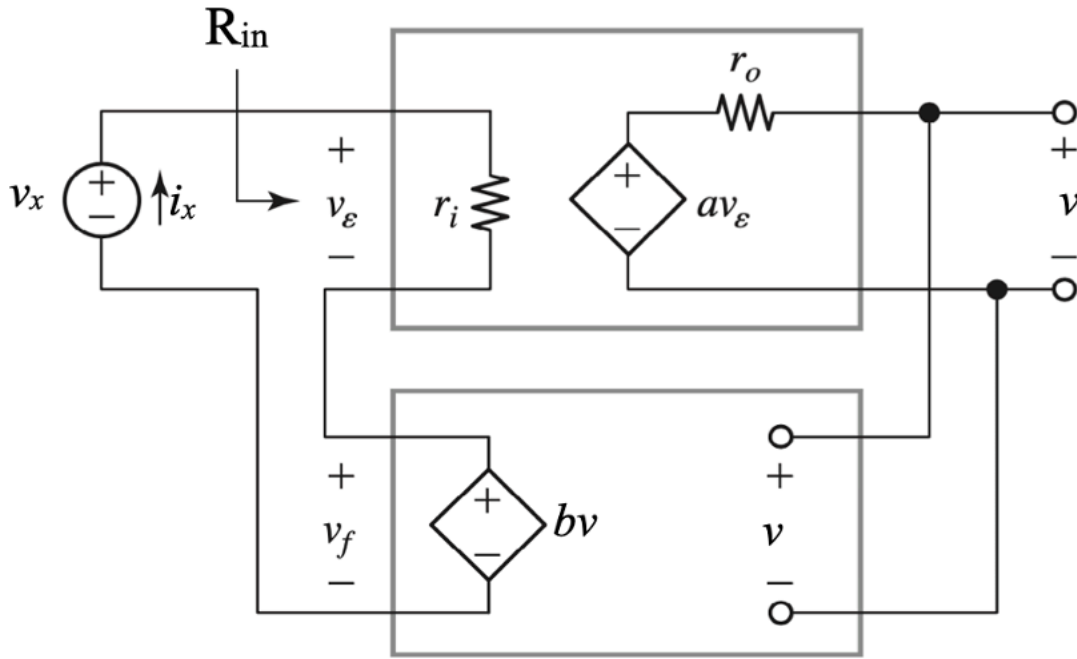
#### 8.4.3 Series-series (voltage-current) feedback configuration - Transconductance Amplifier

Let's consider the application of negative feedback around a transconductance amplifier. In this case feedback is performed sampling the output current and then feeding back a voltage that is a scaled version of the output current “into” the external input voltage source driving the amplifier. Note that the operation of current sensing at the output is performed in series, or shunt (when we measure a current we place the ampmeter in series, never in parallel).

To neglect loading at the input's of the basic amplifier, we assume that the sources  $v_{in}$  and  $bi_{out}$  have *zero* series resistances. To neglect loading at the output's port of the basic amplifier,



(a)

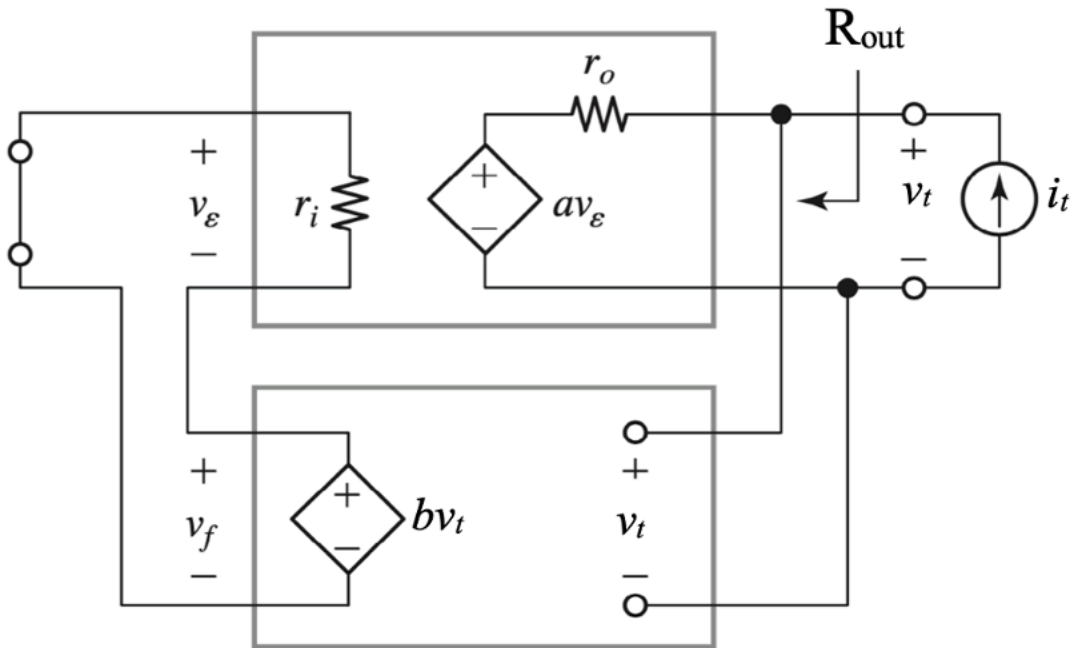

(b)

Figure 11: (a) test circuit for the calculation of the input impedance and (b) test circuit for the calculation of the output impedance

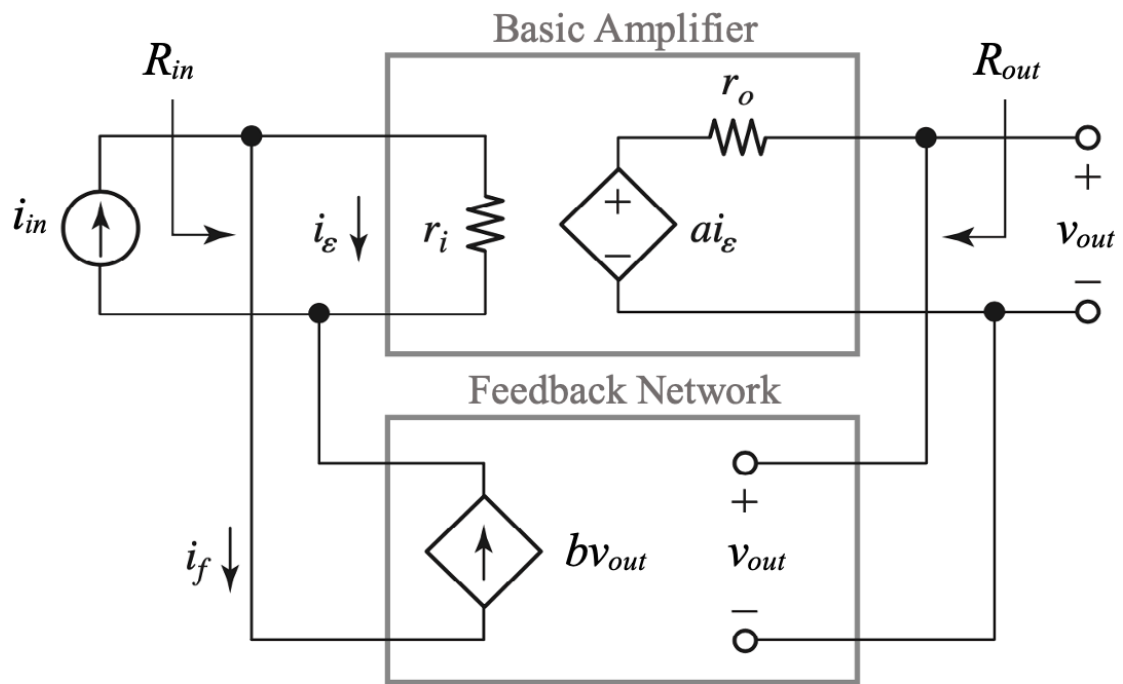


Figure 12: The ideal shunt-shunt configuration or transimpedance amplifier (Franco 2015)



we assume the output port of the basic amplifier is shorted and the input port of the feedback network has *zero* resistance.

Note: for the series-series feedback configuration,  $b$  has dimensions of  $\Omega$ .

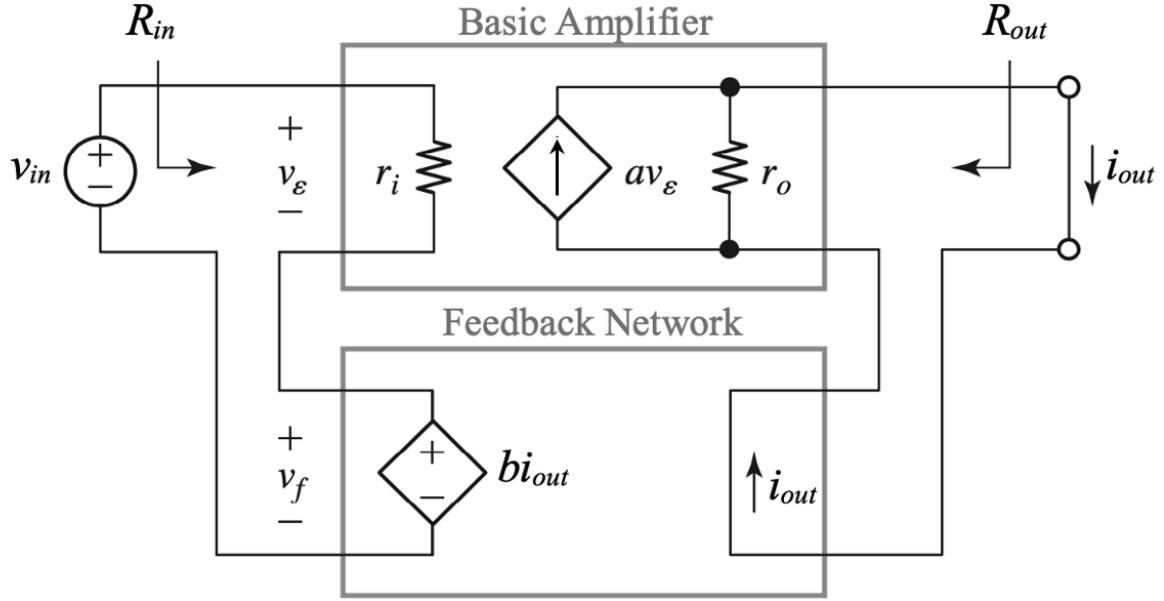


Figure 13: The ideal series-series configuration or transconductance amplifier (Franco 2015)

$$R_{in} = r_i(1 + L)$$

$$R_{out} = r_o(1 + L)$$

For  $L \rightarrow \infty$  the series-series configuration gives  $R_{in} \rightarrow \infty$  and  $R_{out} \rightarrow \infty$

#### 8.4.4 Shunt-series (current-current) feedback configuration - Current Amplifier

Let's consider the application of negative feedback around a current amplifier. In this case feedback is performed sampling the output current and then feeding back a current that is a scaled version of the output current “into” the external input current source driving the amplifier.

To neglect loading at the input's of the basic amplifier, we assume that the sources  $i_{in}$  and  $bi_{out}$  have *infinite* parallel resistances. To neglect loading at the output's port of the basic

amplifier, we assume the output port of the basic amplifier is shorted and the input port of the feedback network has *zero* resistance.

Note: for the shunt-series feedback configuration,  $b$  is unitless.

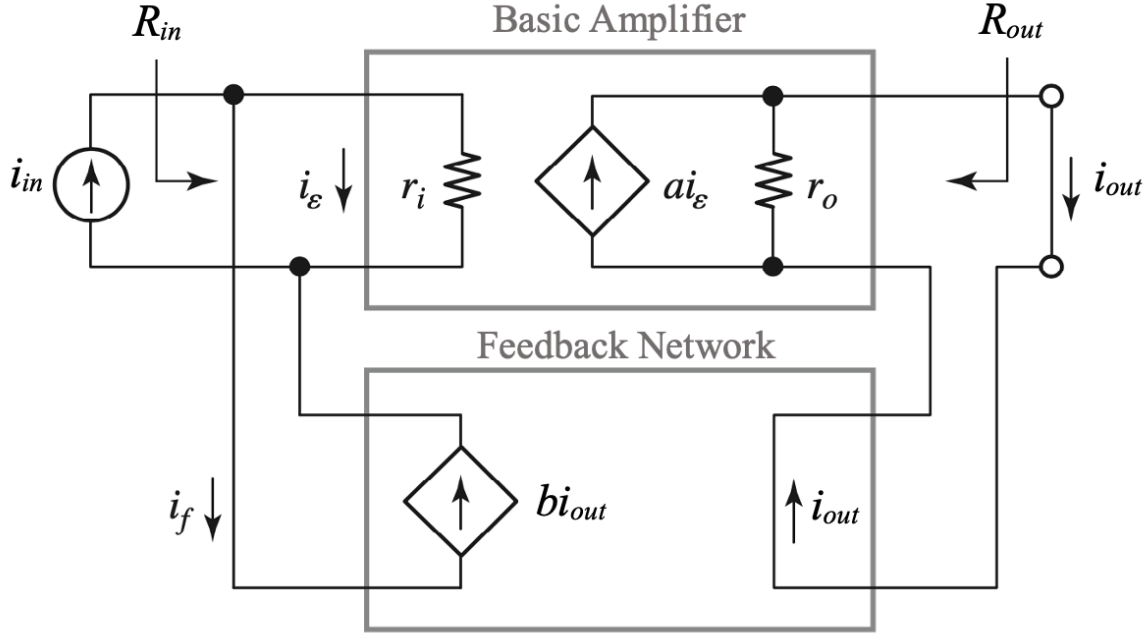


Figure 14: The shunt-series configuration or current amplifier (Franco 2015)

$$R_{in} = \frac{r_i}{1 + L}$$

$$R_{out} = r_o(1 + L)$$

For  $L \rightarrow \infty$  the shunt-series configuration gives  $R_{in} \rightarrow 0$  and  $R_{out} \rightarrow \infty$

## 9 Feedback analysis of op amp circuits

In typical op amp circuits  $r_i$  and  $r_o$  are negligible compared to the resistances used in the feedback network.

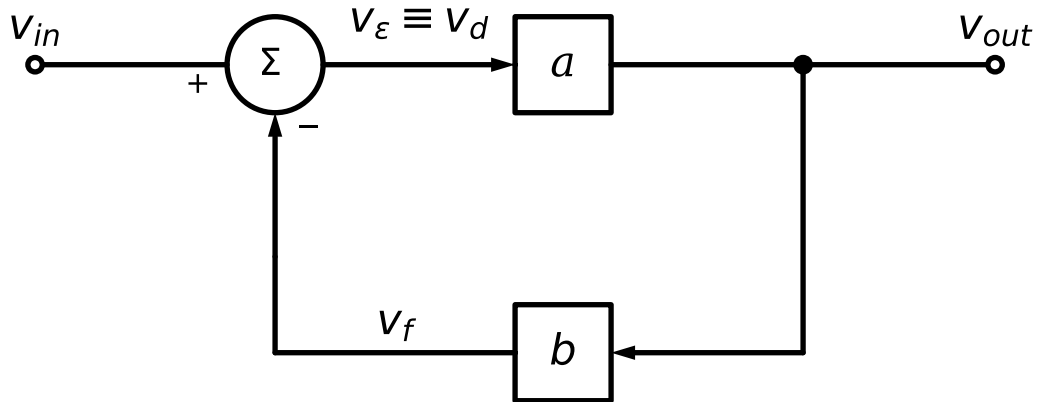


Figure 15: Block diagram of negative feedback system.

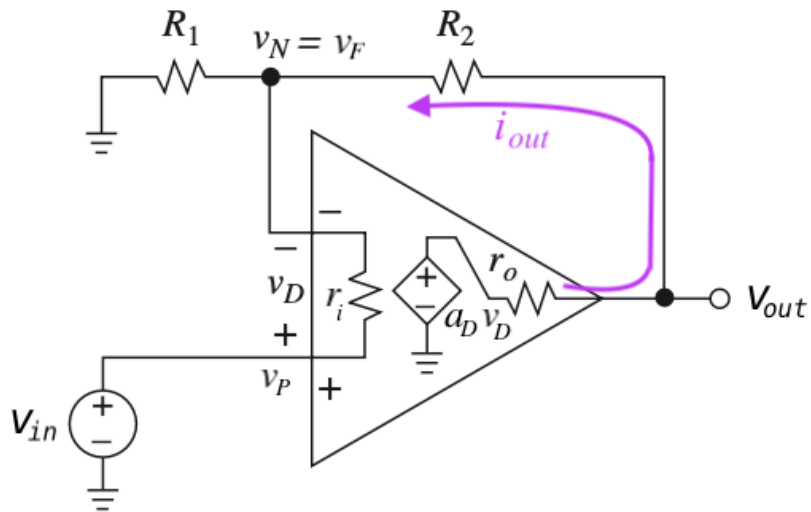


Figure 16: Non inverting op amp amplifier (Franco 2015).

## 9.1 Non Inverting configuration

For identifying  $a$  and  $b$  directly from the circuit, we can set  $v_{in} = 0$  and note that with  $v_{in} = 0$

$$i_{out} = \frac{v_{out}}{R_2 + R_1 || r_i} = \frac{a_D v_D}{r_o + R_2 + R_1 || r_i}$$

$$v_f = -v_D = i_{out} \cdot (R_1 || r_i)$$

$$v_{out} = i_{out} \cdot (R_2 + R_1 || r_i)$$

So,

$$b = \frac{v_f}{v_{out}} = \frac{R_1 || r_i}{R_1 || r_i + R_2} \approx \frac{R_1}{R_1 + R_2}$$

$$a = \frac{v_{out}}{v_D} = a_D \cdot \frac{R_2 + R_1 || r_i}{R_2 + R_1 || r_i + r_o} \approx a_D$$

In practice, for identifying  $a$  and  $b$  is better to think directly in terms of loop gain  $L$

$$L = ab = -\frac{v_r}{v_t}$$

The minus sign is due to the  $-$  at the summing node

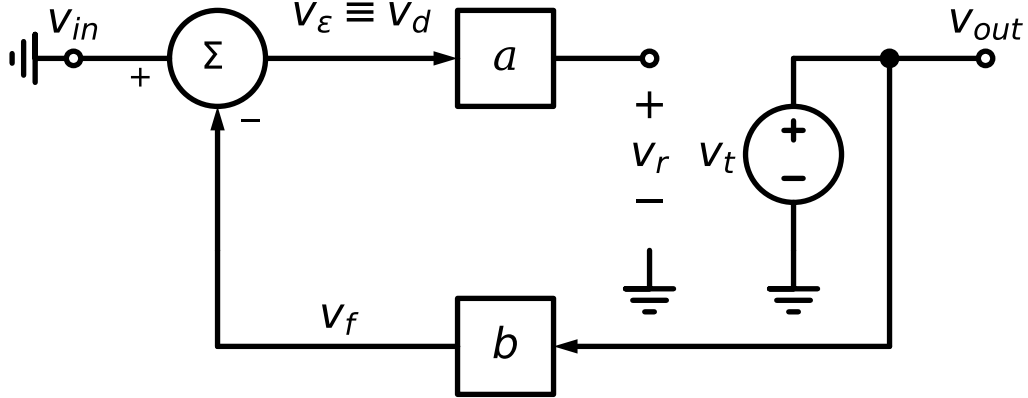


Figure 17: Breaking the Loop.

Note: To find the loop gain, it is best to break the loop at the opamp's voltage controlled voltage source. This approach preserves all of the node impedances in the circuit.

$$L = -\frac{v_r}{v_t} = a_D \cdot \frac{R_1 || r_i}{R_1 || r_i + R_2 + r_o}$$

$$A = A_{ideal} \frac{L}{1 + L} \approx A_{ideal} \left(1 - \frac{1}{L}\right)$$

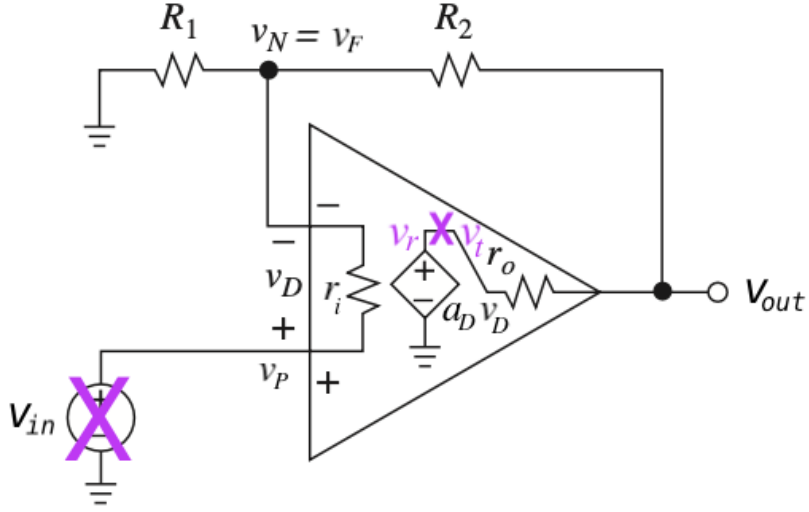


Figure 18: Non inverting op amp amplifier with  $v_{in}$  nulled and the loop broken at the opamp's vcv's.

$$gain_{error} \approx \frac{A_{ideal} \left(1 - \frac{1}{L}\right) - A_{ideal}}{A_{ideal}} = -\frac{1}{L}$$

The value of  $A_{ideal}$  is already known from the ideal op amp analysis

- infinite opamp's gain ( $a_D \rightarrow \infty$ ) implies infinite open-loop gain ( $a \approx a_D$ ) and therefore infinite loop gain  $L = ab$

$$A_{ideal} = \frac{1}{b} \approx 1 + \frac{R_2}{R_1}$$

#### Example 4 - non inverting op amp based voltage amplifier

For  $a_D = 10^6$ ,  $r_i = 10M\Omega$ ,  $r_o = 10\Omega$ ,  $R_1 = 20k\Omega$  and  $R_2 = 80k\Omega$ :

$$L = -\frac{v_r}{v_t} = a_D \cdot \frac{R_1 || r_i}{R_1 || r_i + R_2 + r_o} \approx 10^6 \frac{20k\Omega}{20k\Omega + 80k\Omega}$$

The exact value of  $L$  is 199600, so the above approximation has 0.2% error.

$$A = 5 \cdot \frac{200000}{1 + 200000} = 4.999975$$

$$gain_{error} \approx -\frac{1}{200000} = -5ppm$$

This is the same result as before, except we did not have to go through a tedious nodal analysis and plug in numbers in a “high entropy” expression.

What if the op amp gain changes ?

If the gain is cut in half :

$$A = 5 \cdot \frac{100000}{1 + 100000} = 4.999950$$

If the gain doubles:

$$A = 5 \cdot \frac{400000}{1 + 400000} = 4.999988$$

- The closed loop gain ( $A$ ) is immune to large variations in the op amp gain
- The voltage gain of the overall circuit (= closed loop gain) is primarily defined by the divider ratio of the resistive feedback
  - A quantity that we can control very precisely

## 9.2 Inverting configuration

In this configuration the resistors affects both the input and the feedback path.

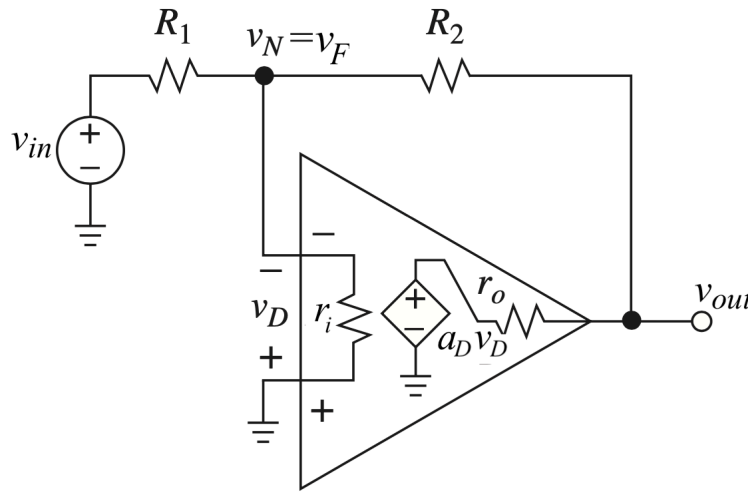


Figure 19: Inverting op amp amplifier. (Franco 2015)}

It is not clear how to map the circuit into the block diagram representation. The flow of the signal through the circuit elements is not unidirectional.

We can still try to make things work using superposition.

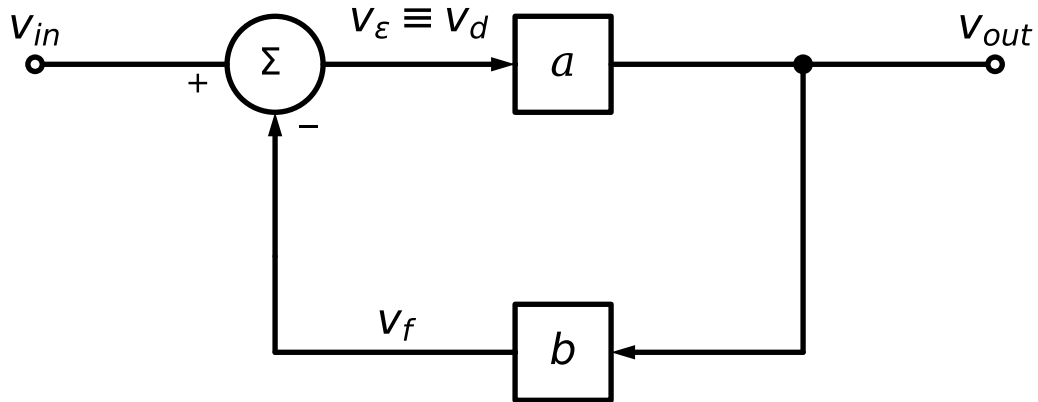


Figure 20: Block diagram of negative feedback system.

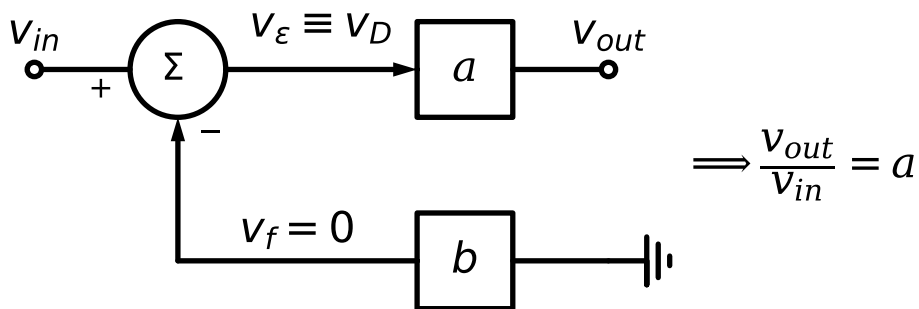


Figure 21: Breaking the loop ( $v_f = 0$ )

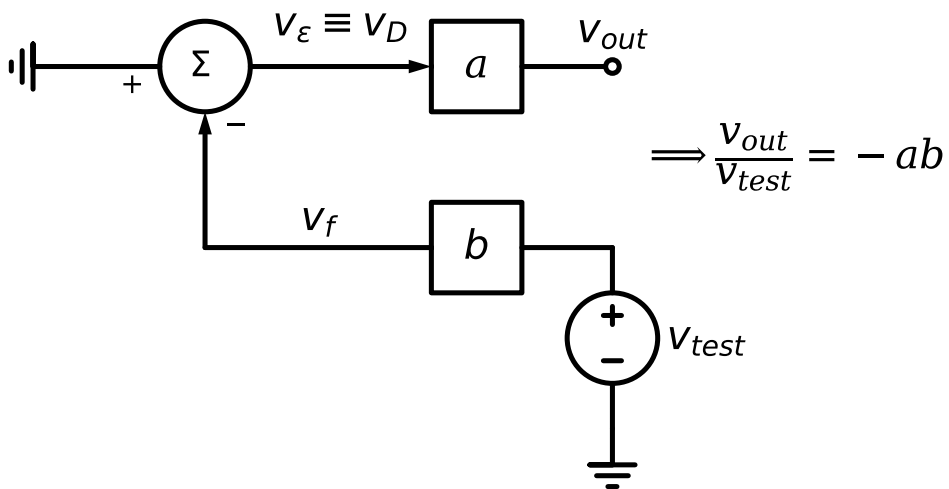


Figure 22: Breaking the loop ( $v_{in} = 0$ )

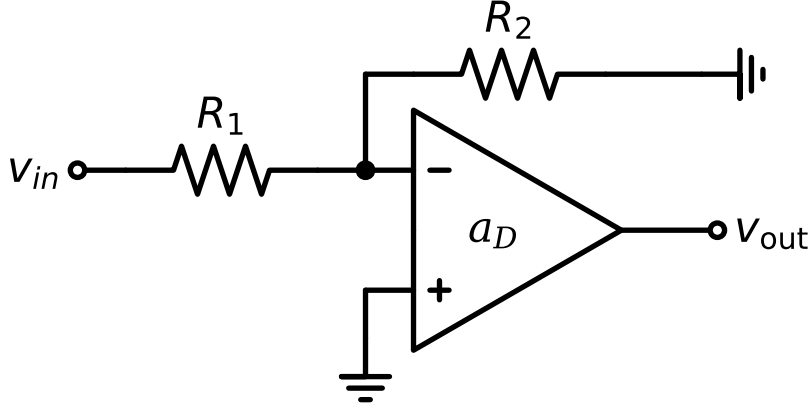


Figure 23: op amp based inverting amplifier with break in the loop ( $v_f = 0$ )

$$a = \frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1 + R_2} \cdot a_D$$

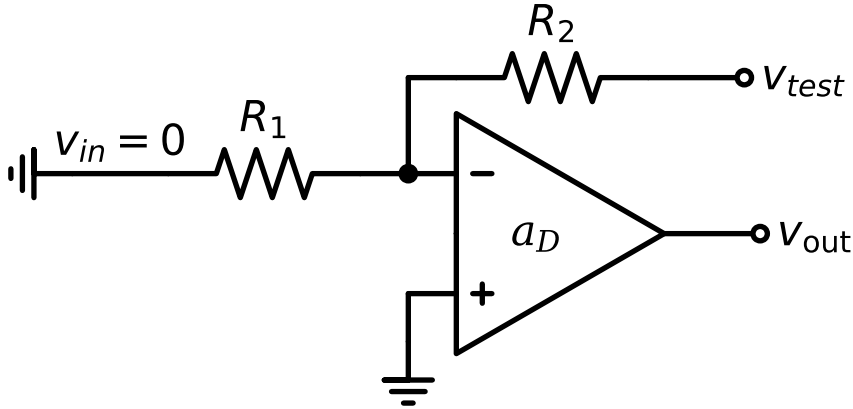


Figure 24: op amp based inverting amplifier with break in the loop ( $v_{in} = 0$ )

$$-ab = \frac{v_{out}}{v_{test}} = -\frac{R_1}{R_1 + R_2} \cdot a_D$$

Note: the loop gain is the same as the one of the non-inverting configuration.

$$A_{ideal} = \frac{1}{b} = \frac{a}{ab} = -\frac{R_2}{R_1}$$

Beyond  $A_{ideal}$  the only other value we need to know is the loop gain  $L = ab$  so we can compute the deviation from ideality



### 9.3 Comparison between non-inverting and inverting topology

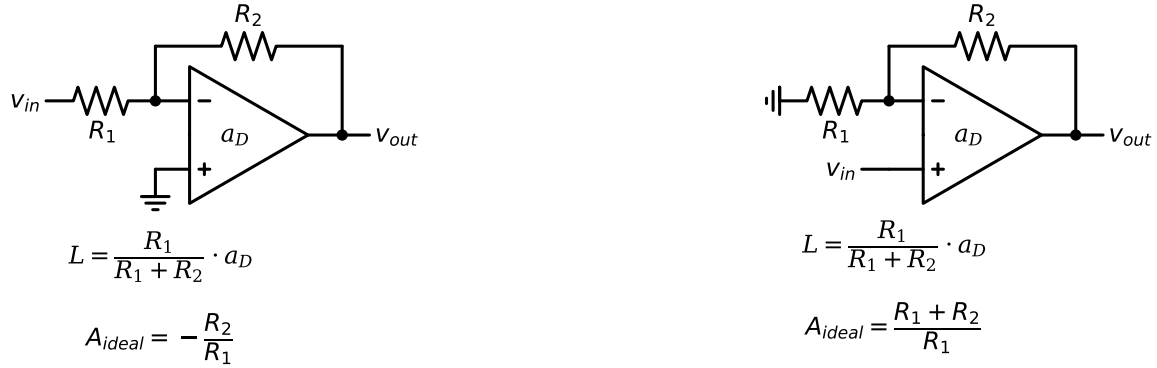


Figure 25: comparison between inverting and non-inverting topology

The following model is valid for both topologies:

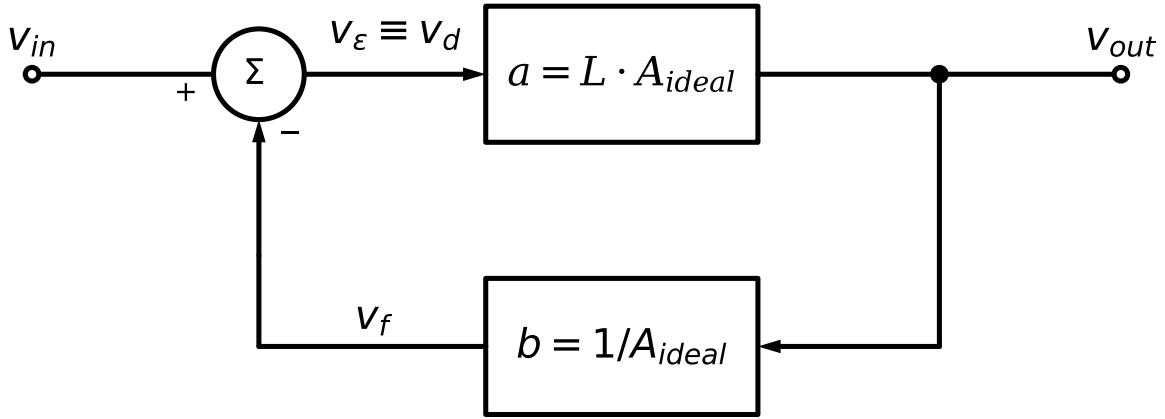


Figure 26: Block diagram model valid for both topologies.

In summary op amp circuits can be analyzed as follows:

- Find  $A_{ideal}$  using nodal analysis, assuming infinite op amp gain
- Find the loop gain to compute the deviation from the ideal case
  - This is usually straight forward, especially when there are ideal breakpoints that do not alter the impedance loading around the loop
  - The best breakpoint for a voltage amplifier is right at the controlled voltage source

$$A = \frac{v_{out}}{v_{in}} = A_{ideal} \cdot \frac{L}{L + 1} = A_{ideal} \cdot \frac{1}{1 + \frac{1}{L}}$$

## 9.4 The four feedback configurations using op amps

Sometimes the operations of output sensing and input returning are not obvious. Even though strictly speaking the op amp is a voltage amplifier, it can be used in any of the four feedback configurations.

### 9.4.1 Series-Shunt (voltage-voltage) configuration (Voltage Amplifier)

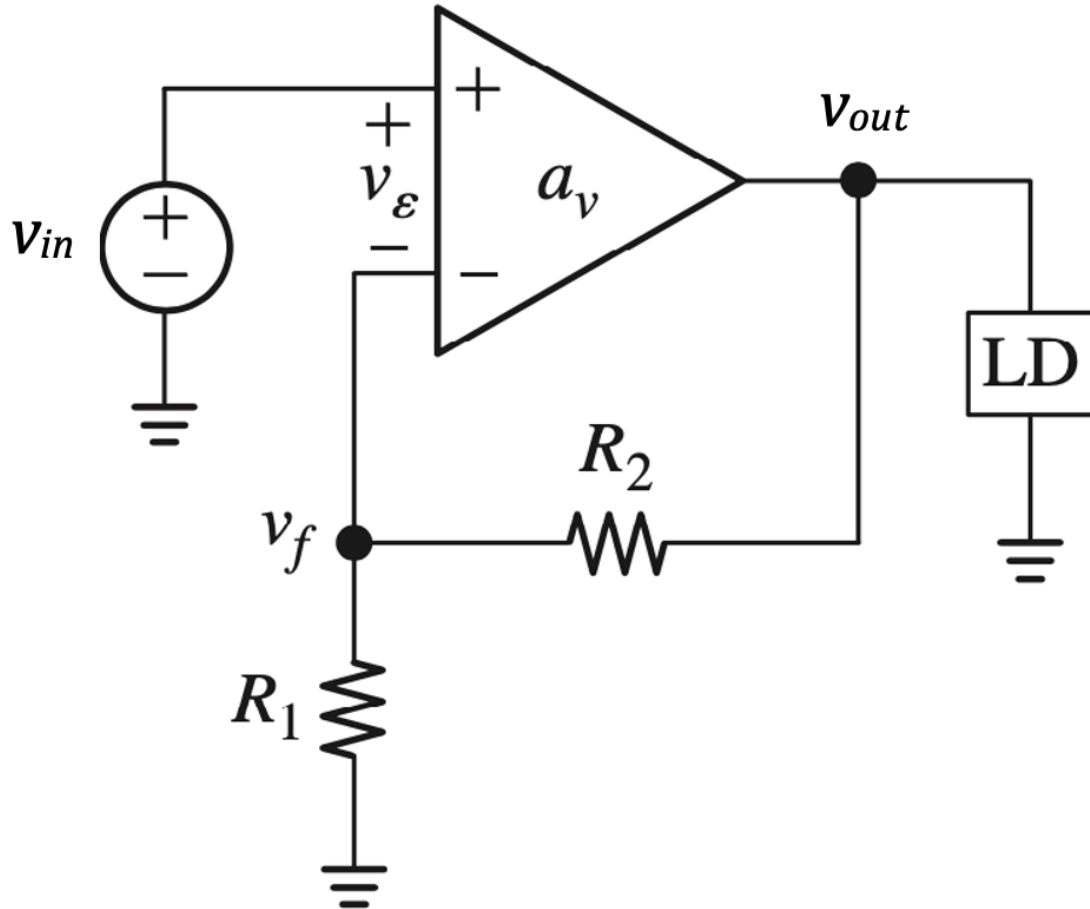


Figure 27: Series-shunt configuration:  $b = \frac{v_f}{v_{out}} = \frac{R_1}{R_1 + R_2}$

For  $a_v \rightarrow \infty$  this circuit gives:

$$A_v = \frac{v_{out}}{v_{in}} = \frac{1}{b} = 1 + \frac{R_2}{R_1}$$

$$R_{in} \rightarrow \infty$$

$$R_{out} \rightarrow 0$$

This circuit is the popular non inverting op amp based voltage amplifier.

#### 9.4.2 Shunt-Shunt (current-voltage) configuration (Transimpedance Amplifier)

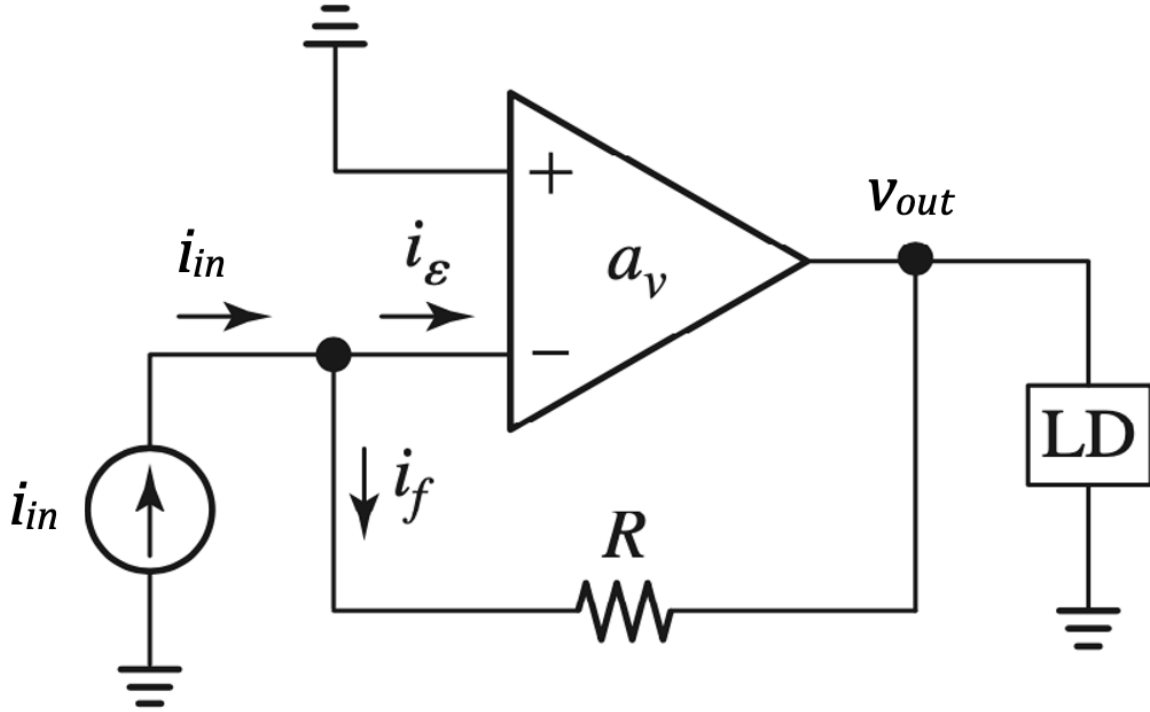


Figure 28: Shunt-shunt configuration:  $b = \frac{i_f}{v_{out}} = -\frac{1}{R}$

For  $a_v \rightarrow \infty$  this circuit (= TIA) gives:

$$R_m = \frac{v_{out}}{i_{in}} = \frac{1}{b} = -R$$

$$R_{in} \rightarrow 0$$

$$R_{out} \rightarrow 0$$

Even though the shunt-shunt configuration is a TIA, it forms the basis of the popular inverting op amp based voltage amplifier.

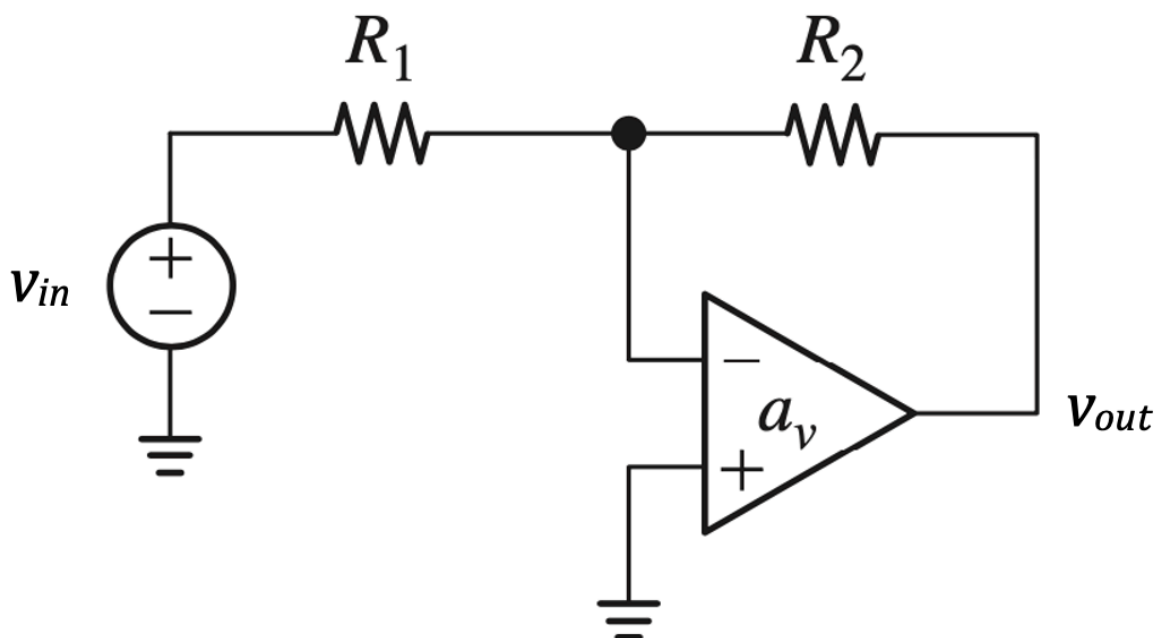


Figure 29: inverting op amp based voltage amplifier

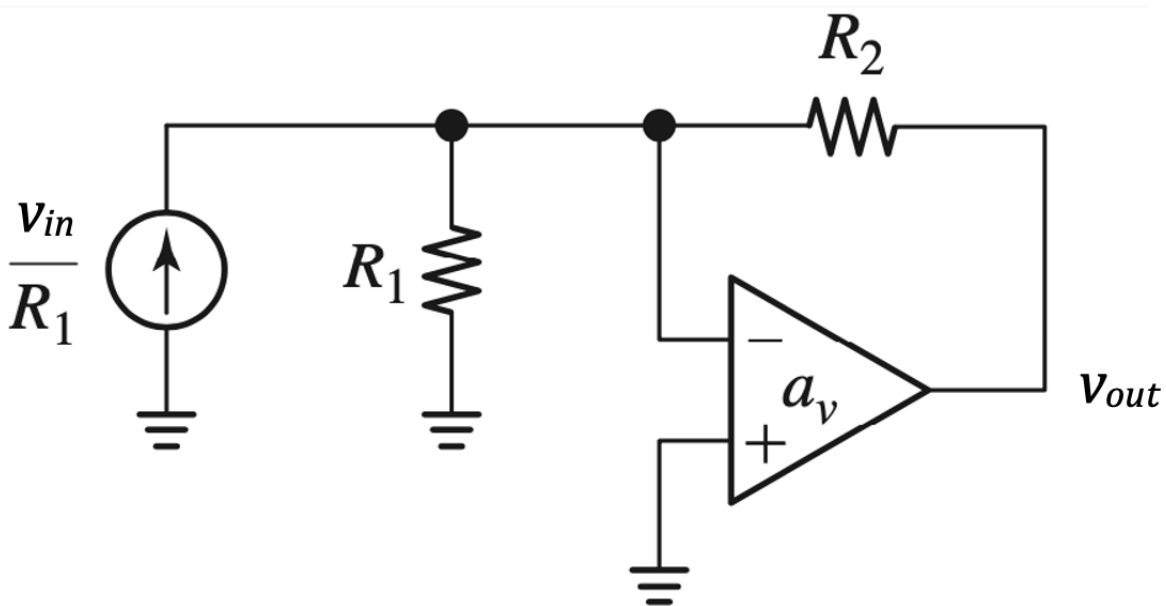


Figure 30: inverting op amp based voltage amplifier with the input voltage source transformed into a current source

This becomes more evident if we perform a source transformation to convert the voltage source  $v_{in}$  in Figure 29 into a current source  $i_{in} = \frac{v_{in}}{R_1}$  as shown in Figure 30.

For the inverting voltage amplifier as  $a_v \rightarrow \infty$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{v_{out}}{i_{in}} \times \frac{i_{in}}{v_{in}} = -\frac{R_2}{R_1}$$

$$R_{in} = R_1$$

$$R_{out} \rightarrow 0$$

### 9.4.3 Series-Series (voltage-current) configuration (Transconductance Amplifier)

For  $a_v \rightarrow \infty$

$$G_m = \frac{i_{out}}{v_{in}} = \frac{1}{b} = \frac{1}{R}$$

$$R_{in} \rightarrow \infty$$

$$R_{out} \rightarrow \infty$$

### 9.4.4 Shunt-Series (current-current) configuration (Current Amplifier)

For  $a_v \rightarrow \infty$

$$A_i = \frac{i_{out}}{i_{in}} = \frac{1}{b} = -(1 + \frac{R_2}{R_1})$$

$$R_{in} \rightarrow 0$$

$$R_{out} \rightarrow \infty$$

## 10 Systematic Feedback Analysis Frameworks

- Two-port Analysis
  - Proposed by Harold Black
  - Helpful for gaining basic intuition about feedback
  - Map the feedback network onto one of 4 topologies
    - \* voltage-voltage (serie-shunt), current-voltage (shunt-shunt), voltage-current (series-series), current-current (shunt-series), depending on the desired input/output quantities

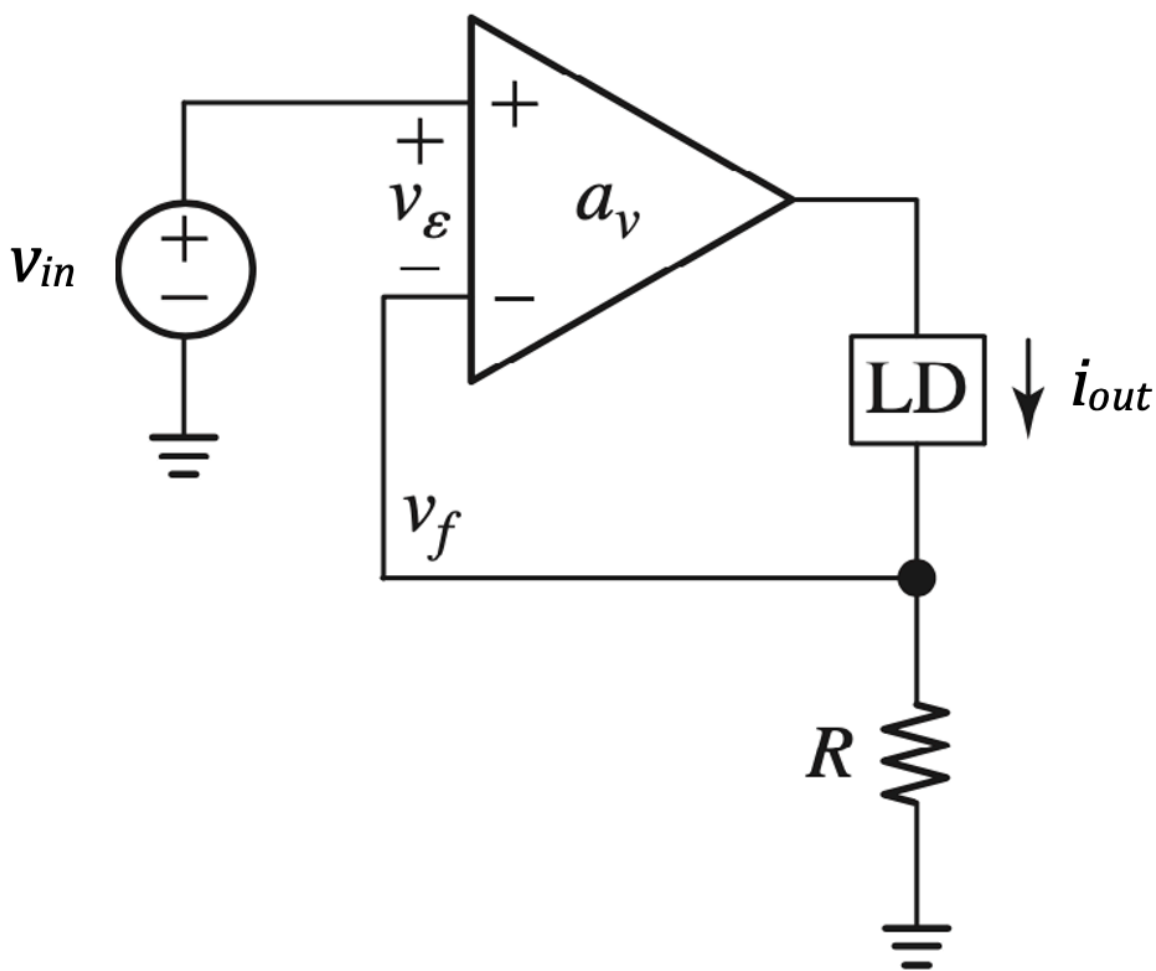


Figure 31: series-series configuration:  $b = \frac{v_f}{i_{out}} = R$

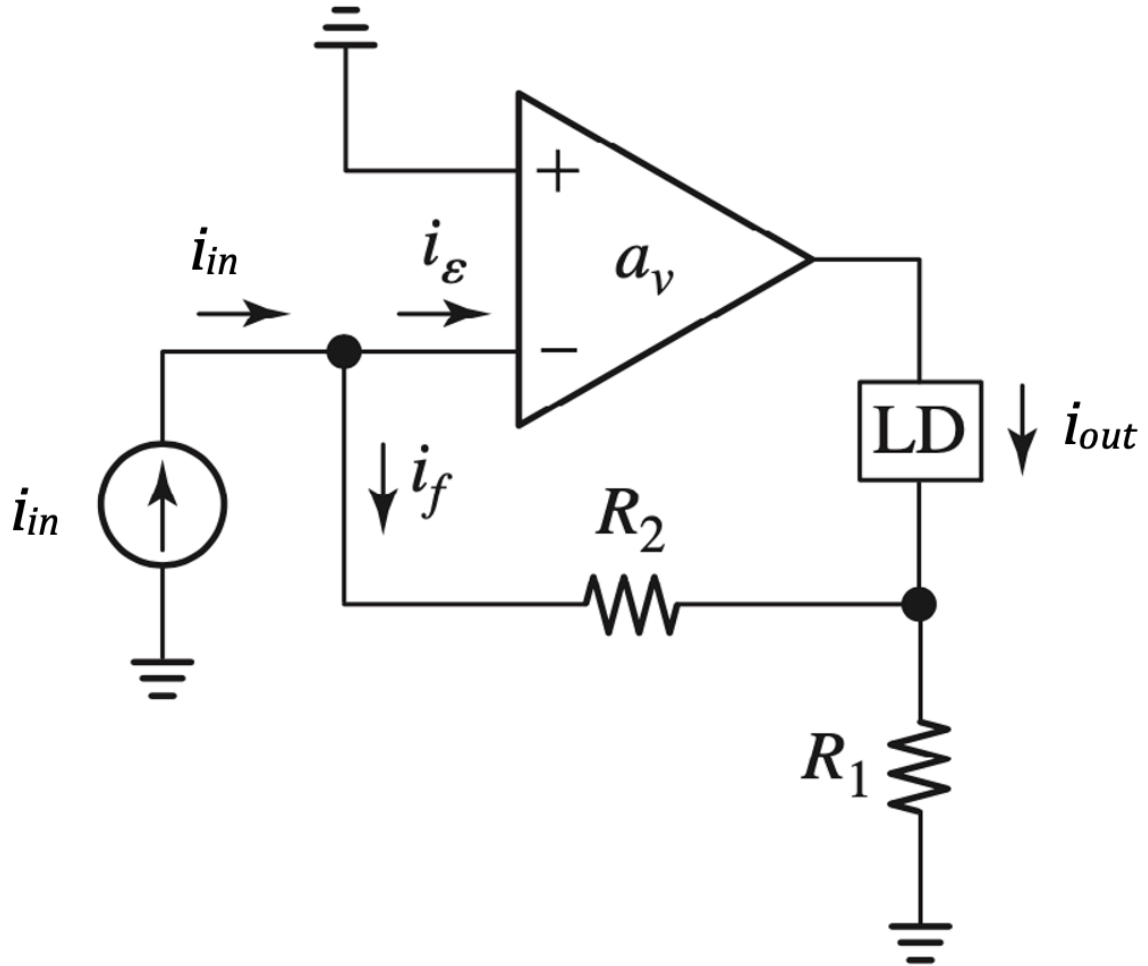


Figure 32: shunt-series configuration:  $b = \frac{i_f}{i_{out}} = -\frac{R_1}{R_1 + R_2} = -\frac{1}{1 + R_2/R_1}$

- In practice, the feedback network “*b*” (and possibly the forward amplifier “*a*”) are not unilateral, so mapping arbitrary circuits into a generic “*ab*” block diagram that uses two-ports is not obvious
- The feedback network causes loading at the input and output of the basic amplifier
  - \* model the feedback network as an ideal two-port and absorb the loading effects into the basic amplifier. This procedure is often quite tedious.
- Some feedback circuits cannot be modeled using two-ports
  - \* e.g. bias circuits with feedback loops tend to have only one port
- Return Ratio Analysis
  - Proposed by Hendrik Bode
  - “Asymptotic” method”, does no attempt to break the circuit into pieces
  - The closed-loop properties of the feedback circuit are described in terms of the *return ratio* of a dependent source in an active device.
  - The block diagram used to analyze the closed loop properties of the feedback circuit is extended to handle the feedforward through the feedback network
  - Often easier than two-port analysis

## 10.1 Return Ratio Analysis

### 10.1.1 Closed-loop gain using return ratio

Given a feedback amplifier, with a controlled source of value  $k$  (see Figure 33), the closed loop gain can be derived as shown in (Gray et al. 2009):

$$A = \frac{s_{out}}{s_{in}} = A_{\infty} \cdot \frac{T}{1 + T} + \frac{d}{1 + T}$$

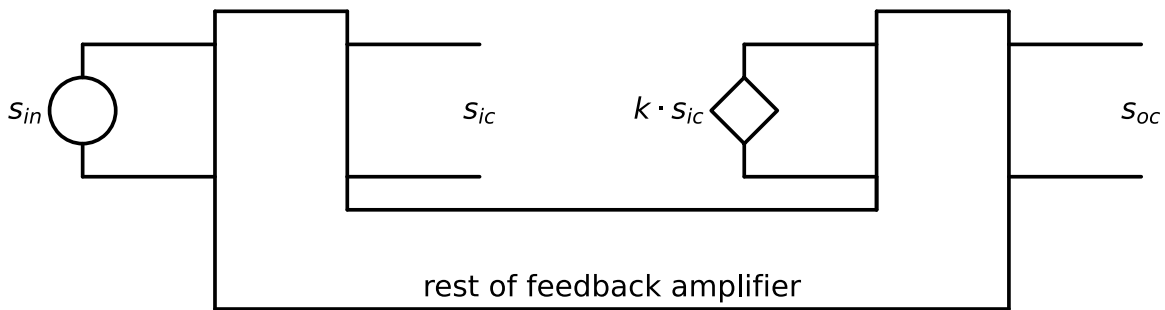


Figure 33: Feedback amplifier: return ratio framework to derive the closed-loop gain



Visually, the expression for the closed loop gain can be summarized through the block diagram in Figure 34:

$$\left(s_{in} - \frac{s_{out}}{A_{\infty}}\right) \cdot TA_{\infty} + d \cdot s_{in} = s_{out}$$

$$A = \frac{s_{out}}{s_{in}} = A_{\infty} \cdot \frac{T}{1+T} + \frac{d}{1+T}$$

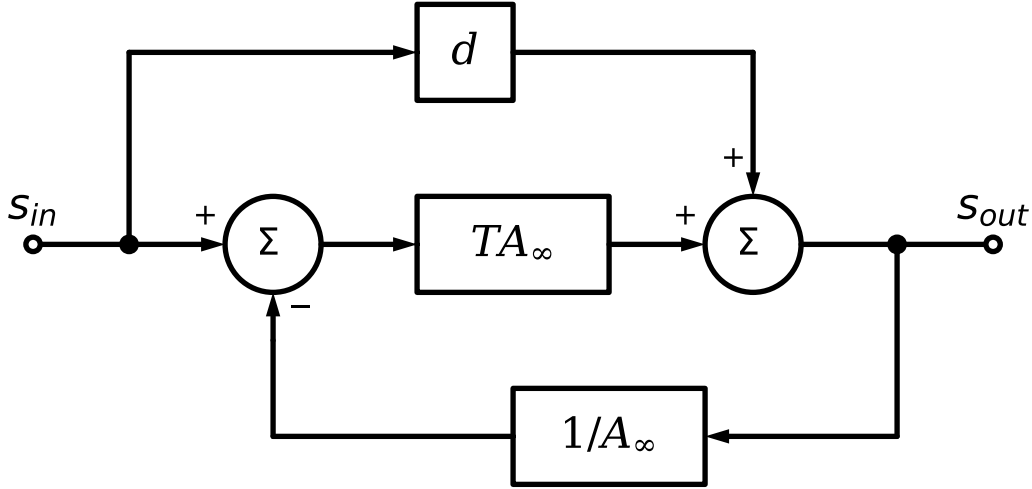


Figure 34: Block diagram for closed-loop gain using return ratio framework

The three terms needed to find the closed loop gain ( $A_{\infty}$ ,  $T$ ,  $d$ ) are all directly computable and measurable (SPICE), and do not rely on any idealization of the feedback network.

In practical circuits the feedback network loads both the input and output of the amplifier, so idealizing its effect is not realistic. With two-port analysis incorporating the effect of loading without the use of suitable approximations/idealizations of the feedback network becomes extremely tedious.

The return ratio analysis does not try to identify the transfer function of the basic amplifier and the feedback network separately. It aims to identify directly the gain around the feedback loop. From the loop gain of a circuit, we can determine:

- stability
- closed loop gain
- nodal impedances

The return ratio analysis can be applied to any arbitrary feedback circuit, independent of topology and port structure.

The return ratio for a dependent source in a feedback loop is found as follows:

1. Set all independent sources to zero
2. identify a dependent source in the feedback loop that you want to analyze and break the loop by disconnecting the dependent source from the rest of the circuit. Leave the dependent source open-circuited if it is of the voltage type, or short-circuited if it is of the current-type
3. On the side of the break that is not connected to the dependent source, inject an independent test source  $s_t$  of the same sign and type as the dependent source
4. Find the return signal  $s_r$ , generated at the controlled source that was disconnected
5. The return ratio  $T$  for the dependent source is  $T = -s_r/s_t$ 
  - Provided that we have chosen a controlled source that breaks the loop globally, the return ratio of the dependent source is equal to the loop gain of the circuit.
  - For the stability analysis of a feedback circuit we must have the loop gain not just any return ratio. Unless, we have a single loop feedback circuit, the return ratios computed for different dependent sources are not necessarily equal (Hurst 1991), so in general, the return ratio is not a global property of the loop. (Hajimiri 2023)

The direct feedthrough  $d$  is given by:

$$d = \left. \frac{s_{out}}{s_{in}} \right|_{k=0}$$

which is the transfer function from input to output evaluated for  $k = 0$ . In other words, the direct feedthrough  $d$  is

the signal transfer from input to output through the passive elements, it represent a signal path from input to output that goes around rather than through the controlled source  $k$ .

The value of  $A_\infty$  is the closed loop gain when the feedback circuit is ideal (that is when  $T \rightarrow \infty$ ). If  $T \rightarrow \infty$  then  $A = A_\infty$ , because  $\frac{T}{1+T} \rightarrow 1$  and  $\frac{d}{1+T} \rightarrow 0$

Since letting  $k \rightarrow \infty$  causes  $T \rightarrow \infty$  (Gray et al. 2009) the value of  $A_\infty$  can be easily found by evaluating

$$\left. \frac{s_{out}}{s_{in}} \right|_{k \rightarrow \infty}$$

When  $k \rightarrow \infty$ , the controlling signal  $s_{ic}$  for the dependent source must be zero for the output of the controlled source to be finite. The controlled source output will be finite if the feedback is negative.

The key difference between the return ratio analysis and the two-port analysis can be seen comparing Figure 34 and Figure 35 In the two-port analysis all forward signal transmission is lumped in the block  $a$ . In the return ratio analysis, there are two forward signal paths: one path ( $d$ ) for the feedback network and another path ( $TA_\infty$ ) for the forward gain.

#### **Example 5 - common source stage with current source biasing**

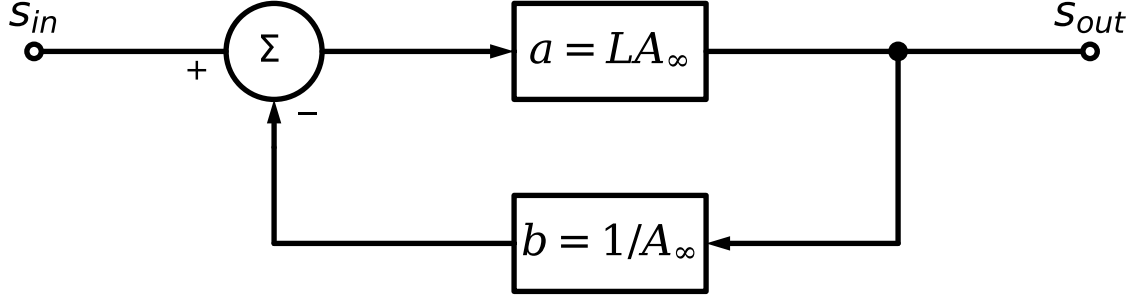


Figure 35: Block diagram model for closed-loop gain using the two-port framework

Consider the circuit in Figure 36 and its AC equivalent model in Figure 37

Current source biasing in this circuit doesn't work without feedback setting the drain voltage. The resistive feedback  $R_2$  constrains the drain and gate voltages to be equal.

Given the finite gain and the nature of the impedances of the MOS, in this circuit is hard to decouple  $a(s)$  and  $b(s)$ , so using the two-ports analysis is not a good option.

$$A(s) = \frac{a(s)}{1 + a(s)b(s)}$$

In this case, since the circuit is not very complex we can use exact nodal analysis.

$$\frac{v_{in} - v_x}{R_1} + \frac{v_{out} - v_x}{R_2} = 0 \Leftrightarrow \frac{v_{in}}{R_1} - \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \cdot v_x + \frac{v_{out}}{R_2} = 0 \quad (3)$$

$$\frac{v_x - v_{out}}{R_2} = g_m v_x \Leftrightarrow v_x = \frac{v_{out}}{1 - g_m R_2} \quad (4)$$

Substituting Equation 3 in Equation 4:

$$\frac{v_{out}}{v_{in}} = \frac{1 - g_m R_2}{1 + g_m R_1} = -\frac{R_2}{R_1} \left( \frac{1 - \frac{1}{g_m R_2}}{1 + \frac{1}{g_m R_1}} \right)$$

If the  $g_m R$  terms are much greater than 1, the result is the same as the op amp solution.

Let's now confirm that return ratio analysis produces the same result.

*Return ratio calculation*

$$v_{gs} = -R_1 i_t$$

$$i_r = g_m v_{gs} = -g_m R_1 i_t$$

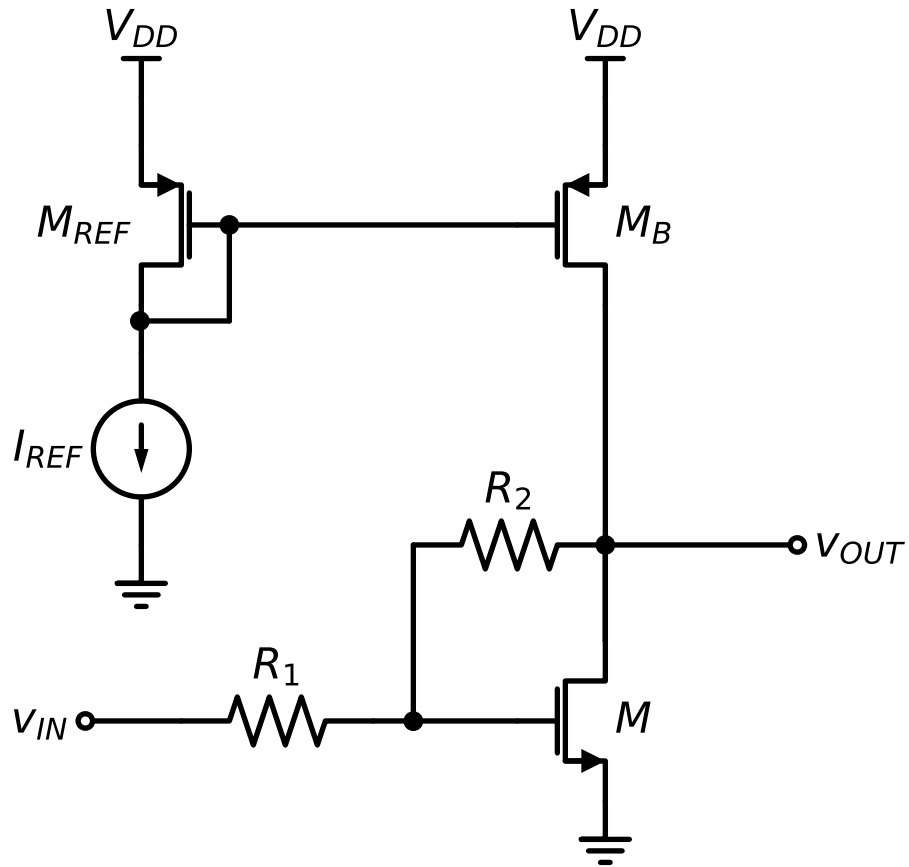


Figure 36: Common source with current-source biasing

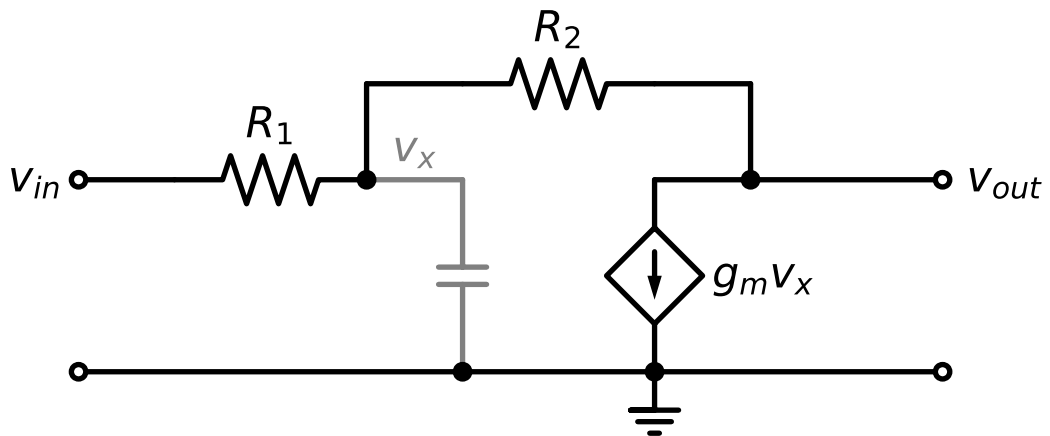


Figure 37: AC equivalent model of the feedback circuit in Figure 36

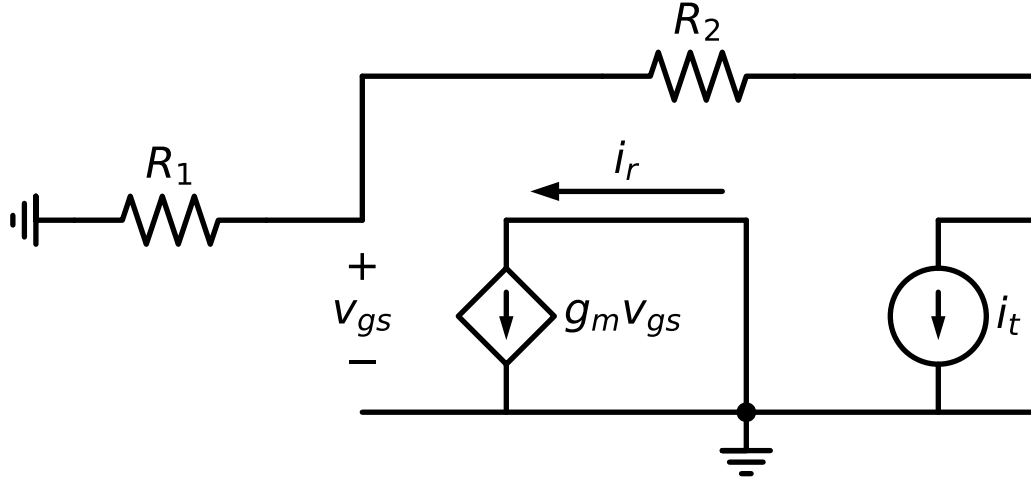


Figure 38: return ratio calculation

$$\frac{i_r}{i_t} = -g_m R_1$$

$$T \equiv -\frac{i_r}{i_t} = g_m R_1$$

*Ideal closed loop gain calculation*

$A_\infty$  is the transfer function when the gain element of the controlled source becomes  $\infty$ . In our case this corresponds to  $g_m \rightarrow \infty$ . If the gain element becomes  $\infty$  the controlling signal must be zero. In our case this corresponds to the input node  $v_{gs} = 0$ , therefore:

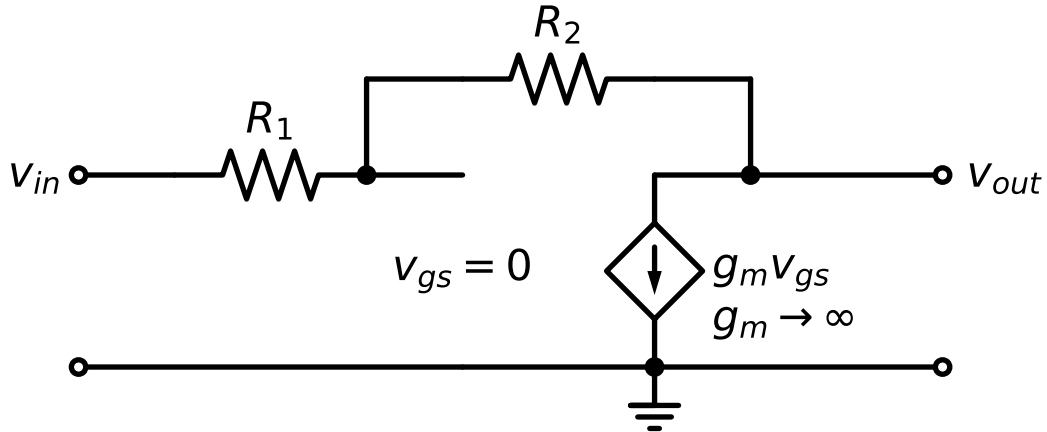


Figure 39: Ideal closed loop gain Calculation

$$\frac{v_{in}}{R_1} = -\frac{v_{out}}{R_2} \Leftrightarrow A_{\infty} = \frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1}$$

Direct feedthrough ( $d$ ) calculation

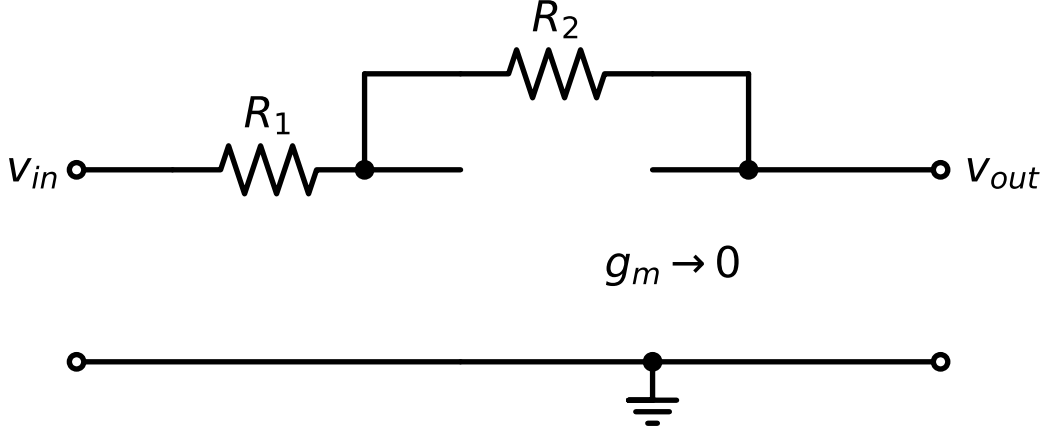


Figure 40: Direct feedthrough Calculation

$d$  is defined as the transfer function when the gain element becomes zero. In our case for  $g_m = 0$

$$v_{out} = v_{in} \Leftrightarrow d = \frac{v_{out}}{v_{in}} = 1$$

In summary:

- $T = g_m R_1$
- $A_{\infty} = -\frac{R_2}{R_1}$
- $d = 1$

Therefore, as expected the closed loop gain computed using the return ratio framework matches with the result obtained using exact nodal analysis:

$$\begin{aligned} A &= A_{\infty} \cdot \frac{T}{1+T} + \frac{d}{1+T} \\ &= -\frac{R_2}{R_1} \cdot \frac{g_m R_1}{1+g_m R_1} + \frac{1}{1+g_m R_1} \\ &= \frac{1 - g_m R_2}{1 + g_m R_1} \end{aligned}$$

**Example 6 - constant- $g_m$  reference**

In this example, we will use the return ratio framework to evaluate the stability of the bias circuit in Figure 41. The bias circuit in Figure 41 is known as constant- $g_m$  reference or  $\Delta V_{GS}$  reference.

Note: this circuit has only one-port so it cannot be analyzed using the two-ports framework.

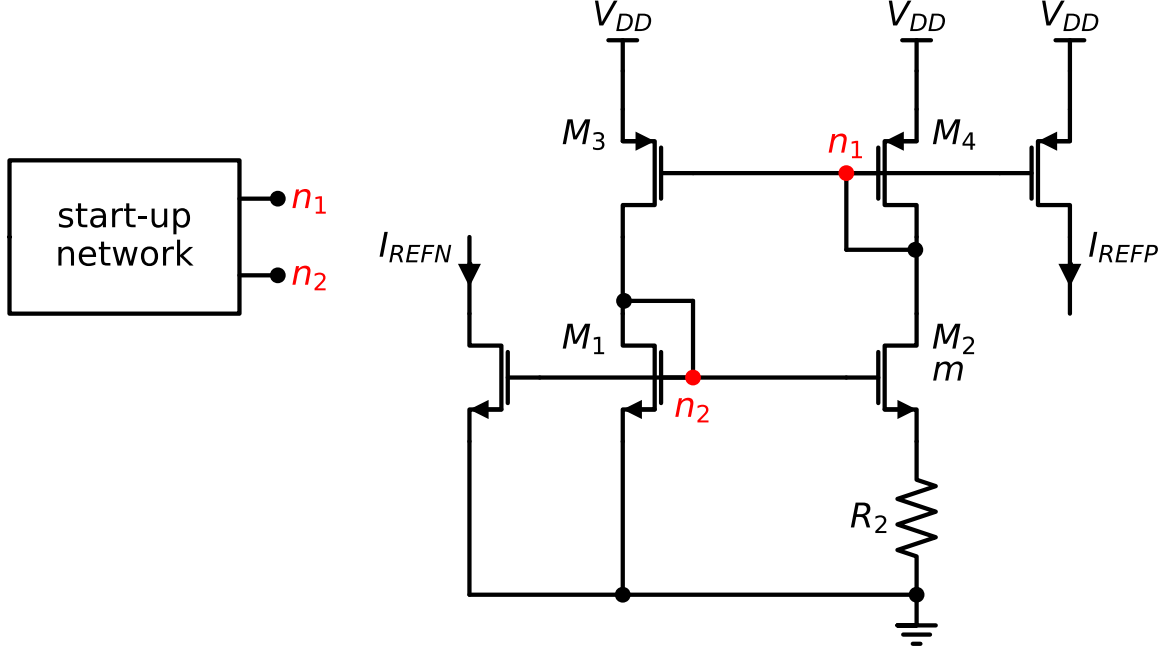


Figure 41: Constant- $g_m$  reference

$$\begin{aligned}
 I_{REF} \cdot R_2 &= V_{GS1} - V_{GS2} = V_{OV1} - V_{OV2} \\
 &\approx V_{OV1} \left( 1 - \frac{1}{\sqrt{m}} \right) \\
 I_{REF} &\approx \frac{V_{OV1} \left( 1 - \frac{1}{\sqrt{m}} \right)}{R_2}
 \end{aligned}$$

- This circuit has positive feedback.
- A positive feedback system is stable only if its loop gain is less than 1 ( $T < 1$ )

To identify which dependent source to use for computing the loop gain  $T$  of the circuit, the feedback loop we break must be global.

- $M_2$  and  $R_2$  degeneration, form a local feedback loop, so  $M_2$  cannot be used to break the main loop

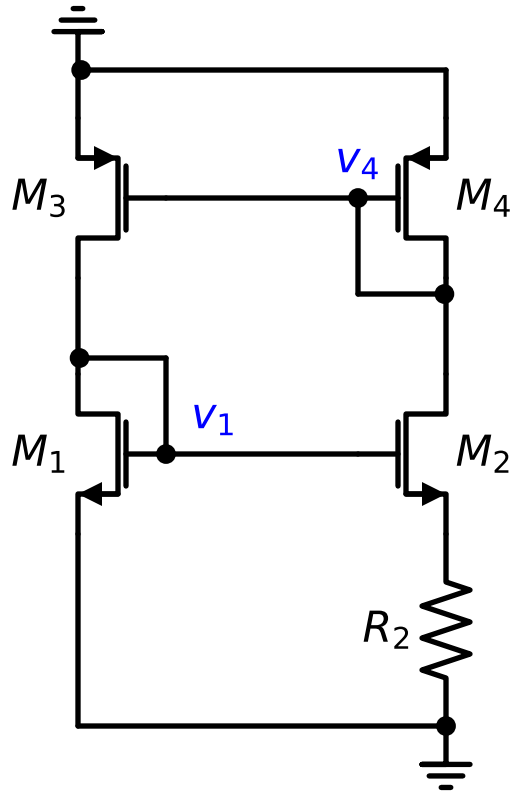


Figure 42: AC equivalent model of the constant- $g_m$  bias circuit



- $M_1$  and  $M_4$  are diode-connected; their transconductance elements are equivalent to a resistance  $1/g_m$ , so cannot be used to break the main loop
- $M_3$  is the only “normal” CS gain stage in the circuit, so it is the only element that can be used to break the main loop

In general, **the return ratio of CG, CD, or degenerated CS cannot be used** to find the “global” loop gain of a circuit.

To compute the loop gain  $T$  of the circuit, it is convenient to first unroll and linearize the AC equivalent model in Figure 42:

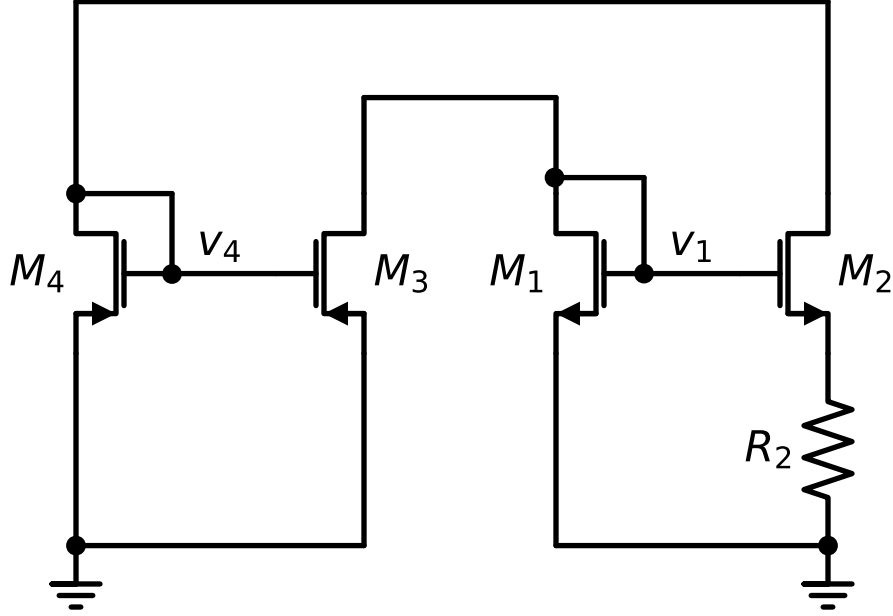


Figure 43: Unrolled AC equivalent model for the constant- $g_m$  bias circuit

and then insert the test source:

$$i_r = g_{m3}v_4$$

$$i_t = -g_{m1}v_1$$

$$v_4 = -i_2 (1/g_{m4})$$

$$i_2 = g_{m2}v_2$$

$$v_1 = v_2 + g_{m2}v_2 R_2 \Leftrightarrow v_2 = \frac{v_1}{(1 + g_{m2}R_2)}$$

Putting the pieces together:

$$\frac{i_r}{i_t} = \left( -\frac{g_{m3}}{g_{m1}} \right) \left( -\frac{g_{m2}}{g_{m4}} \right) \left( \frac{1}{1 + g_{m2}R_2} \right)$$

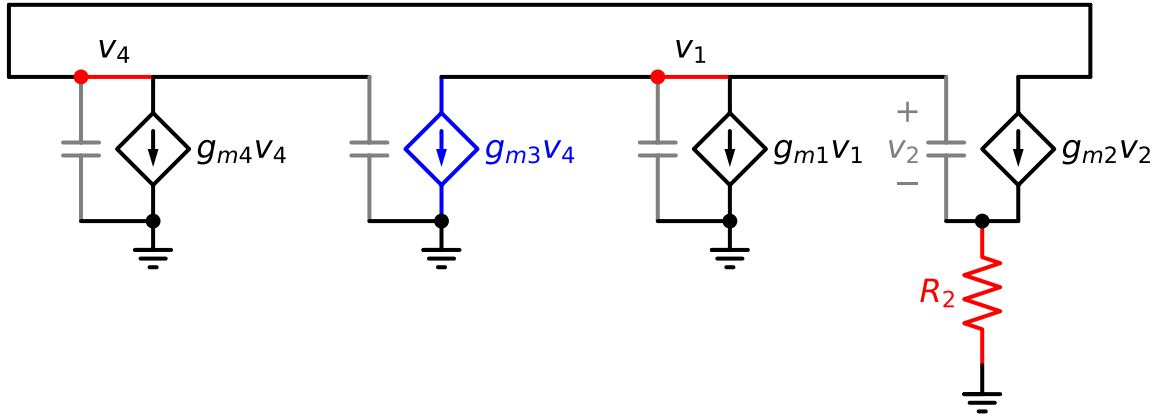


Figure 44: Small signal equivalent model for the constant- $g_m$  bias circuit, (a) red: circuit features that make  $s_t$  insertion not possible, (b) blue: best place for  $s_t$  insertion

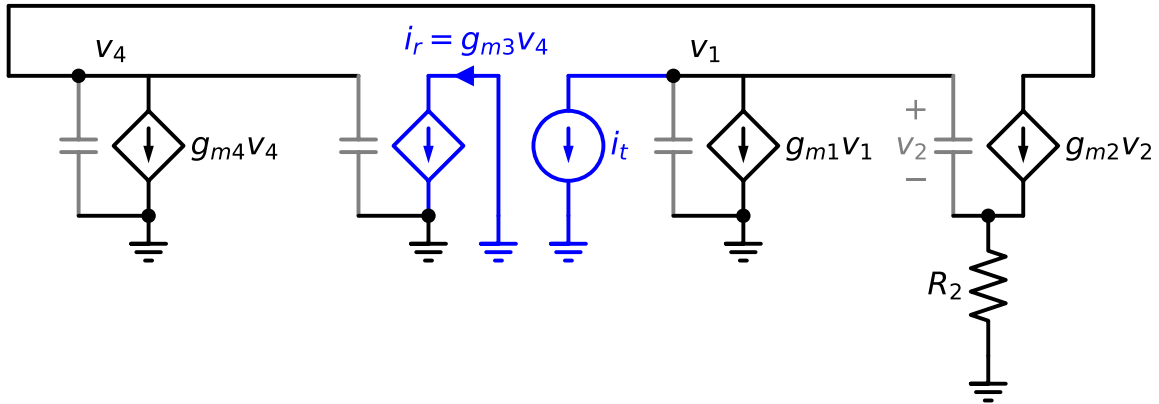


Figure 45: Computing the return ratio for the constant- $g_m$  bias circuit

Therefore:  $T = -\frac{i_r}{i_t} = -\left(\frac{g_{m3}}{g_{m1}}\right)\left(\frac{g_{m2}}{g_{m4}}\right)\left(\frac{1}{1 + g_{m2}R_2}\right)$

The resulting return ratio is negative (i.e. the feedback is definitely not negative, even at zero frequency). The challenge is to keep the magnitude of the return ratio less than unity ( $|T| < 1$ ).

The loop has two inverting gain blocks, each loaded with a “diode connected” MOS device. The gain block formed by  $M_3$  is loaded by the diode connected MOS  $M_1$  and the gain block formed by  $M_2$  and  $R_2$  is loaded by the diode connected MOS  $M_4$ .

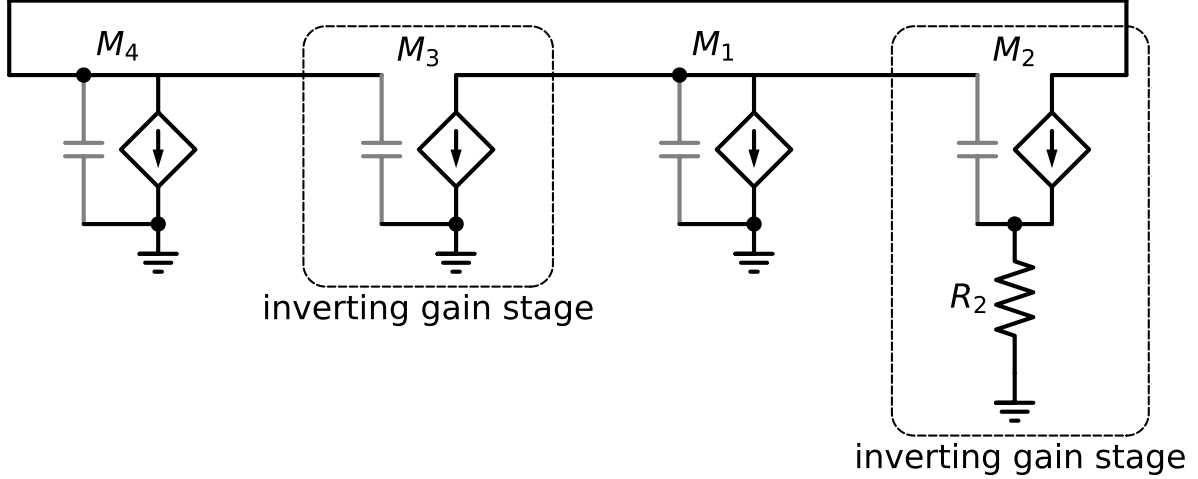


Figure 46: Small signal equivalent model for the constant- $g_m$  bias circuit

### Example 7 - potential stability issue of the constant- $g_m$ reference

Consider the design of the constant- $g_m$  reference circuit in Figure 47:

Assume:  $I(M_3) = I(M_4) = I_{REFN} = 100\mu A$

$V_{OV1} = 200mV$

$m = 2$

For the given circuit:

$$g_{m4} = g_{m3} = g_{m1} = \frac{2 \cdot 100\mu A}{200mV} = 1mS$$

Recalling that:

$$V_{OV2} = \frac{V_{OV1}}{\sqrt{m}}$$

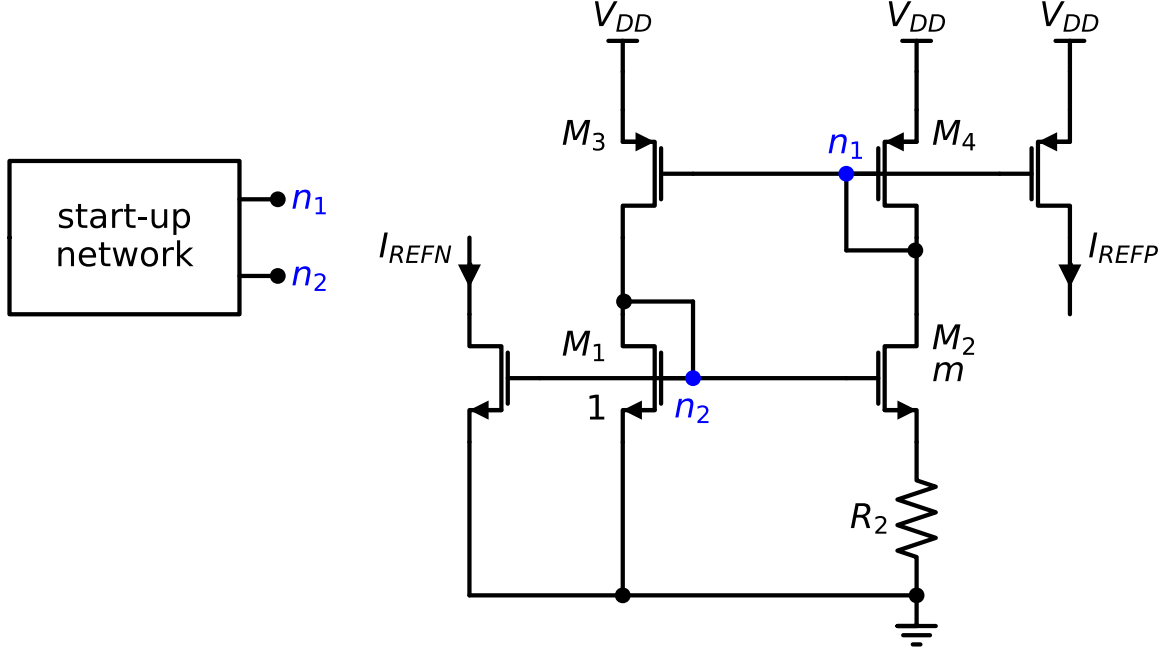


Figure 47: Constant- $g_m$  reference: design example

$$I_{REF} = \frac{V_{OV1} \left(1 - \frac{1}{\sqrt{m}}\right)}{R_2}$$

for  $m=2$ :

$$V_{OV2} = 141mV$$

$$R_2 = 586\Omega$$

$$g_{m2} = \frac{2 \cdot 100\mu A}{141mV} = 1.41mS$$

$$\frac{g_{m2}}{1 + g_{m2}R_2} = 772\mu S$$

The magnitude of the return ratio is less than 1:

$$|T| = \frac{i_r}{i_t} = \left( \frac{g_{m2}}{1 + g_{m2}R_2} \right) \left( \frac{1}{g_{m4}} \right) \left( \frac{\cancel{g_{m3}}}{\cancel{g_{m1}}} \right) = 0.772 (< 1)$$

Therefore, the circuit designed is stable, **but is possible to have problems**. Consider, Figure 48, if the parasitic capacitance  $C$  shorts  $R_2$ , the return ratio becomes larger than 1 and the circuits becomes unstable.

$$\frac{i_r}{i_t} = \left( \frac{1}{1 + g_{m2}R_2} \right)^1 \left( \frac{g_{m2}}{g_{m4}} \right) \left( \frac{g_{m3}}{g_{m1}} \right) \rightarrow 1.41$$

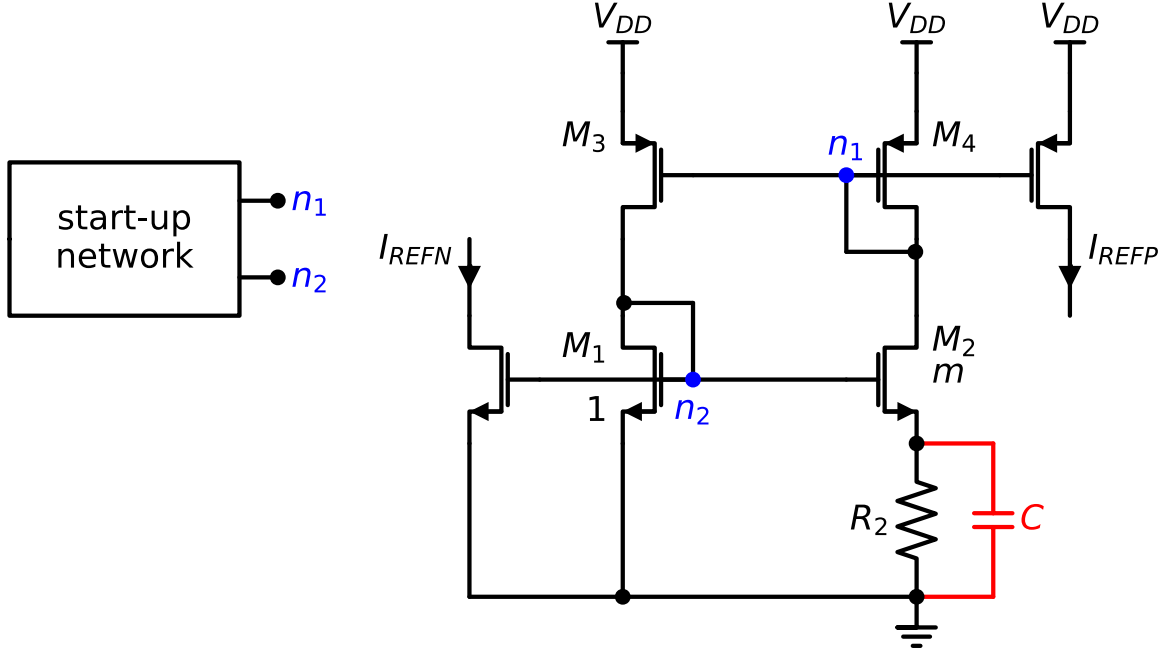


Figure 48: Constant- $g_m$  reference: possible problem

### 10.1.2 Closed-loop impedances using return ratio

Feedback can be used to modify the port impedances of a circuit.

Given a feedback circuit with a controlled source of value  $k$  (see Figure 49), the impedance at any port, including the input and output ports, can be computed (Gray et al. 2009) using the following expression (a.k.a. **Blackman's formula**):

$$Z_{port} = Z_{port}(k = 0) \cdot \left[ \frac{1 + T(portshorted)}{1 + T(portopen)} \right]$$

- $Z_{port}(k = 0)$  is the port impedance with the return ratio's gain element  $k$  set to 0 (either set  $g_m = 0$  or  $a_v = 0$ )
- $T(portshorted)$  is the return ratio with the port under consideration *shorted*
- $T(portopen)$  is the return ratio with the port under consideration *open*

Often, one of the two return ratios in the formula is zero, in these cases feedback increases or decreases the impedance by a factor  $(1 + T)$

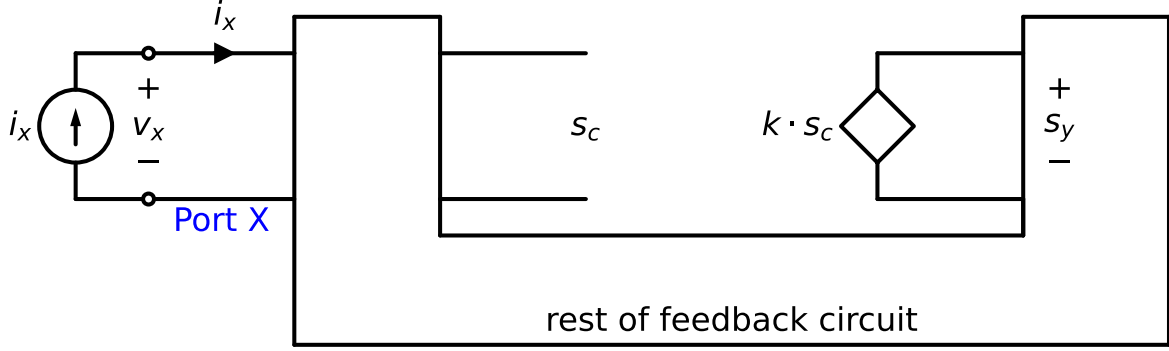


Figure 49: Feedback circuit to derive Blackman's formula with respect to port x

In summary, Blackman's impedance formula:

- it applies to any feedback circuit, regardless of the type of feedback
- it is extremely useful and easy to use
- it is based on return ratio calculations

#### Example 8 - Input resistance of non-inverting op amp configuration

$$R_{in} = R_{in0} \cdot \left[ \frac{1 + T(\text{portshorted})}{1 + T(\text{portopen})} \right]$$

- To find  $R_{in0}$  set the op amp gain  $a_v$  to zero:

$$R_{in0} = r_i + R_1 || (R_2 + r_o || R_L) \approx r_i$$

- To compute  $T(\text{portshorted})$  short the node  $v_p$  to ground and find the return ratio:

$$T_{sc} = -\frac{v_r}{v_t}|_{sc} = a_v \cdot \frac{R_1}{r_o + R_L || (R_2 + r_i || R_1)} \approx a_v \cdot \frac{R_1}{R_1 + R_2}$$

- To compute  $T(\text{portopen})$  leave the node  $v_p$  floating and find the return ratio:

$$T_{open} = -\frac{v_r}{v_t}|_{open} = 0$$

Feedback increases the input impedance of the circuit significantly.

$$R_{in} \approx r_i \cdot \frac{1 + a_v \cdot \frac{R_1}{R_1 + R_2}}{1 + 0} = r_i \cdot \left( 1 + a_v \cdot \frac{R_1}{R_1 + R_2} \right)$$

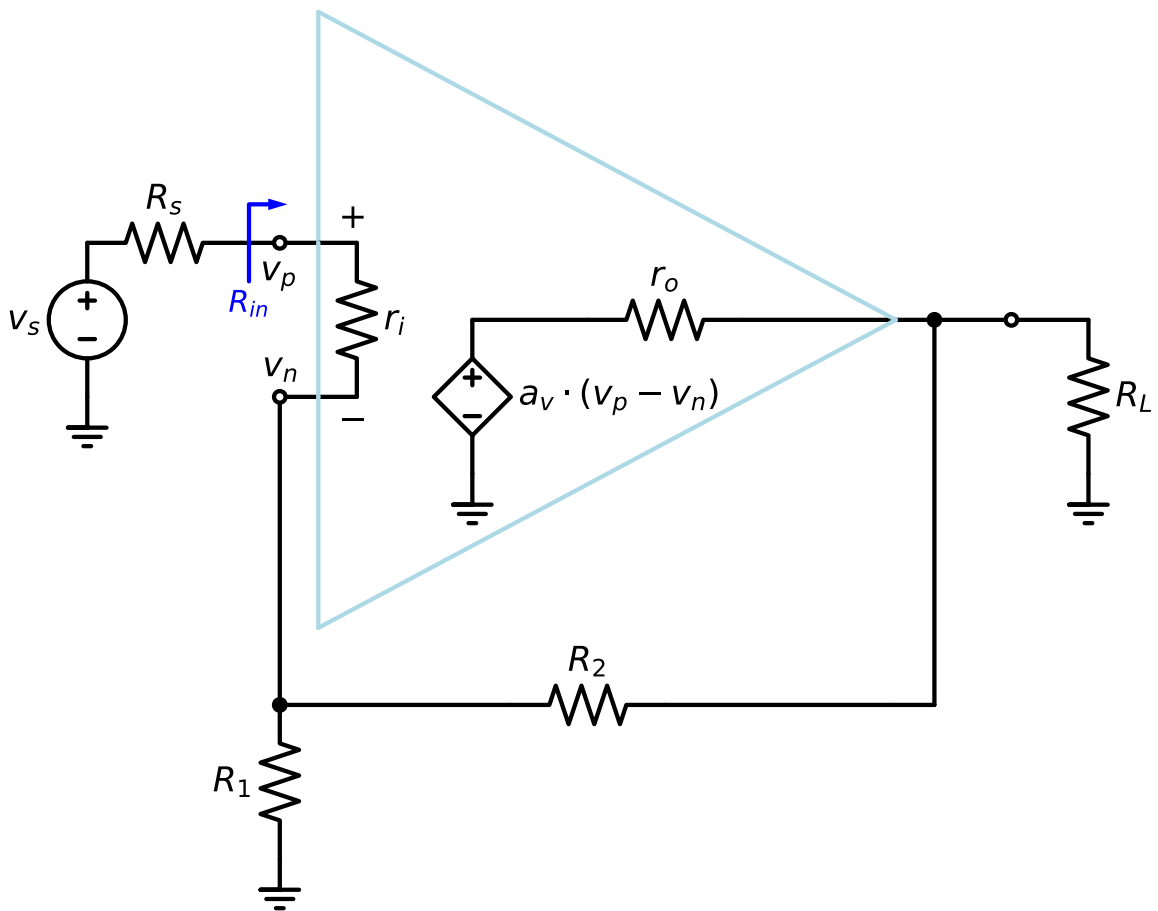


Figure 50: Input resistance of non-inverting op amp circuit

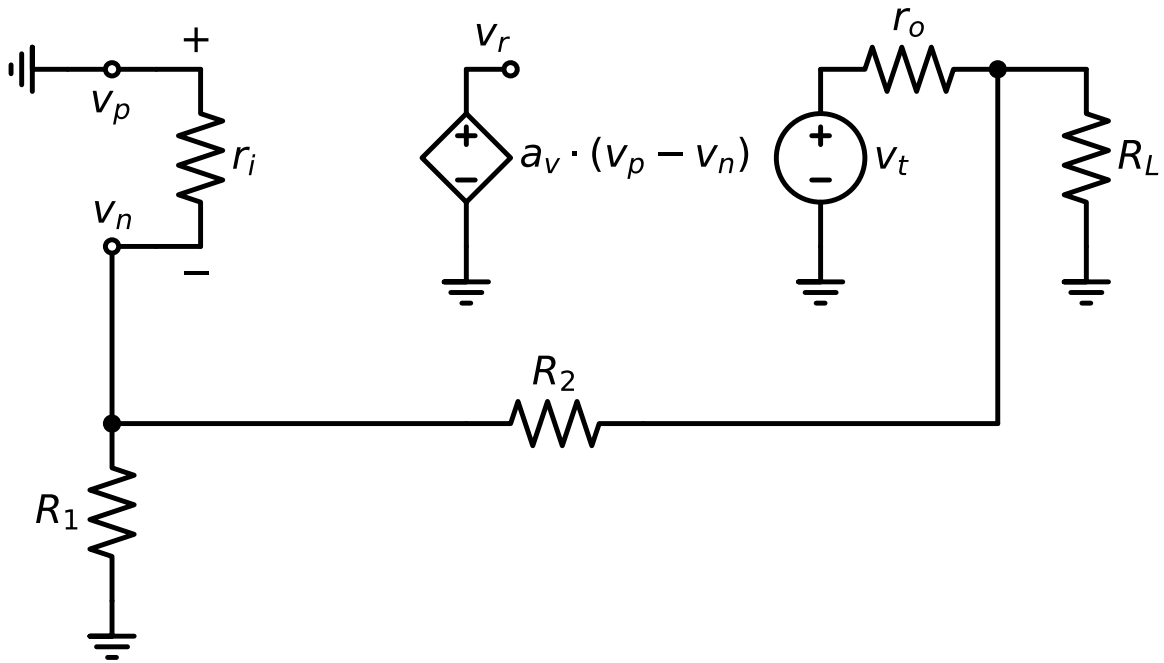


Figure 51: T(with input port shorted) for non inverting configuration

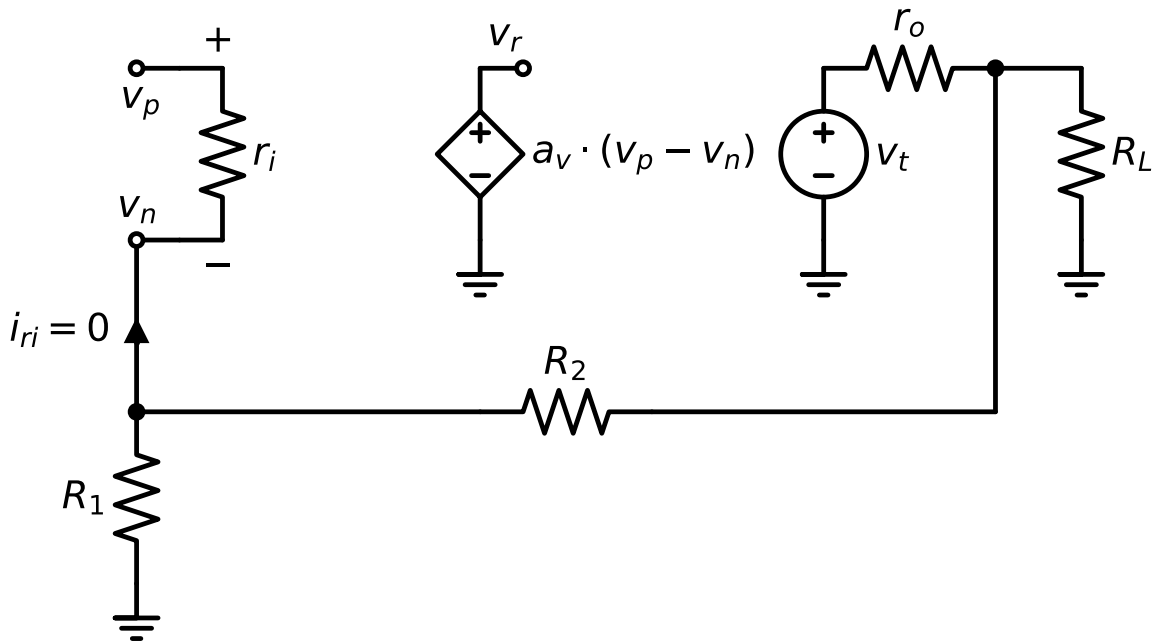


Figure 52: T(with input port open) for non inverting configuration



For  $a_v = 10^6$ ,  $R_1 = 20k\Omega$ ,  $R_2 = 80k\Omega$ :

$$R_{in} \approx r_i \cdot 200000$$

**Example 9 - Output resistance of non-inverting op amp configuration**

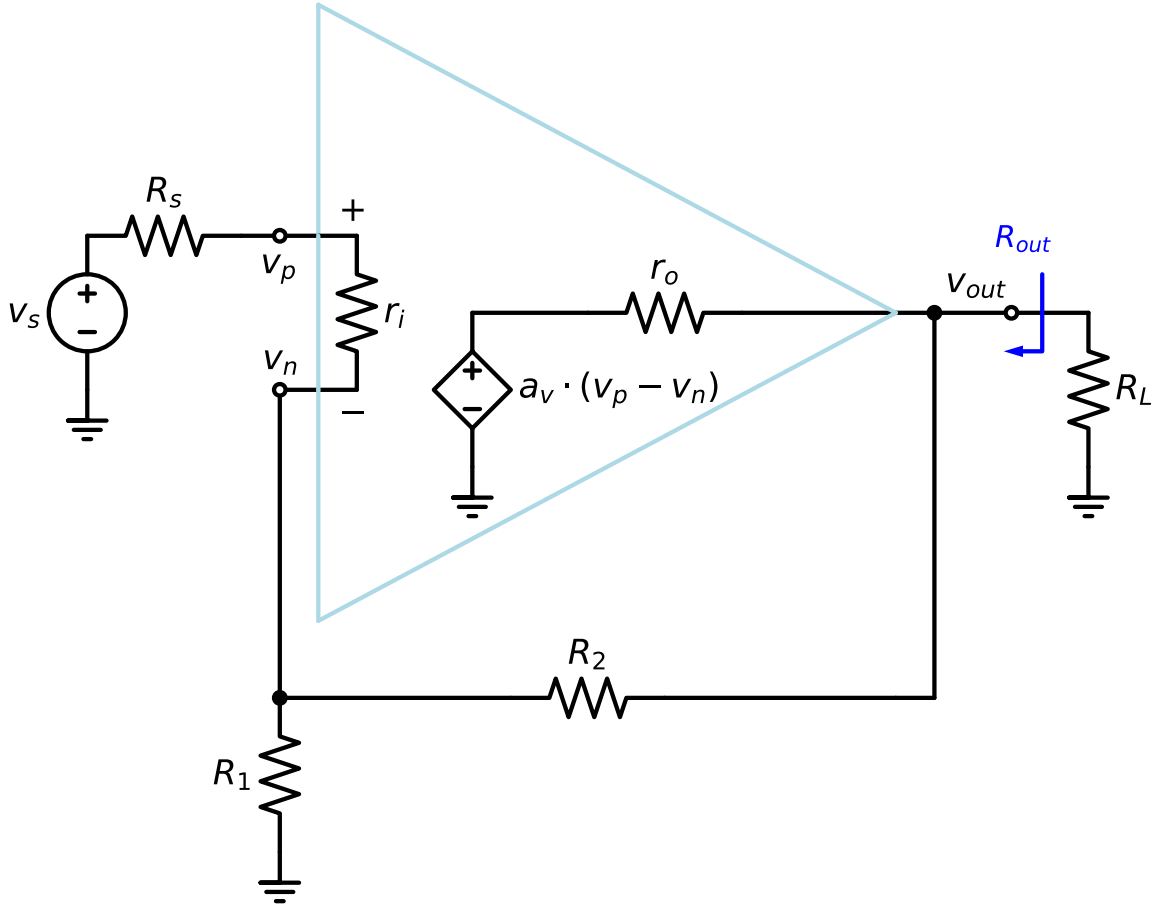


Figure 53: Output resistance of non-inverting op amp circuit

$$R_{out} = R_{out0} \cdot \left[ \frac{1 + T(portshorted)}{1 + T(portopen)} \right]$$

- To find  $R_{out0}$  set the op amp gain  $a_v$  to zero:

$$R_{out0} = r_o || [R_2 + R_1 || (r_i + R_s)] \approx r_o$$

- To compute  $T(portshorted)$  short the node  $v_{out}$  to ground and find the return ratio:

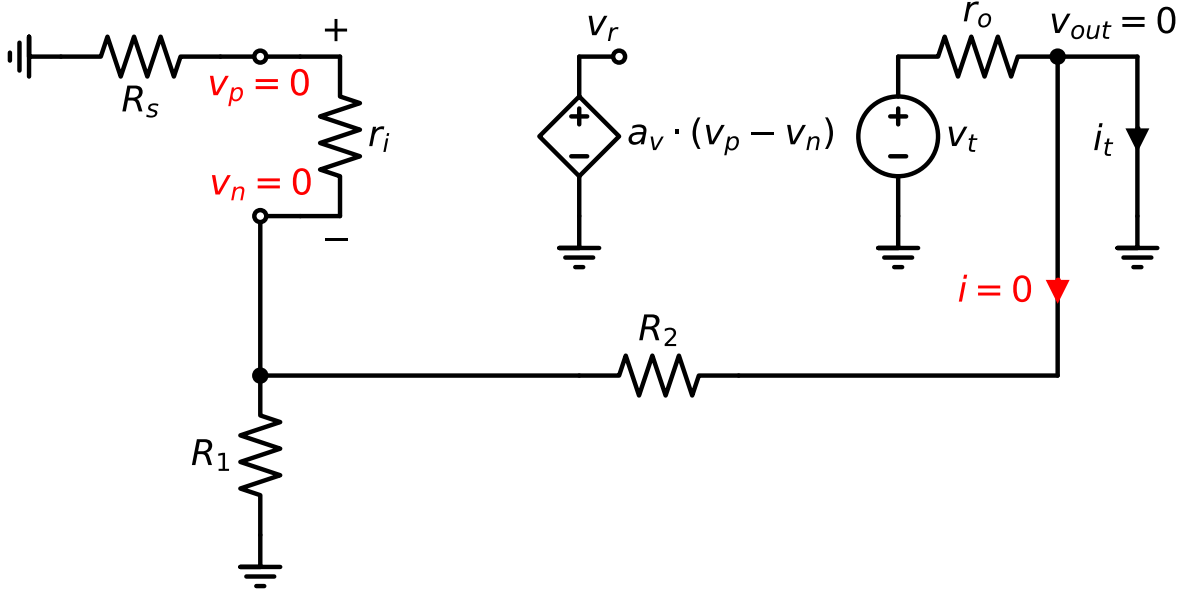


Figure 54: T(with output port shorted) for non-inverting configuration

$$T_{sc} = -\frac{v_r}{v_t}|_{sc} = 0$$

- To compute  $T(portopen)$  leave the node  $v_{out}$  floating and find the return ratio:

$$v_n = \frac{v_t}{r_o + R_2 + [R_1 || (r_i + R_s)]} \cdot R_1 || (r_i + R_s) \approx \frac{v_t}{R_2 + R_1} \cdot R_1$$

$$v_p = v_n \frac{R_s}{r_i + R_s} \approx 0$$

$$T_{open} = -\frac{v_r}{v_t}|_{open} = -\frac{a_v(v_p - v_n)}{v_t} \approx a_v \cdot \frac{R_1}{R_1 + R_2}$$

Feedback decreases the output impedance of the circuit significantly.

$$R_{out} \approx r_o \cdot \frac{1 + 0}{1 + a_v \frac{R_1}{R_1 + R_2}} = \frac{r_o}{1 + a_v \frac{R_1}{R_1 + R_2}}$$

For  $a_v = 10^6$ ,  $R_1 = 20k\Omega$ ,  $R_2 = 80k\Omega$ :

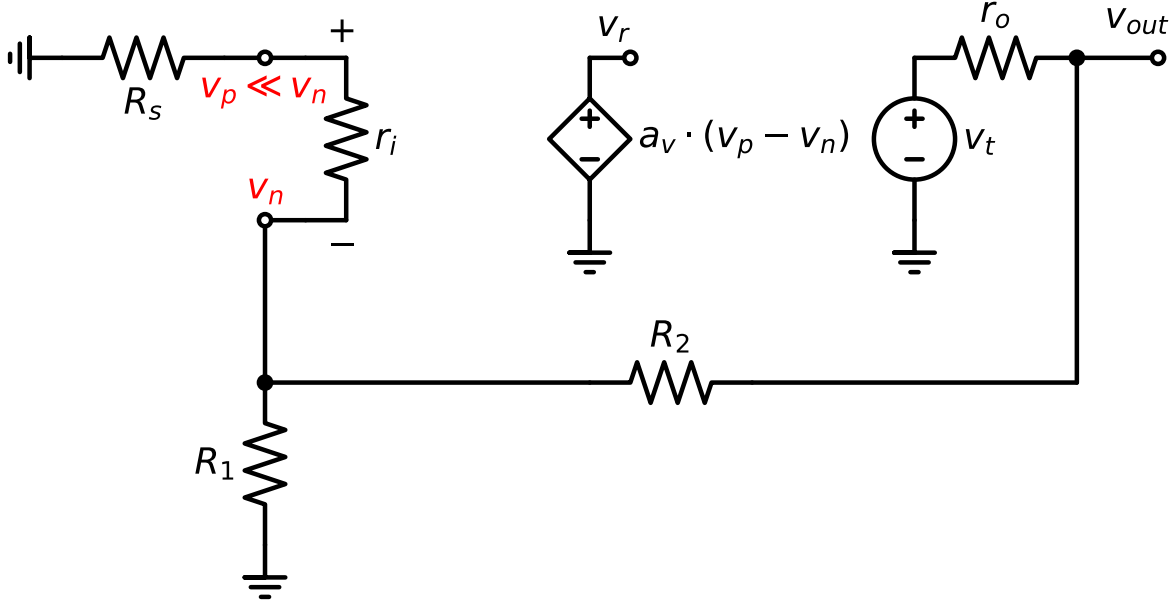


Figure 55: T(with output port open) for non-inverting configuration

$$R_{out} \approx \frac{r_o}{200000}$$

#### Example 10 - Output resistance of bootstrapped source follower

Consider the bootstrapped source follower stage of Figure 56 and its equivalent small signal circuit to compute the return ratio with the output port shorted (Figure 57) and with the output port left floating (Figure 58)

The output resistance for  $k = a_v = 0$  is:

$$R_{out0} \equiv R_{out}(k = 0) \equiv R_{out}(a_v = 0) = \frac{1}{g_m}$$

Output port shorted implies:

$$T_{sc} = -\frac{v_r}{v_t}|_{sc} = 0$$

Output port open means:

$$g_m \cdot v_{gs} = 0 \rightarrow v_{gs} = 0 \rightarrow -v_d = v_t \rightarrow v_r = -a_v \cdot v_t$$

$$T_{open} = -\frac{v_r}{v_t}|_{open} = a_v$$

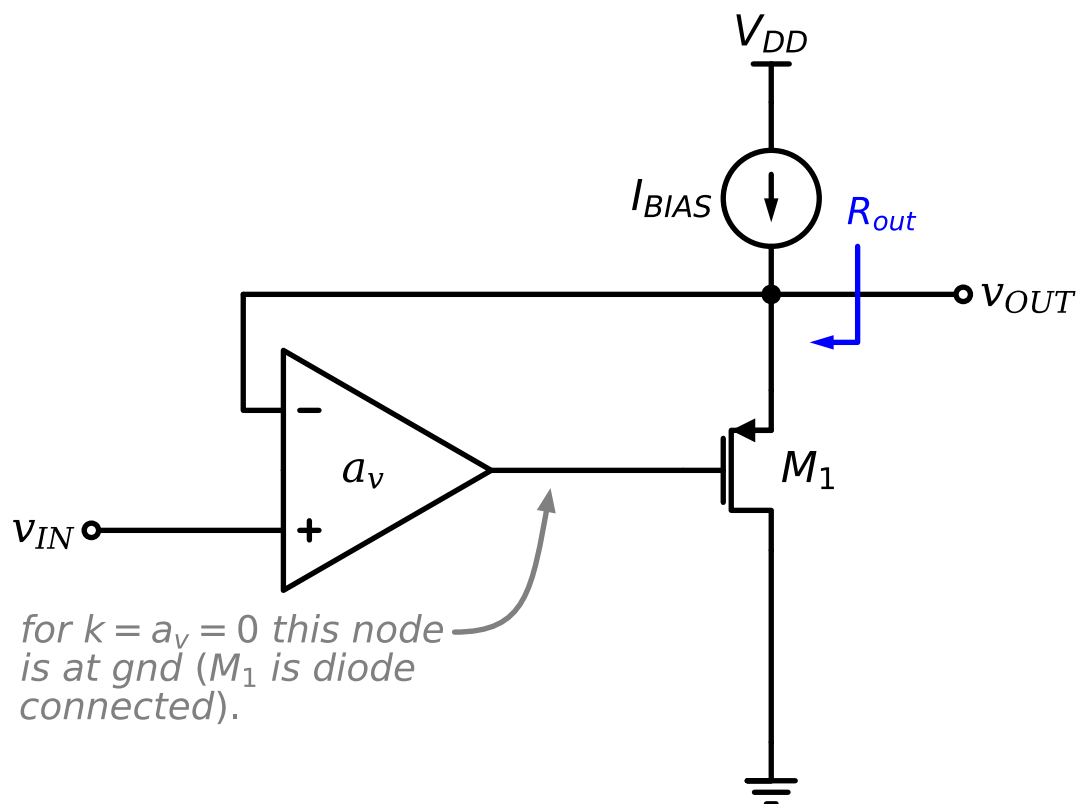


Figure 56: A bootstrapped source follower stage

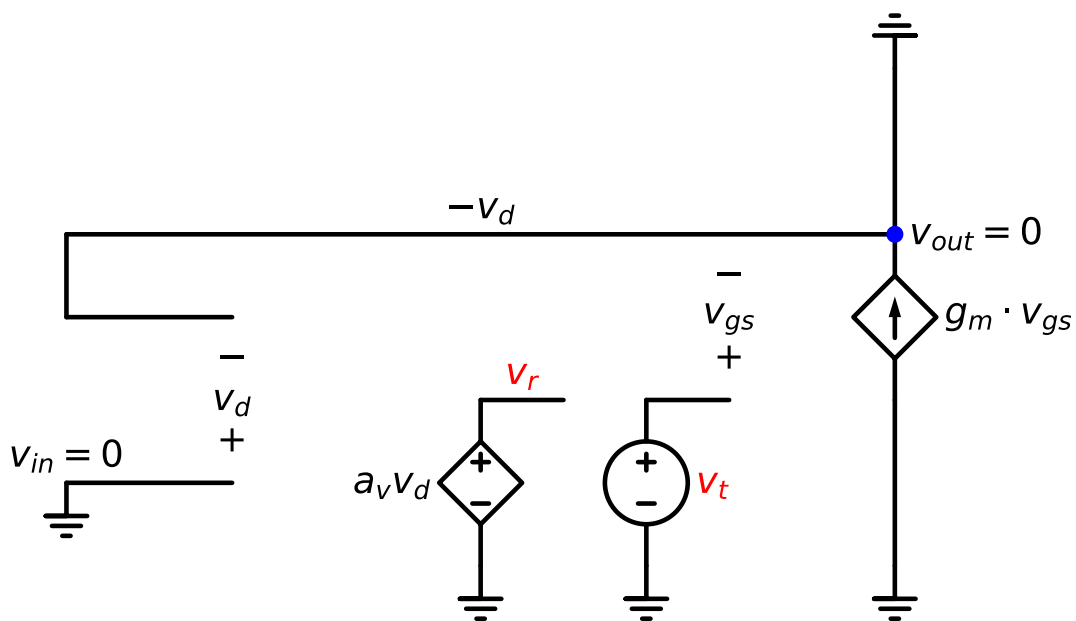


Figure 57: Finding  $T$ (with output port shorted),  $-v_d = v_{out} = 0$

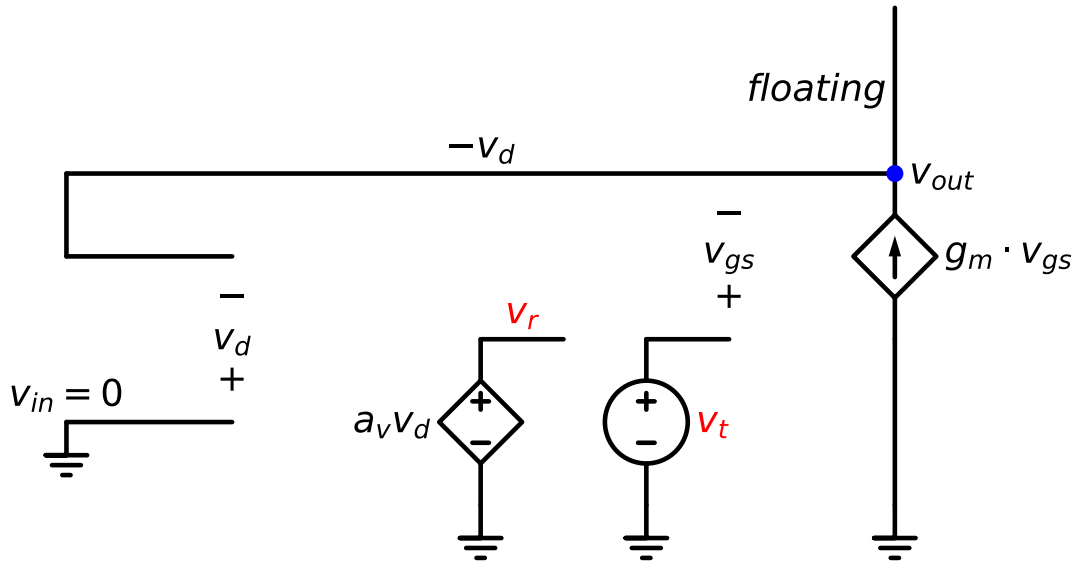


Figure 58: Finding  $T$ (with output port open),  $v_{out} = -v_d = -v_{gs} + v_t$

Therefore, the closed-loop output resistance is:

$$R_{out} = R_{out0} \cdot \frac{1 + T_{sc}}{1 + T_{open}} = \frac{1}{g_m} \cdot \left( \frac{1}{1 + a_v} \right)$$

### Example 11 - Output resistance of super source follower

The super-source follower uses feedback to reduce its output impedance.

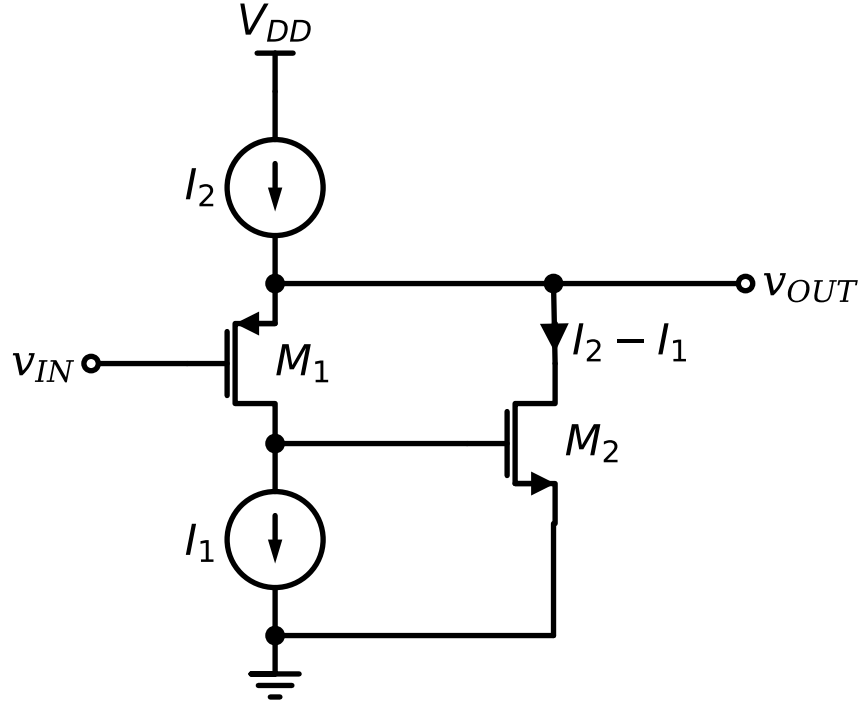


Figure 59: Super-source follower stage

The small signal model of the super-source follower is shown in Figure 60.

- To find  $R_{out0}$  we must set  $v_{in} = 0$  and  $k = 0$ . In this circuit we can use, either  $g_{m1}$  or  $g_{m2}$  as  $k$ . We will use,  $k = g_{m2}$ .

The current in the  $g_{m1}$  generator flows only in  $r_{o1}$ , so  $M_1$  has no effect on the output resistance when  $g_{m2} = 0$

$$R_{out0} \equiv R_{out}(g_{m2} = 0) = r_{o2}$$

- The return ratio for  $g_{m2}$  with the output port shorted is:

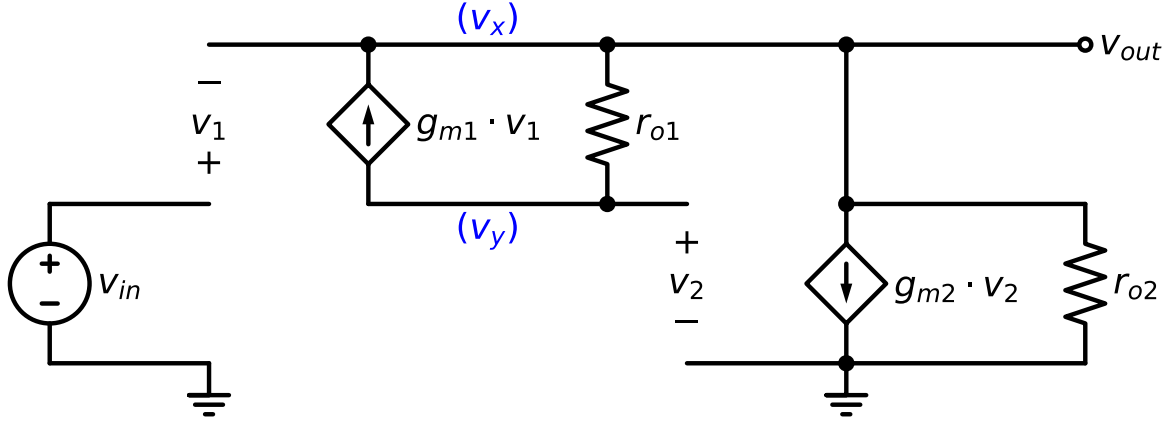


Figure 60: Small-signal model of the super-source follower

$$T_{sc} = -\frac{i_r}{i_t}|_{sc} = 0$$

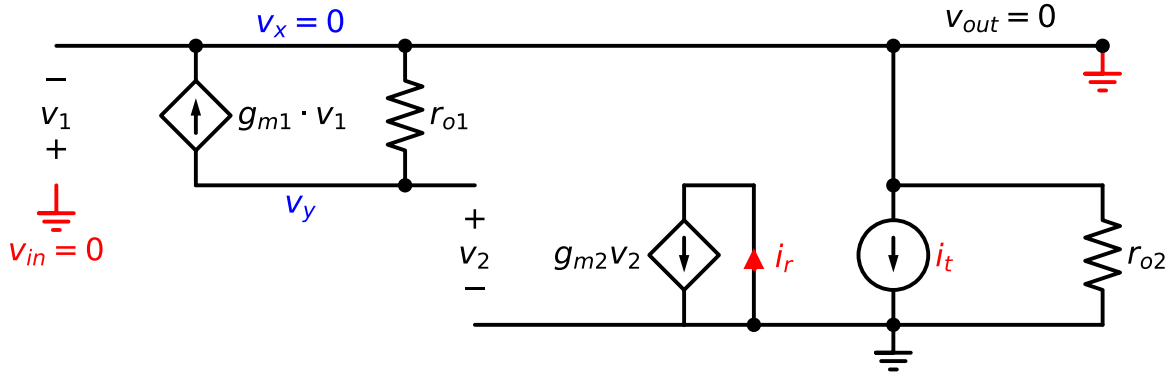


Figure 61: Return Ratio for  $g_{m2}$  with the output port shorted

Shorting the output port forces  $v_{out} = 0$

$$v_{out} \equiv v_x \Leftrightarrow v_x = 0$$

$$v_x = -v_1 \Leftrightarrow v_1 = 0$$

$$g_{m1} \cdot v_1 = 0 \Leftrightarrow v_y = 0$$

$$v_2 = v_x - v_y = 0 \Leftrightarrow g_{m2} v_2 \equiv i_r = 0$$

- The return ratio for  $g_{m2}$  with the output port open is:

$$T_{open} = -\frac{i_r}{i_t}|_{open} = g_{m2}r_{o2}(1 + g_{m1}r_{o1})$$

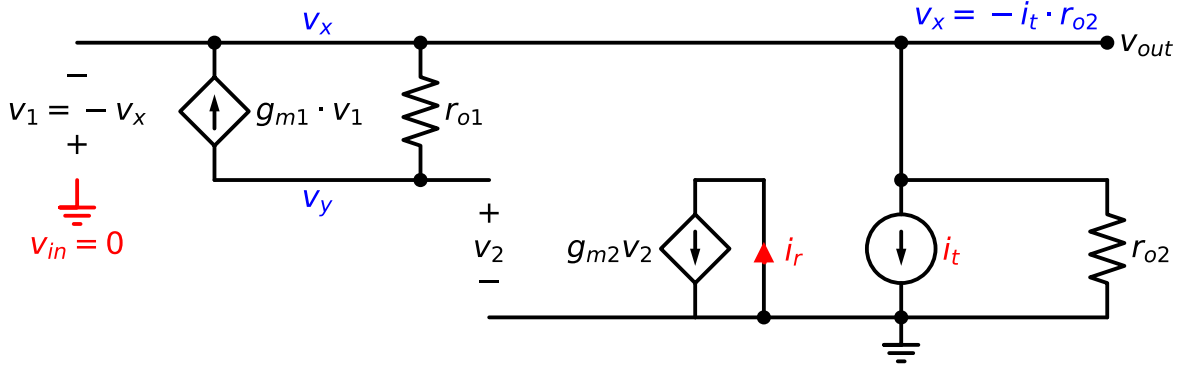


Figure 62: Return Ratio for  $g_{m2}$  with the output port open

Opening the output port gives:

$$v_x = -i_t \cdot r_{o2} \Leftrightarrow i_t = -\frac{v_x}{r_{o2}}$$

$$v_x = -v_1$$

$$v_y - v_x = -g_{m1} \cdot v_1 \cdot r_{o1} \Leftrightarrow v_y = v_x + g_{m1} \cdot r_{o1} \cdot v_x \Leftrightarrow v_y = v_x (1 + g_{m1}r_{o1})$$

$$v_2 = v_y$$

$$i_r \equiv g_{m2}v_2 = g_{m2}(1 + g_{m1} \cdot r_{o1}) \cdot v_x$$

$$T_{open} = -\frac{i_r}{i_t} = g_{m2}r_{o2}(1 + g_{m1}r_{o1})$$

- The closed-loop output resistance is:

$$R_{out} = R_{out0} \cdot \frac{1 + T_{sc}}{1 + T_{open}} = \frac{r_{o2}}{1 + g_{m2}r_{o2}(1 + g_{m1}r_{o1})}$$

Assuming  $g_m r_o \gg 1$

$$R_{out} \approx \frac{1}{g_{m1}g_{m2}r_{o1}}$$

### Example 12 - Input and output resistance of shunt-shunt stage (TIA)

*Closed-loop input resistance*

$$R_{in}(g_m = 0) = R_F + r_o$$



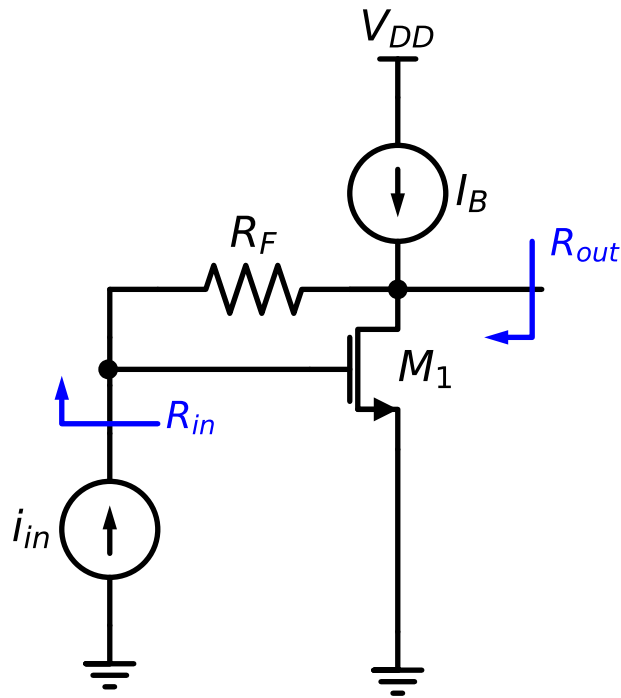


Figure 63: Shunt-shunt stage (Transimpedance Amplifier)

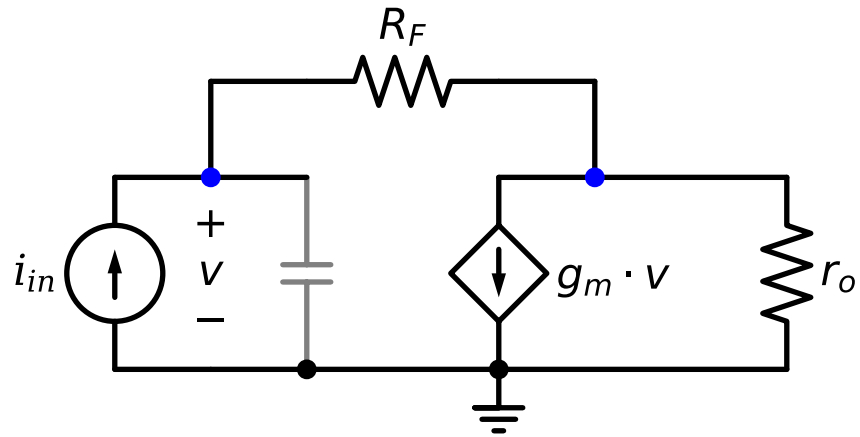


Figure 64: Small signal model of the shunt-shunt stage

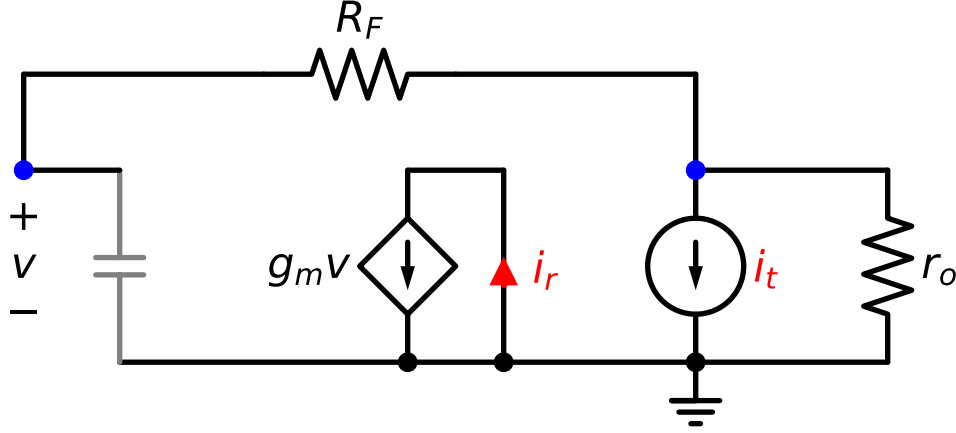


Figure 65: Small signal model to find the return ratio for  $g_m$

$$T(\text{inputshorted}) = 0$$

$$T(\text{inputopen}) = g_m r_o$$

Therefore, the closed-loop input resistance is:

$$R_{in} = (R_F + r_o) \cdot \frac{1}{1 + g_m r_o} \approx \frac{1}{g_m} \left( 1 + \frac{R_F}{r_o} \right)$$

*Closed-loop output resistance*

$$R_{out}(g_m = 0) = r_o$$

$$T(\text{inputshorted}) = 0$$

$$T(\text{inputopen}) = g_m r_o$$

Therefore, the closed-loop output resistance is:

$$R_{out} = r_o \cdot \frac{1}{1 + g_m r_o} \approx \frac{1}{g_m}$$

### Example 13 - Output resistance of active cascode

The “active cascode” circuit is also referred as “regulated cascode” or “gain-boosting” technique.

- To find  $R_{out0}$  we set  $v_{in} = 0$  and  $k = a_v = 0$

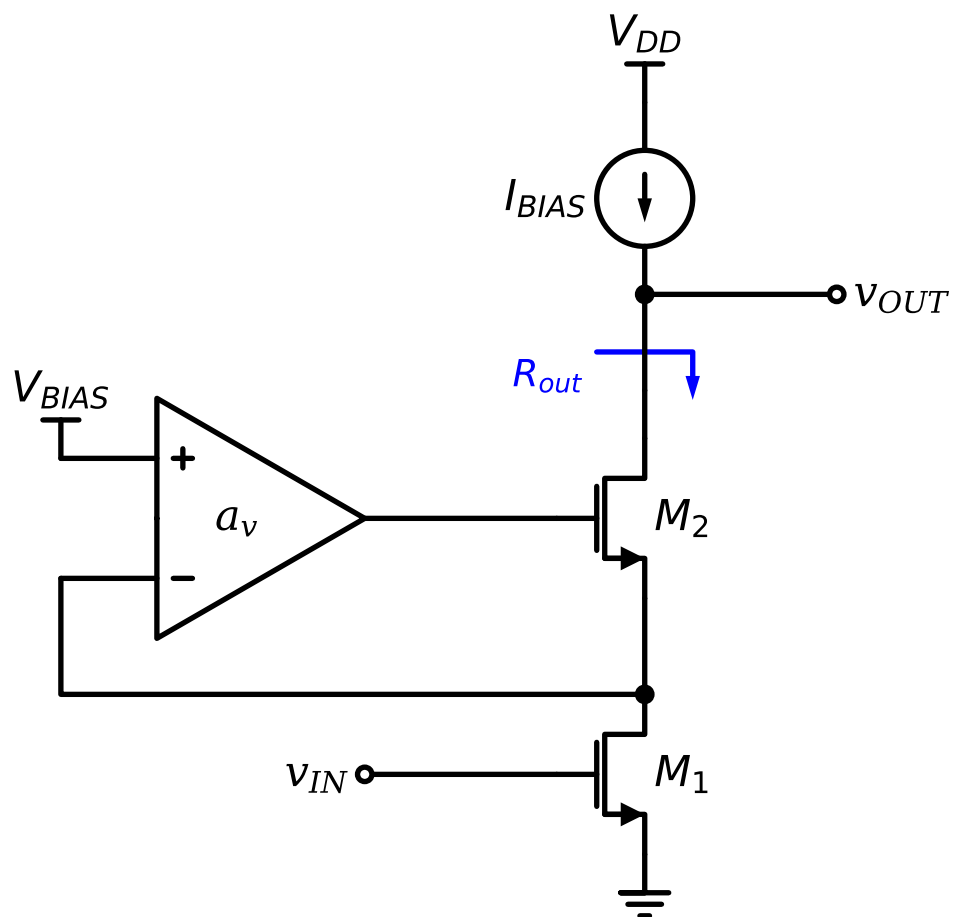


Figure 66: Active cascode gain stage

With  $a_v = 0$  the gate of  $M_2$  gets grounded:

$$R_{out0} \equiv R_{out}(a_v = 0) = r_{o1} + r_{o2} (1 + g'_{m2}) \approx r_{o1} \cdot r_{o2} \cdot g'_{m2}$$

note:  $g'_{m2} = g_{m2} + g_{m2b}$

- To find the return ratio for  $a_v$  with the output port open, we set  $v_{in} = 0$  and leave the output node floating

The current of the  $g_m$ -generators ( $g_{m2}v_{gs2}$  and  $g_{mb2}v_{bs2}$ ) flows only in  $r_{o1}$ , changing the drain voltage of  $M_2$ , but keeping the source voltage of  $M_2$  to  $v_x = 0 \Rightarrow v_d = -v_x = 0$ . Therefore,  $v_r = a_v \cdot v_d = 0$

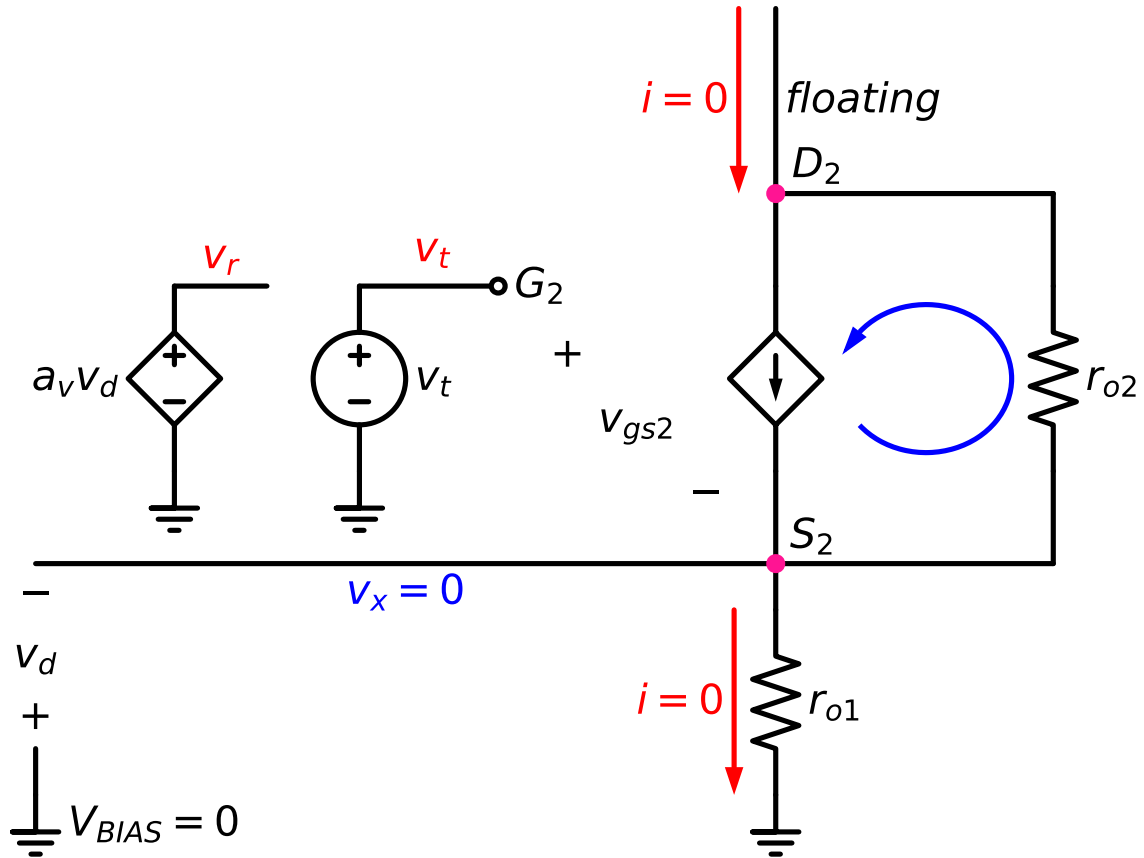


Figure 67: Return ratio for  $a_v$  with the output port open

$$T_{open} = -\frac{v_r}{v_t}|_{open} = 0$$

- 

With  $M_2$  drain to ground (CD),  $v_x = -v_d$  is the output of a CD with  $v_t$  as input. Noting that  $v_t = v_{gs2} - v_d$ , and neglecting the  $r_o$  terms w.r.t. the  $1/g_m$  terms:

so the return ratio is:

- The closed-loop output resistance is:

### Example 14 - Using Blackman's formula for ZVTC calculations

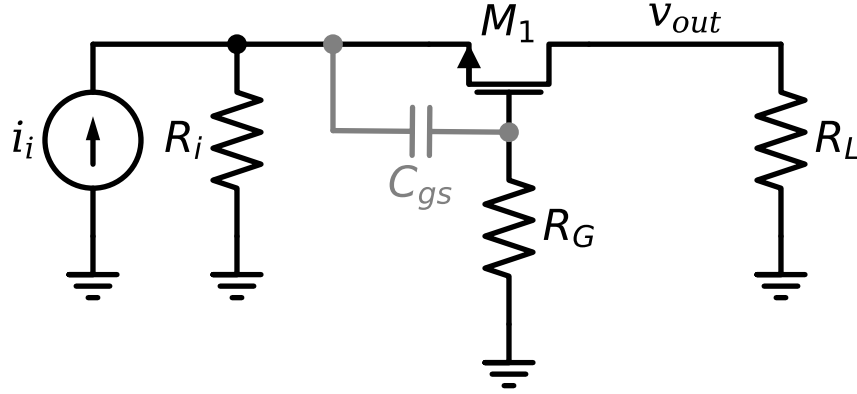


Figure 69: ZVTC calculations

Using first principles (KVL and KCL) we can derive that:

$$\tau_{C_{gs}} = C_{gs} \cdot \frac{R_i + R_G}{1 + g_m R_i}$$

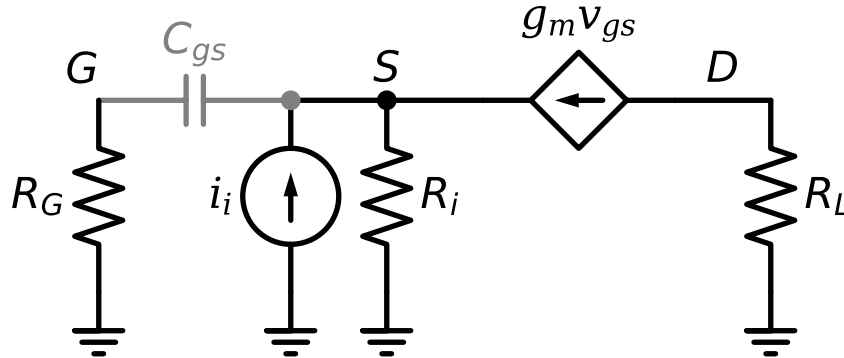


Figure 70: Small signal model for ZVTC calculations, assuming  $r_o$  can be ignored

Let's look at the problem, using return ratio.

The port (gate-source) impedance with the return ratio's gain element  $g_m$  set to 0 is:

$$R_{gs}(g_m = 0) = R_i + R_G$$

The return ratio for the gain element  $g_m$  with port under consideration shorted is:

$$T_{sc} = -\frac{i_r}{i_t}|_{sc} = 0$$

Shorting the port forces  $v_{gs} = 0$  so it "kills" the  $g_m$  generator.

The return ratio for the gain element  $g_m$  with port under consideration open is:

$$T_{open} = -\frac{i_r}{i_t}|_{open} = g_m \cdot R_i$$

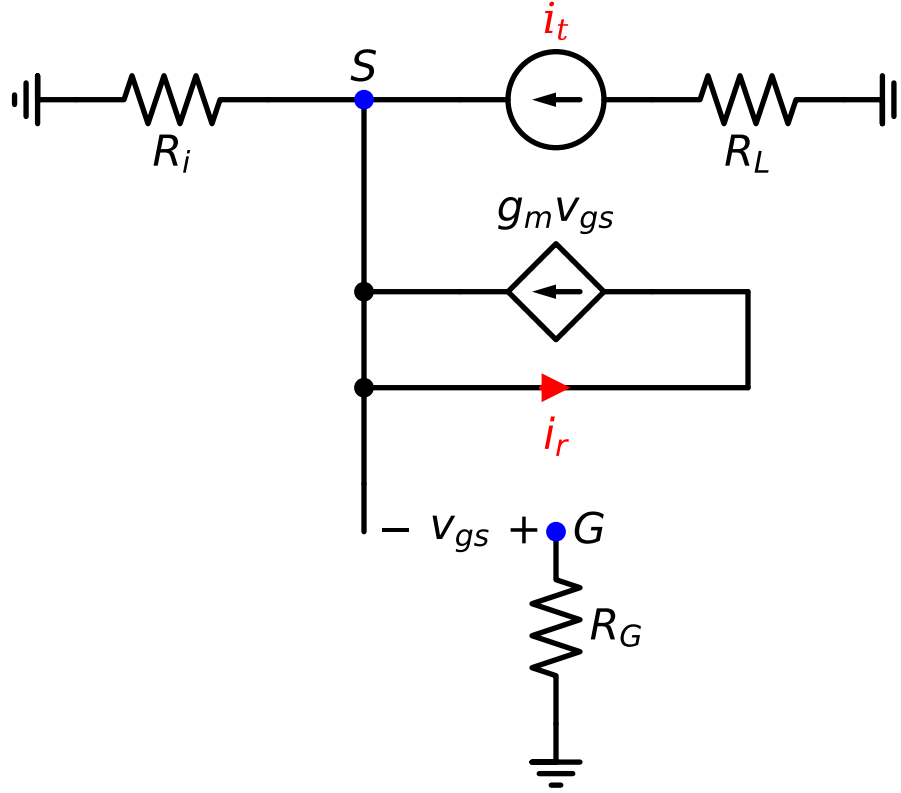


Figure 71: return ratio with port G-S open

$$v_s = i_t \cdot R_i$$

$$v_g = 0 \Rightarrow v_{gs} = -i_t \cdot R_i$$

$$i_r = g_m v_{gs} = -g_m R_i i_t$$

The closed-loop port impedance between G and S is:

$$R_{gs} = R_{gs}(g_m = 0) \cdot \frac{1 + T_{sc}}{1 + T_{open}} = \frac{R_i + R_G}{1 + g_m R_i}$$

### 10.1.3 Summary - return ratio analysis

- Return-ratio analysis is an alternative approach to two-port feedback analysis.

- Provided the return ratio  $T$  is computed for a dependent source that breaks the feedback loop globally, the return ratio is a measure of loop gain. In general, the return ratio of a controlled source is a measure of how much of the signal generated by that controlled source is returned due to feedback, it is not necessarily the loop gain. (Hurst 1992)
- For negative feedback circuits  $T > 0$
- In an ideal feedback system  $T \rightarrow \infty$  and the closed loop gain is  $A_\infty$
- Blackman's formula gives the closed-loop impedance in terms of two return-ratios. The formula is the same for any type of feedback circuit, and it applies to any port (not only the input and output ports)
- Return-ratio analysis is often simpler than two-port analysis
- Return-ratio analysis uses equations that are independent of the type of feedback.
- Two-port analysis uses four-feedback configurations (series-series, series-shunt, shunt-series, and shunt-shunt), therefore, the type of feedback must be correctly identified before starting the analysis
- In practice, all physical networks are multiloop feedback structures. Unwanted local return loops exist around individual transistor through the parasitic capacitances (Tian et al. 2001). Dealing with multiple feedback mechanisms makes identifying an appropriate controlled source to use for the return ratio analysis more difficult. When dealing with multiloop feedback structures, the controlled source used to compute the return ratio, must be one that breaks the loop globally (Hurst and Lewis 1995).
- One aspect that is often cause of confusion, about return-ratio analysis and two-port analysis is that the loop gain  $L$  computed through two-port analysis and the loop gain  $T$  computed using the return ratio, can be different. This is because they are intrinsically two different measures of transmission, however both methods lead to correct closed-loop expressions and both can be used to check stability (Chiu 2012).

**Example 15 - Voltage gain and output resistance of common source with degeneration using return ratio**

*voltage gain (assuming  $r_o$  negligible)*

$$A_v = \frac{v_{out}}{v_{in}} = A_\infty \cdot \frac{T}{1+T} + \frac{d}{1+T}$$

$A_\infty$  is the gain of the circuit when the gain element  $k$  of the controlled source tends to  $\infty$  (note that if  $k = g_m = \infty$ , for the current of the dependent source to be finite, it must be  $v_{gs} = 0$ ).

$$A_\infty = \left. \frac{v_{out}}{v_{in}} \right|_{g_m \rightarrow \infty} = -\frac{R_D}{R_S}$$

$d$  is the gain of the circuit when the gain element  $k$  of the controlled source equals 0.

$$d = \left. \frac{v_{out}}{v_{in}} \right|_{g_m=0} = 0$$



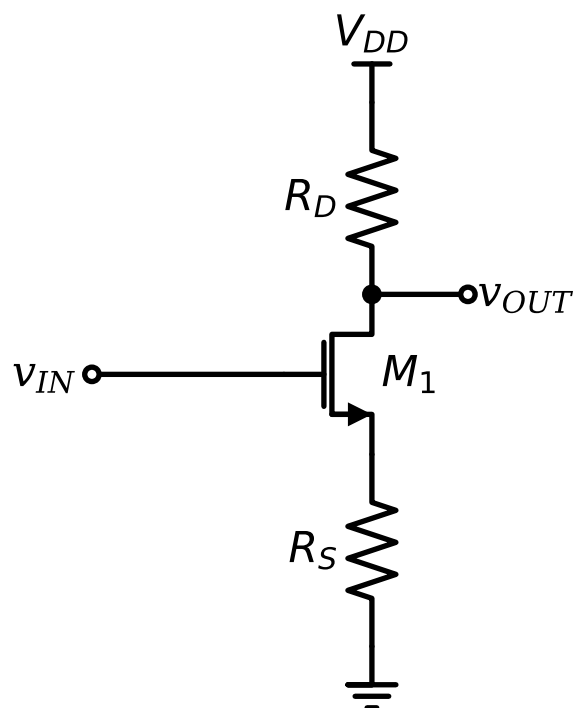


Figure 72: Common source with degeneration

$T$  is the return ratio of the dependent source.

To compute the return ratio instead of separating the dependent source from the rest of the circuit and replacing it with an independent source of the same kind as always done so far, we will follow an equivalent procedure consisting in adding an independent source  $s_x$ . In practice, this procedure is usually more easily performed, because it does not require tearing the original circuit apart. See (Middlebrook 2006) and (Hajimiri 2023).

The introduction of  $s_x$  is completely equivalent to using an independent source  $s_t$  in place of the separated dependent source and monitoring the signal  $s_r$  that returns to the separated dependent source.

$$s_t = s_x + s_r$$

$$v_{gs} = -i_t R_S$$

$$i_r = g_m v_{gs} = -g_m R_S i_t$$

$$T = -\frac{i_r}{i_t} = g_m R_S$$

Therefore, as expected:

$$A_v = \frac{v_{out}}{v_{in}} = A_\infty \cdot \frac{T}{1+T} + \frac{d}{1+T} = \frac{-g_m R_D}{1+g_m R_S}$$

### *Output resistance*

To find the output resistance we use Blackman's formula.

The output resistance with  $g_m = 0$  is:

$$R_{out}(g_m = 0) = R_S = r_o$$

With the output port open:

$$v_{gs} = -i_t R_S = 0 \Rightarrow i_r = g_m v_{gs} = 0$$

So, the return ratio with the output port open is:

$$T_{open} = -\frac{i_r}{i_t}|_{open} = 0$$

With the output port shorted:

$$v_{gs} = -(R_S || r_o) \cdot i_t \Rightarrow i_r = g_m v_{gs} = -g_m \cdot (R_S || r_o) \cdot i_t$$

So, the return ratio with the output port shorted is:

$$T_{sc} = -\frac{i_r}{i_t}|_{sc} = g_m (R_S || r_o)$$

And the output resistance is:

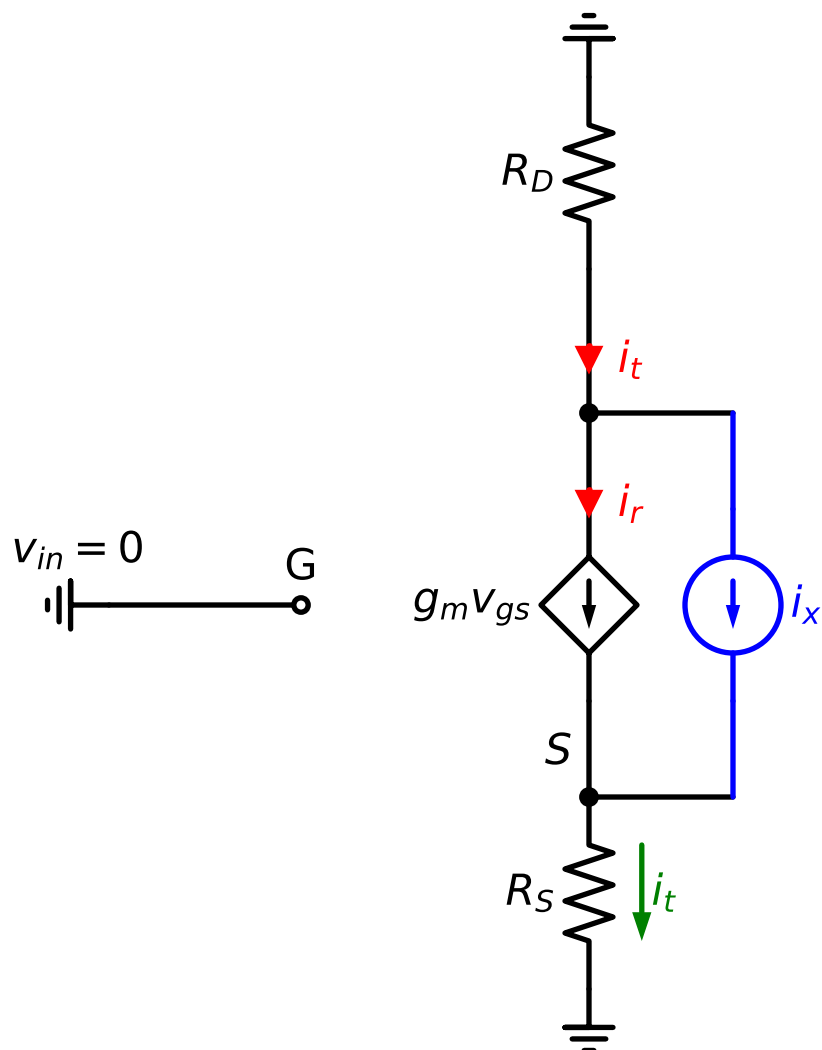


Figure 73: Small signal model to find the return ratio of  $g_m$

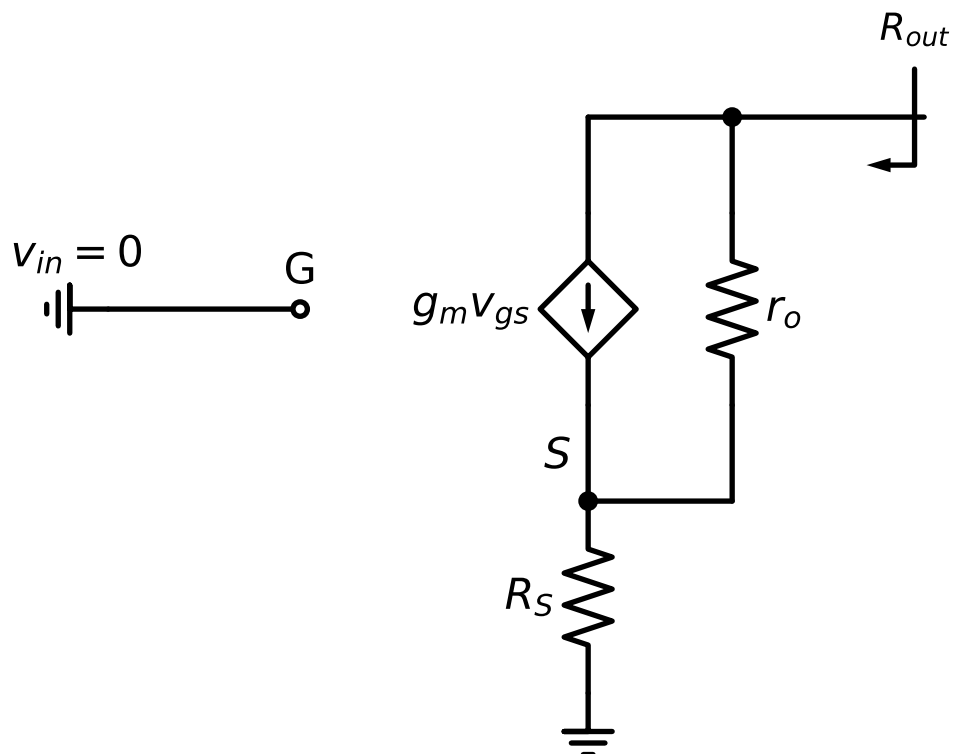


Figure 74: Small signal model to find the output resistance

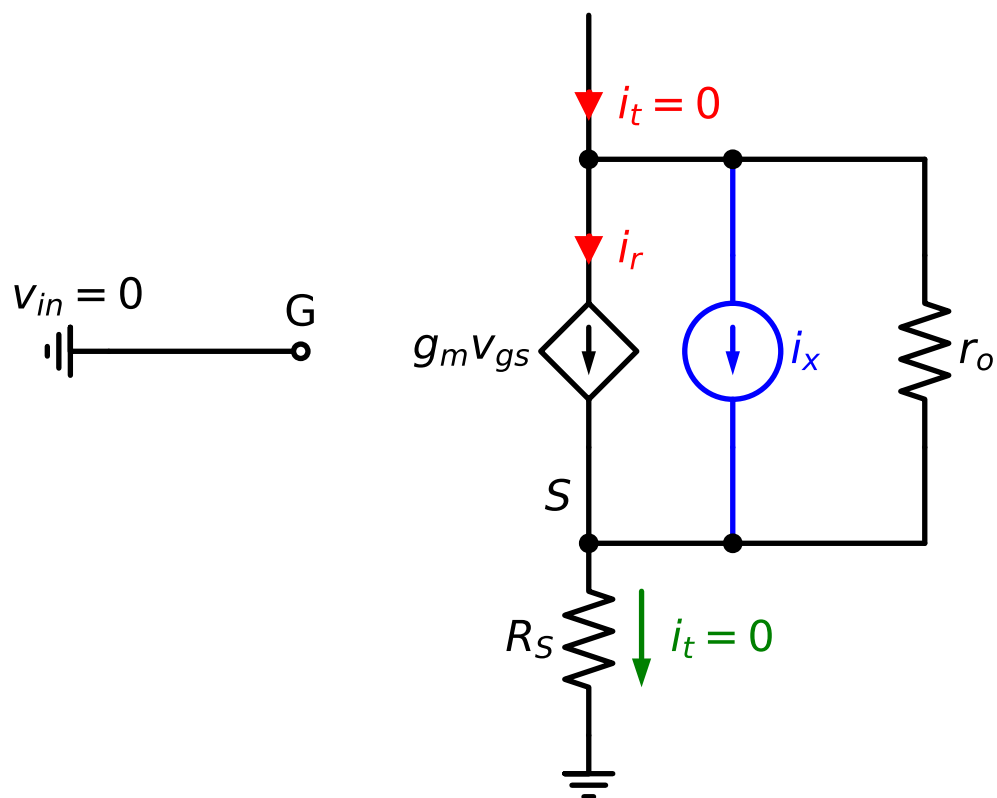


Figure 75: return ratio with output port open

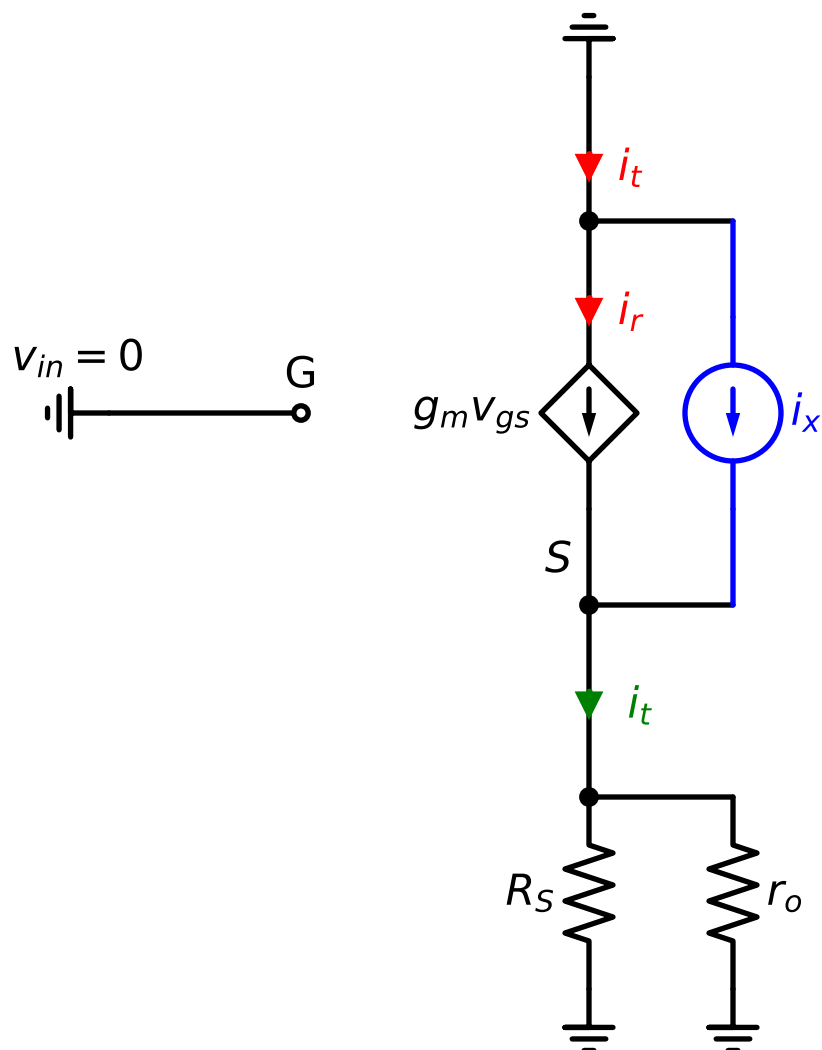


Figure 76: return ratio with output port shorted

$$\begin{aligned}
R_{out} &= R_{out}(g_m = 0) \cdot \frac{1 + T_{sc}}{1 + T_{open}} = (R_S + r_o) \left( 1 + g_m \frac{R_S r_o}{R_S + r_o} \right) = \\
&= R_S + r_o(1 + g_m R_S)
\end{aligned}$$

- Chiu, Yun. 2012. “Demystifying Bilateral Feedback Analysis.” In *2012 IEEE 11th International Conference on Solid-State and Integrated Circuit Technology*, 1–4. <https://doi.org/10.1109/ICSICT.2012.6467588>.
- Franco, Sergio. 2015. *Analog Circuit Design: Discrete & Integrated*. New York: McGraw-Hill Education.
- Gray, Paul R, Paul J Hurst, Stephen H Lewis, and Robert G Meyer. 2009. *Analysis and Design of Analog Integrated Circuits*. John Wiley & Sons, 4/e.
- Hajimiri, Ali. 2023. “Analog. Inexact Science, Vibrant Art.” 2023. [https://chic.caltech.edu/wp-content/uploads/2023/01/Hajimiri\\_Analog\\_DRAFT012023.pdf](https://chic.caltech.edu/wp-content/uploads/2023/01/Hajimiri_Analog_DRAFT012023.pdf).
- Hurst, P. J. 1991. “Exact Simulation of Feedback Circuit Parameters.” *IEEE Transactions on Circuits and Systems* 38 (11): 1382–89. <https://doi.org/10.1109/31.99170>.
- . 1992. “A Comparison of Two Approaches to Feedback Circuit Analysis.” *IEEE Transactions on Education* 35 (3): 253–61. <https://doi.org/10.1109/13.144656>.
- Hurst, P. J., and S. H. Lewis. 1995. “Determination of Stability Using Return Ratios in Balanced Fully Differential Feedback Circuits.” *IEEE Transactions on Circuits and Systems II: Analog and Digital Signal Processing* 42 (12): 805–17. <https://doi.org/10.1109/82.476178>.
- Middlebrook, R. D. 2006. “The General Feedback Theorem: A Final Solution for Feedback Systems.” *IEEE Microwave Magazine* 7 (2): 50–63. <https://doi.org/10.1109/MMW.2006.1634022>.
- Tian, M., V. Visvanathan, J. Hantgan, and K. Kundert. 2001. “Striving for Small-Signal Stability.” *IEEE Circuits and Devices Magazine* 17 (1): 31–41. <https://doi.org/10.1109/101.900125>.